

INDEX

A

AC-to-DC power supplies, 284-288
 Accessory noise, 357
 Active filter, 58
 Active mixer, 96, 146
 Adjacent-channel rejection, 17, 101, 233
 AGC (Automatic Gain Control), 3, 91, 92, 101, 109-113, 115, 123, 139, 142, 250, 265-268
 troubleshooting, 105, 117, 268
 ALC (Automatic Level Control), 5, 182, 248-251, 266, 269
 AM (Amplitude Modulation), See Modulation
 AMC (Automatic Modulation Control), 5, 182, 190, 223, 250, 269
 ANL (Automatic Noise Limiter), 106, 108, 113, 141
 Alignment:
 AM/FM receiver, 13, 14, 139-142
 AM/FM transmitter, 204, 205
 PLL synthesizer, 80, 81, 269
 SSB transceiver, 253, 268-272
 tools, 8, 81
 Alternator noise, 357
 Amateur band conversions, 74, 223
 Amateur radio suppliers, 20, 21
 Amplified AGC, 111, 267
 Amplified squelch, 125, 266
 Amplifier:
 audio, 128-133, 178, 182
 biasing, 30, 34, 35, 36, 43-45, 47, 62, 95, 149, 150, 152-154, 162, 189, 190, 238-247
 Class A, 35, 95, 129, 149, 150, 162, 175, 238
 Class AB, 153, 155, 209, 238
 Class B, 16, 131, 154, 223, 238
 Class C, 43, 62, 150, 151, 153, 155, 162, 166, 171, 175, 188, 189, 235, 238, 253, 254
 Common Base, 32, 89
 Common Emitter, 32, 89, 92, 101, 116, 129, 179
 Common Collector (Emitter Follower), 32, 101, 281
 duty cycle, 241, 242
 efficiency, 150, 172
 error sensing, 283, 285, 294
 Field Effect Transistor (FET), 32, 39, 89, 94, 98
 Final, 27, 28, 146, 149, 150, 153, 156, 157, 162, 164, 168, 172, 173, 175, 204, 240, 243, 246, 248, 254, 280, 298, 303, 312, 313, 316, 345, 352
 IC audio, 131
 instability, 152, 239
 Intermediate Frequency (IF), 99-106, 256, 265, 266
 phase, 32, 89, 116
 Radio Frequency (RF), 149-157
 speech, 171, 178-182
 stability measures, 152, 153, 156, 162
 troubleshooting, 34-36, 131
 voltage, 150, 178, 238, 267, 297
 Amplitude Modulation (AM),
 See Modulation
 AN612 IC, 226, 229

Antenna:
 balun, 348
 bandwidth, 319, 330, 335, 336, 352
 base-loaded, 320, 323, 325, 335, 336, 340, 341
 base station, 311, 322, 323, 326, 329-332, 343, 346-351
 beam, 306, 320, 321, 343
 center-loaded, 323, 325
 coaxial type, 350
 coaxial cable, 312-314, 319, 340, 355
 connectors, 318, 319
 cophase, 321, 327, 328, 341, 343, 344, 345
 current, 309, 312, 313, 323-327, 334, 337, 341, 347, 348, 350
 dipole, 321, 322, 329, 332, 334, 350
 directional, 308, 320, 327-333, 341
 director, 329, 330
 driven array, 320
 dummy load, 6, 7, 343, 345, 346, 357
 effect on reception, 305, 306
 elements, 329
 elevation angle, 320-323, 325, 335
 failure symptoms, 303
 Front-to-Back (F/B) ratio, 321, 329, 330, 332
 gain, 306, 320, 321, 329, 330, 332, 337, 341, 347
 Gamma match, 347
 ground plane, 323, 334, 335, 341, 350-352
 grounding, 340, 341, 347, 355
 half-wave, 309-312, 322, 334
 height, 322, 330, 334, 335
 helically-wound, 309, 323, 351
 horizontal, 328, 329
 impedance, 309, 311, 312, 314, 330, 334-336, 339-341, 343, 346, 350, 351
 isotropic radiator, 320, 321
 L/D ratio, 319, 320, 351
 loading, 303, 304, 310, 311, 320, 323, 325, 335, 336, 339, 349, 351
 magnetic, 335, 340, 341, 357
 manufacturers, 22
 marine, 350, 351
 matcher (tuner), 310, 315, 316, 320, 345
 matching, 194, 306, 310, 312, 313, 320, 334-352
 mobile, 304, 323, 325, 327, 335-346
 mounting, 304, 323, 325, 338-342
 no-ground-plane, 351
 omnidirectional, 320, 323-327, 335, 337, 346
 phase, 306, 309, 310, 312, 320, 322, 325-328, 330, 332, 341
 polarization, 308, 309, 321, 325, 329, 330, 332
 Polar Diversity Loop (PDL), 332, 333
 power ratio chart, 321
 Quad, 320, 330, 331, 332
 quarter-wave, 326, 327, 334, 335, 337
 radials, 335, 346, 349, 350
 radiation angle, 323, 325-327, 332, 337, 347, 350

radiation pattern, 321-324, 330, 341, 349
 radiation resistance, 311, 312, 314, 320, 323, 324, 332, 335, 338, 347, 350
 range, 303, 308, 321, 323, 325, 336, 337
 reactance, 5, 7, 311, 315, 319, 320, 323, 325, 337, 340, 343, 346, 347
 reflector, 329, 330
 rotator, 329, 330
 SWR (Standing Wave Ratio) 5, 7, 19, 158, 177, 196, 312-317, 319, 334, 337, 340, 343, 345
 Starduster, 350
 Super Scanner, 332
 top-loaded, 323, 325
 troubleshooting, 313, 336-341
 tuning, 306, 310, 315, 336, 343, 347
 vertical angle of radiation, 320-323, 325, 326, 330
 vertical Polarization, 308, 309, 321, 325, 329, 332
 Yagi, 320, 329, 330, 343
 Antenna Warning Indicator (AWI) circuit, 197, 303
 AT crystal cut, 42
 Attenuator, 20 dB T-pad, 12
 Audio amplifier, 128-133, 178, 182
 Audio-derived AGC, 110
 Audio detector, 106, 107
 "Audio Distortion" symptom, 28, 30, 103, 105, 106, 109, 111, 112, 126, 128-131, 133, 134, 154, 179, 206, 207, 241, 252, 268
 Audio Driver stage, 129
 Audio frequency response, 5, 18, 106, 131
 Audio output stage, 128-133
 Audio power calculations, 142
 Audio troubleshooting, 106, 132-134, 192
 Automobile electrical system, 16, 277, 356, 357
 Autoranging VOM, 3
 Average power, 171, 208, 241

B

Balanced Demodulator, 229, 256-258
 Balanced Detector, 259
 Balanced mixer, 96, 208, 235, 257
 Balanced Modulator, 192, 200, 208, 223-229, 251, 252
 diode ring circuit, 225, 226
 IC circuit, 226
 troubleshooting, 229
 Bandpass filter, 102, 103, 139, 147, 148, 231, 236, 237
 Bandpass tuning, 139
 Bandspeed circuit, 50, 51
 Bandwidth, 17, 22, 63, 104, 166, 188, 191, 200, 206-208, 229, 231, 233, 252, 319, 320, 330, 351, 352
 Base-leak bias, 152, 162

Base loading, 320, 323, 325, 335, 336, 340, 341
 Base station antennas, 311, 329-332, 343, 346-351
 Base station power supply, 284-288
 Beat Frequency Oscillator (BFO), 200
 Bias:
 in amplifier, 47, 62, 92, 149, 151, 152, 162, 182, 238-241, 251, 294
 in RF power amplifier, 151-154, 156, 251, 269
 in tube circuits, 153, 154, 239, 284, 286
 interpreting measurements, 29, 34-36, 111
 stabilizing, 131, 152, 239-241, 297
 switching in AM/SSB transceivers, 153, 239
 Bipolar transistor, 31-34, 43, 50, 89, 94, 96, 98, 101, 147, 178, 198, 266
 Binary Coded Decimal (BCD), 64, 66, 68
 Binary numbering system, 65, 66
 Binary PLL programming, 65
 Bleedover, 17, 102, 103, 105, 124, 167, 182, 206, 238, 252
 Block diagrams:
 basic AM/FM transceiver, 27
 basic SSB transceiver, 208
 FM Detector IC, 119
 noise blanker, 114
 PLL synthesizer, 55, 56, 60-62, 67, 69, 73, 76-80
 scan circuit, 127
 Speech Processor, 169
 SSB crystal synthesizer, 216-218, 220-222
 "Blows Fuses" symptom, 35, 36, 41, 128, 131, 133, 146, 155, 247, 279, 280, 298-300
 Bootstrap circuit, 131
 Bridge rectifier, 284, 290
 British CB, See UK CB
 Broadbanding, 63, 71, 74, 75, 319, 320
 Buffer, 101, 149, 150, 152, 226, 267
 "Buzz-it" RF generator, 5
 Bypass capacitor, 30, 106, 129, 133, 154, 175, 179, 181, 226, 238, 278, 356, 357

C

Capacitance meter, 8, 47
 Capture effect, 101
 Carrier balance, 224-226, 269
 Carrier insertion, 211, 229, 266
 Carrier offset methods, 209-233
 Carrier Oscillator, 48, 209-212, 215, 226, 229, 231, 235, 256, 258, 266, 292, 294
 Carrier power control, 241-247, 269
 Carrier shift, 167
 Carrier squelch, 121, 124, 125
 Carrier suppression, 16, 206, 223, 225, 226, 229, 232-235, 252, 259, 269
 Cathode bias, in vacuum tubes, 153-155, 175
 CB radio manufacturers, 22
 CB-to-10M Amateur conversion, 74, 223
 Ceramic IF filter, 101, 103-105, 106, 210
 Channel Selector, 61, 66, 72, 135, 256
 Charge pump, 58
 Circular Polarization, 308

Clamp, 3, 82, 92, 93, 95, 173, 198, 247, 266-268, 281, 292
 Clarifier, 8, 19, 45, 47, 48, 50, 57, 62, 85, 123, 136, 137, 200, 207, 223, 256, 260-265
 "Clarifier Doesn't Work" symptom, 47, 264, 298, 301
 Clipping:
 in ANL circuit, 108, 109, 113
 in FM use, 117, 118, 190
 in speech circuits, 96, 168
 RF peak, 253, 254
 CMOS, 65, 82, 84, 127, 286
 Coax cable:
 characteristics of, 311, 312, 314, 317
 connector installation, 318
 length effect on SWR, 313, 314, 316
 losses, 315-319
 radiation, 347, 348
 splicing, 318
 transformer, 343, 350
 Coaxial antenna, 350
 Coaxial capacitor, 357
 Coil impedance, 63, 93, 123, 237, 339
 Colpitts oscillator, See Oscillator
 Common Base amplifier, 32, 89
 Common Collector (Emitter Follower), 32, 101, 281
 Common Emitter amplifier, 32, 89, 92, 101, 116, 129, 179
 Common Gate RF amp, 94, 95
 Common Source RF amp, 95
 Comparator:
 in PLL circuit, 58
 op-amp, 199, 297
 voltage, 199, 200
 Conventional current flow, 32, 38, 267
 Conversion, 74, 223, 235
 Converter, 96, 284
 Cophasing, in antenna, 327, 328, 341, 343
 Coupling, 101, 103, 168, 178
 Coupling transformer, 99, 104, 109, 235
 "Cracked Tuning Slug" symptom, 81
 Cross modulation, 17, 95, 96, 237
 Crystal:
 construction, 42, 43
 14-crystal synthesizer, 51, 52
 holder types, 46
 how to order, 48
 IF filter, 16, 89, 103, 209, 229-235, 265
 oscillator, 11, 42-44
 parallel-mode operation, 43, 48, 233
 series-mode operation, 43, 45, 48, 104, 211, 212, 233
 SSB synthesizer, 214-222
 suppliers, 25
 troubleshooting in oscillators, 47, 48, 53
 12-crystal synthesizer, 53-55
 Crystal mixing, in Walkie-Talkies, 49
 Crystal mixing charts:
 23-channel AM, 52, 54, 87, 88
 23-channel SSB, 273-276
 Crystal synthesizer, 51-55, 87, 88, 136, 146, 147, 214-222
 Crystal checker, 11, 47
 Current detector, 107
 Current distribution, in antenna, 323, 325, 347, 348
 Current drain specification, 16
 Current Feed, See Antenna
 Current limiting, 30, 131, 280, 281, 283, 297, 301
 Current fed antenna, 309

Current loop & node, in antenna, 309, 312, 326
 CW keying circuit, 200, 201

D

D Flip-Flop, 64
 Darlington amplifier, 173, 245, 246, 283, 284
 dBm, 13, 109, 178
 DC amplifier, 101, 111, 123, 125, 180, 266, 267, 281
 DC coupling, 101, 104, 123
 DC grounding, in antenna, 340, 357
 DC switching, 31, 32, 38, 123, 201, 202, 247, 262, 263 290-297, 280, 281, 288
 DC-to-DC converter, 288-290
 "Dead Carrier" symptom, 163, 175, 247
 "Dead Channel(s)" symptom, 49, 53, 81, 272
 "Dead Radio" symptom, 263, 280, 283, 299
 Decibel (dB), 13, 321
 De-emphasis, 119, 120
 Degenerative (Negative) feedback, 95, 98, 101, 102, 104, 131, 155, 156, 175, 179, 181, 247
 Delayed AGC, 109, 110
 Delta Tune, 45, 50, 57, 62, 123, 136-138
 Desensitization, in receiver, 96, 101
 Detectors:
 AGC, 109-111, 265-268
 audio, 106, 107, 129, 139
 current, 107
 failure symptoms, 106, 123
 FM, 117-123, 139
 half-wave, 106, 108
 meter, 106, 112, 312
 SSB, 256-260
 troubleshooting, 111
 Deviation, See FM
 Device, understanding markings, 39
 Difference amplifier, 297
 Differential Peak Detector, 120
 Digital divider, 63-68
 Digital PLL programming, 65-68
 Digital VOM, 3, 269
 Diode ring Balanced Modulator, 225, 226, 229
 Diode:
 detector, 106-111, 117, 139, 256, 312
 germanium, 36, 95, 96, 106, 107, 110, 112, 114, 182, 192, 258
 isolation, 131, 173, 245, 251, 267, 268, 280, 294
 mixer, 96, 257
 reverse-polarity, 279, 284, 298
 RF overload protection, 92, 93, 162
 silicon, 36, 106-108, 131, 182, 192, 225, 226, 240, 241, 258, 285
 surge protection, 281, 292
 testing with ohmmeter, 36
 varactor, 56, 189, 260, 263-265, 301
 Zener regulator, 280, 281, 301, 302
 Dipole antenna, See Antenna
 Directional antenna, See Antenna
 Directional RF coupler, 195
 "Distorted Audio" symptom, 28, 30, 103, 105, 106, 109, 111, 112, 126, 128-131, 133, 134, 154, 179, 206, 207, 241, 252, 268
 Distortion test, 141-142
 Disturbance checks, 26, 28

Double Sideband (DSB), 209
 Downmixer stage, 61, 73, 82
 Downward modulation, 165, 167, 168, 247
 Dual-conversion receiver, See Receiver
 Dynamic mike, 9, 14, 171, 177, 178
 Dynamic range, 18, 91, 95, 96, 101, 109, 111, 257, 267
 Dummy load, 6, 7, 168, 197, 198, 252, 345, 346, 357

E

Efficiency, 30, 43, 62, 63, 129, 150, 151, 153, 154, 172, 188, 238, 240, 303, 306, 308, 312, 335, 337, 341
 EIA specifications, 18, 140, 142
 EIAJ device markings, 39
 Electronic I/R switching, 93, 132, 162, 238, 248, 260, 280, 281, 290, 292-297, 299
 Electronic voltage regulation, 281, 283
 Emitter ballasting, 152
 Emitter Follower, 32, 101, 281
 Envelope measurement, See Modulation
 Error amplifier, 283, 285, 294
 Even-order product, 129, 130, 252
 Expanded channel methods, See Frequency
 Export model radios, 3, 8, 16, 22, 25, 63, 71-75, 78, 81, 101, 117, 121, 127, 135, 140, 156, 157, 168, 172, 187, 189, 192, 199-201, 234, 246, 247, 251, 265, 268, 277, 292, 294, 320
 External speaker, 9, 133

F

FCC license requirements, 20
 FCC, 14, 16, 17, 50, 66, 137, 138, 161, 166, 182, 184, 200, 206, 207, 234, 252, 253, 256, 260
 Feedback, 43, 44, 47, 50, 58, 98, 101, 104, 131, 155, 156, 162, 175, 177, 179, 180-182, 248, 281, 283, 285, 297
 FET (Field Effect Transistor):
 in AGC circuit, 266, 267
 in mixer, 31, 89, 98, 147
 in RF amplifier, 32, 94
 testing with VOM, 39
 Filament, in tube, 26, 41, 277, 284, 286, 290
 Filter:
 High-pass, 355
 IF, 16, 89, 103, 119, 209, 229-235, 265
 Low-pass, 57-59, 63, 106, 158, 190, 353, 354
 noise, 279, 356, 357
 Final RF amplifier, See Amplifier
 Flat-topping, 168, 187, 253, 254
 Flip-flop, 58, 60, 64, 65, 127
 Floating chassis, 16, 277
 Flywheel effect, 130, 151, 238
 FM (Frequency Modulation), 7, 57, 103, 117-123, 139, 187-192
 alignment, 120, 123, 140, 141
 characteristics of, 16-18, 187, 188
 detector, 117, 119-121
 deviation, 4, 7, 103, 117, 163, 188, 190, 204

deviation meter, 7, 8, 204, 205
 receiver troubleshooting, 119, 123
 sensitivity rating, 17, 117
 signal generator, 3, 123
 transmitter troubleshooting, 192
 varactor modulation, 57, 189-191
 Freon flux solvent, 10
 Frequency:
 channel chart, 75, 358
 divider, 63-68
 downmix stage, 61, 73, 82
 expansion, 71-74
 filtering, 57-59, 63, 106, 119, 120, 179
 fundamental, 45
 image, 101, 101
 modulation, See FM
 multiplication, 45, 62, 188, 189
 offset, 8, 209, 211, 214, 223, 229, 256, 260, 292
 reference, 56, 58, 69
 response, 5, 17, 18, 131, 138, 142, 179, 191, 192
 selection pin on PLL IC, 70
 Frequency conversion, 61, 62, 96, 209, 256
 Frequency Counter, 4, 11, 29, 47, 49, 81, 99, 149, 187, 238, 336
 Frequency stability, See Stability
 Frequency synthesizer, See Synthesizer
 Frequency tolerance, 14
 Front-end, 91, 94, 109, 110, 114, 116, 124, 139, 162, 267, 281
 Front-end overload, 91, 92, 94, 140, 162, 354, 355
 Front-to-Back ratio, 321, 329, 330
 Full-wave rectifier circuit, 284, 286, 288, 290, 299
 Fuses, 35, 41, 128, 131, 146, 247, 279, 298-300

G

Gain:
 antenna, 306, 320, 321, 329, 330, 332
 power, 321, 332
 RF amplifier, 94
 voltage, 62, 63, 119, 178
 Gamma match, See Antenna
 Generator noise, 357
 Germanium diode, See Diode
 Grid Dip Meter, 8, 336
 Grid-leak bias, 153, 154
 Ground loops, 16, 277, 278, 284, 355, 357
 Ground plane, 334, 335, 341, 351
 Ground wave, 307, 325
 Guy wire effects, 349

H

Half-lattice crystal filter, 233
 Half-wave antenna, See Antenna
 Half-wave detector, See Detector
 Half-wave filter, 159, 160, 163
 Half-wave rectifier, 286

Harmonic:
 in audio stage, 129, 166, 168, 190, 226
 in CW circuit, 200
 in PLL circuit, 58
 in mixer stage, 96, 147, 237, 252, 257
 in RF/IF stage, 16, 17, 45, 58, 62, 63, 114, 152, 154, 158, 163, 198, 226, 237, 257, 353, 354
 Harmonic filter, 158-162, 198, 353
 Heat sink grease, 11
 Heat sinking, 129, 131, 239, 240
 Heterodyne, 16, 51, 89, 163, 207, 235, 256
 "High SWR" symptom, 7, 48, 303, 312, 318, 323, 336, 337, 339, 340, 343, 345, 347, 349
 High-level modulation, 16, 171, 242
 High-side mixer injection, 50, 62, 99, 149, 213-215, 219, 235
 High-voltage precautions, 155, 175, 329
 "Hum" symptom, 41, 128, 129, 133, 134, 284, 300
 Human senses, use in testing, 40, 41

I

IC:
 audio amplifier, 129, 131, 181, 189, 190
 balanced modulator, 226
 mixer, 237
 Noise Blanker, 116
 voltage regulator, 292, 296, 297, 301
 IC Master Reference Book, 40
 IC part substitutions:
 audio & squelch, 126, 133, 268
 FM detector, 123
 Noise Blanker amp, 116
 voltage regulator, 292, 297
 IC troubleshooting, 30, 31, 129, 133, 194, 229, 297
 IF (Intermediate Frequency), 18, 49, 55, 69, 96, 209
 alignment in receivers, 105, 140, 269
 IF amplifier, 99-106, 256, 263, 266
 failure symptoms, 105
 troubleshooting, 5, 105, 106
 IF filter, 16, 89, 103, 119, 209, 229-235, 265
 IF/RF-derived AGC, 110, 266
 IF selectivity, 16, 102-105, 119, 136, 140, 207, 233
 Ignition noise, 113, 114, 187, 279, 309, 341, 355-357
 Image frequency, 100, 101
 Image rejection, 18, 89, 100, 101, 233
 Impedance:
 antenna & coax, 17, 309, 311, 312, 314, 318, 330, 334-336, 339-341, 343, 346, 350, 351
 calculation in RF power stage, 158, 159
 effects of, 4, 63, 101, 104, 169, 226, 234, 237, 266, 278
 in audio amplifier, 18, 129, 131, 175, 179
 inverter, 314, 315, 336
 of microphone, 14, 32, 176, 181
 of op-amp, 58
 of RF/IF amplifier, 43, 75, 92, 94, 95, 101, 152, 158, 168, 248, 313
 repeater, 160, 314, 336, 343
 Input voltage, 14, 286

Interference:

adjacent-channel (bleedover), 16, 17, 102, 103, 105, 124, 167, 182, 206, 233, 238, 252
ignition noise, 113, 114, 279, 341, 356, 357
RFI, 278, 353-356
TVI, 278, 347, 348, 353-356
Intermittents, 26, 28, 41, 46, 47, 303, 341
Intermodulation distortion (IMD), 16, 93, 94, 96, 98, 99, 237, 238, 252, 253, 354
Inverse Square Law, 306, 321
Isolation diode, 131, 173, 212, 226, 245, 250, 251, 259, 260, 263, 268, 280, 294, 297
Isolation in mixer ports, 96, 99
Isotropic radiator, 320, 321

L

Lamps, meter, 41, 298, 301
LC7130/LC7131 PLL IC, 62, 68, 78
Lead identification, 39, 135, 242
Leakage, in capacitors, 47, 179, 299, 300, 356
Leakage, testing in semiconductor, 37, 39
Least Significant Digit (LSD), 65
LED bar/graph display, 112, 113, 192-194
LED channel display, 26, 41, 71, 134-136, 292, 301
LED T/R indicator, 198
License, FCC study courses, 20
Lightning protection, 340
Light, modulation, 7
Limiting, in FM detector, 17, 117-119
Linear amplifier, 3, 6, 20, 25, 40, 149, 154, 157, 159, 165, 172, 173, 177, 235, 238, 313, 316, 317, 352, 354
Load Capacitance, 48, 104, 264
Loading, effect on circuit, 3-5, 47, 62, 106, 107, 168, 192, 226, 229, 267
Loading, See Antenna
Local-DX switch, in receiver, 92
Local Oscillator (L.O.), 47, 48, 89, 96, 99, 260
Lock Detector circuit, 69, 84, 162, 237, 292, 297
Lock condition in PLL, 58, 59
"Low Volume" symptom, 126, 128, 131, 175
Low-level modulation, 16, 172
Low-Pass filter:
antenna, 158, 160, 198, 316, 353
in detector circuit, 106
in modulator, 170, 190
in PLL circuit, 57-59
"Low Transmit Power" symptom, 47, 48, 81, 146, 149, 152, 163, 206, 237, 247, 303
Lower Sideband (LSB), 166, 206-208
Low-side mixer injection, 50, 99, 149, 213, 214, 235

M

Magnetic antenna, See Antenna
Marine antenna, 310, 320, 345
Master Oscillator, 27, 42, 49, 51, 53, 213, 215, 219, 223

Matcher (Tuner), See Antenna
MB8719/MB8734 PLL IC, 62, 82-84, 292-294
MC145106 PLL IC, 72, 73
MC3357 FM IC, 119, 121, 122, 124
Meters:
FM Deviation, 7, 8, 204, 205
modulation, 26, 192, 194
ohmmeter, 3, 8, 36-39, 96, 106, 126, 133, 186, 229, 298, 299, 339, 340, 351
RF ammeter, 6, 168, 175, 309
S-Meter, 9, 26, 106, 111-113, 128, 139, 141, 184, 192, 266, 268, 272
S/Rf Meter, 26, 192, 205, 269
SWR Meter, 5, 19, 26, 41, 195-197, 205, 312-317, 347
wattmeter, 5-8, 19, 155, 158, 204, 205, 208, 225, 251, 252, 268, 269, 312
Mike amplifier, 171, 178-182

Microphone:

breakdown, 176, 299
cable, 173, 177
ceramic, 176, 181
construction, 177, 178
dynamic, 9, 14, 171, 177, 178
impedance, 14, 32, 134, 176, 181
noise-cancelling, 171
output level, 178
Power (Preamplified), 171
push-to-talk (PTT) switch, 9, 128, 133, 176, 199, 280, 292
replacement parts, 177
"Squeal" symptom, 177
troubleshooting, 10, 133, 176, 177, 299
wiring, 10, 133, 176

Mixers, 96-99, 256-259

failure symptoms, 99, 149
in receivers, 89, 96-99
in transmitters, 146-149, 235-237
troubleshooting, 99, 168, 229, 237, 299
Mixing, 51, 55, 63, 82, 96-98, 146-149, 209, 219, 235, 256
MODE switch, 120, 173, 189, 192, 212, 226, 229, 242, 243, 245, 246, 292, 294, 302

Modulation:

adjustment, 4, 157, 269
Amplitude (AM), 163-175, 246
compressor, 171, 250, 251
downward, 165, 167, 247
dummy load light, 7, 168
envelope measurement, 4, 167, 184
Frequency (FM), See FM
high-level, 171, 172
limiter, 182-184, 250, 251
low-level, 172
measurement of, 167, 184-187, 254, 255
metering circuit, 194
overmodulation, 131, 177
percentage, 166-168
phase, 188
power distribution, 171
processing, 168-170, 178, 182, 189-191, 208, 248
transformer, 129, 131, 279, 302
trapezoidal measurement, 4, 167, 184
troubleshooting, 128, 131, 133, 167, 168, 176, 177, 192, 227, 247
waveforms, 164, 165, 169, 187, 254, 255

Modulation limiter, See AMC

Monolithic filter, 101, 103, 210, 211, 265

MOSFET RF amp, 95

MOSFET RF mixer, 98, 147, 236, 237

Most Significant Digit (MSD), 65

"Motorboating" symptom, 128, 133, 300
Multimeter See VOM
Multiple-lattice filter, 234

N

N-Code, 66, 68, 71, 77, 78
Negative-ground electrical system, 16, 277
Neutralization, 152, 153, 155
Noise Blanker (NB), 11, 113-117, 356
alignment of, 11, 141
failure symptoms, 117
troubleshooting, 104, 117
Noise Figure, 94, 99, 109
Noise filter, 279, 357
Noise squelch, 121, 124
Noise suppression, 106, 108, 109, 117, 187, 279, 357
Non-linear, 16, 62, 96, 166, 171, 174, 175, 187, 197, 223-225, 235, 238, 241, 251, 253-255, 263, 288
Non-synthesized oscillators, 49
"No AGC" symptom, 112, 117
"No Clarifier Control" symptom, 264
"No FM Receive" symptom, 123
"No FM Transmit" symptom, 192
"No LED Display" symptom, 41, 136, 301
"No Oscillation" symptom, 44, 47, 138, 263
"No Receive Audio" symptom, 29, 128, 133, 175, 178, 298
"No Receive" symptom, 47, 53, 81, 91, 93, 99, 111, 112, 117, 139, 206, 268, 297-299, 302, 303
"No Transmit" symptom, 16, 28, 47, 53, 69, 81, 149, 163, 206, 237, 242, 247, 297-299, 303
"No Transmit Audio" symptom, 129, 131, 132, 163, 175, 178, 179, 247, 299

O

Odd-order product, 252
"Off Frequency" symptom, 41, 81, 264, 269, 299, 302
offset frequency, See Frequency
Ohmmeter, 3, 8, 36-39, 96, 106, 126, 133, 186, 229, 298, 299, 339, 340, 351
Omnidirectional antenna, See Antenna
Op-Amp:
in AGC circuit, 266-268
in DC switching, 297
in LED bar/graph, 194
mike preamp, 181, 189, 190
Oscillator:
Armstrong, 290
Colpitts, 11, 48, 44, 47, 50, 57, 136, 209, 231, 260
crystal-controlled, 42-55
downmix, 61, 73, 82
harmonic, 45, 188, 189
offsets, 209-223
overtone, 11, 45, 47, 48
Reference, 58-61, 82
stability, 14, 43, 44, 50, 51, 55, 56, 191, 207, 211, 214, 226, 262, 263, 280

Oscillator, cont'd:
 switching type, 286, 288, 289
 troubleshooting, 3, 47, 48, 53, 82
 voltage-controlled, See VCO

Oscilloscope:
 modulation measurements, 167, 187, 254, 255
 requirements for CB use, 3, 4
 use in troubleshooting, 11, 29, 31, 35, 47, 58, 81, 82, 99, 105, 123, 133, 149, 168, 178, 192, 200, 204, 229, 238, 251, 252, 298
 waveforms, 164, 165, 169, 187, 201, 253-255

Out-of-lock, 60, 81, d4, 146, 237, 297

Output stage, audio power, 128-133

Output stage, RF power, 150-157, 238-247

Overmodulation, 131, 166, 177, 182, 187, 248

Overload protection:
 in DC power supply, 278, 282, 296
 in receiver RF amplifier, 92, 99, 162

Overloading, in receiver, 91, 92, 354

Overtone oscillator, 45, 47, 48

P

PA circuit, 18, 163, 251

"PA Doesn't Work" symptom, 129, 131, 163, 175, 179, 247

Parallel feed, See Shunt Feed

Parallel mode crystal, 43, 48, 233

Parallel-tuned trap, 160, 161

Parts suppliers, 21-25, 103, 177, 299, 302, 315, 336, 340, 345, 349

Passband, 17, 100, 104, 105, 136, 140, 209-212, 231, 233, 256

Passive mixer, 96

Peak-to-Peak (P-P) voltage measurement, 4, 6, 164

Peak reading wattmeter, 6, 19, 208, 251, 252, 268, 269

PEP (Peak Envelope Power) 5, 6, 16, 156, 171, 192, 208, 238, 240-242, 248, 253, 268, 269

Phase Detector, 58, 65, 69, 189

Phase distortion, 188, 207

Phase Inverter Noise Blanker, 115

Phase Modulation (PM), 188

Phase, in amplifiers, 32, 89, 116

Phase, in antenna, See Antenna

Phasing harness, 327, 330, 341, 343-345

Physical feedback, in troubleshooting, 26, 41

Pi Network, 63, 92, 106, 109, 159, 160

Piezoelectric effect, 42, 176

PLL (Phase Locked Loop), 53-86, 127, 149, 256, 260
 alignment of, 80, 81
 block diagrams, 55, 56, 60-62, 67, 69, 73, 76-80
 elements of, 55-61
 failure conditions, 81
 out-of-lock condition, 60, 81, 84, 146, 237, 297
 programming, 65
 troubleshooting, 81-84, 86
 Truth Chart, 66, 68

PLL02A PLL IC, 64, 66, 67, 70, 74, 76

PL259 connector, installing, 318

PNP transistor, See Transistor

Polarization, 37, 308, 309, 321, 325, 329, 330, 332

"Poor Selectivity" symptom, 16, 104, 105, 233

"Poor Sensitivity" symptom, 16, 47, 48, 91, 105, 107, 111, 112, 117, 268, 303, 340

Positive-ground electrical system, 16, 277

Power control, in AM/SSB transceiver, 241-247

Power doubling circuit, 156

Power meter, 5, 6, 26, 81, 192, 269, 312

Power mike, 171

Power, RF calculation, 6

Power ratio, in dB, 13, 321

Power reduction, 157, 158, 241-247

Power Supplies, 277-302
 AC-DC base type, 284-288
 adjustment of, 286
 AM/SSB multimode type, 290-298
 branch circuits, 277, 280, 290, 292, 299, 300, 302
 DC-to-DC type, 288
 interference in mobile CB, 279, 356, 357
 regulation, 281-284
 requirements for CB servicing, 2, 3
 troubleshooting, 16, 277, 279, 290, 298-302
 tube type circuits, 286-288

Power transformer, 286, 300, 302

Pre-emphasis, 119, 120, 188-191

Presetttable divider, 70, 71, 77, 84

Printed circuit board, checking, 11, 26, 41

Product Detector, 256, 258, 259

Programmable Divider, 58-62

Propagation, of radio waves, 307, 308

Push fit coax plug, 8

Push-pull amplifier, 129, 133, 223, 257-259, 280

Push-to-talk (PTT) switch, See Microphone

Q

Q factor:
 in antennas, 319, 320, 351
 in crystals, 43, 45, 233
 in LC circuits, 63, 75, 92, 94, 104, 121, 140, 147, 152, 153, 160, 161, 212, 234-236, 239, 319

Quad antenna, 320, 330-332

Quadrature coil, 120, 121, 139

Quarter-wave antenna, See Antenna

Quarter-wave transformer, 350

R

Radiation angle, See Antenna

Radiation pattern, See Antenna

Radiation resistance, See Antenna

Radio waves at 27 MHz, 305-309

Range, of CB, See Antenna

Reactance, 43, 154, 158-161, 170, 189, 234, 306, 310, 311, 315, 319, 320, 323, 325, 337, 340, 343, 346, 347

RC network, 18, 34, 58, 60, 89, 110, 120, 123, 128, 156, 177-179, 182, 190, 199-201, 212, 225, 268

Reactance modulator, 189, 223

Read-Only-Memory (ROM), 68, 74, 77-79

Receiver, 89-144
 alignment, 140-143, 269-272
 audio amplifier, 128-133
 detector, 106-113, 117-120, 256-259
 dual-conversion, 18, 51, 53, 69, 77, 89, 96, 101, 139, 210, 211, 219, 232, 233, 265
 IF amplifier, 99-102, 256, 265
 image rejection, 18, 89, 100, 101, 233
 mixer, 96-99, 257-259
 oscillator, 49, 51, 53, 55
 RF amplifier stage, 91-96
 selectivity, 17, 18, 49, 51, 100, 103-105, 200, 231-233, 265
 sensitivity, 16-18, 140, 141, 336
 single-conversion, 18, 49, 89, 100, 109, 119, 121, 210, 219, 232, 233, 265
 specifications, 14-18
 squelch circuits, 123-126
 SSB, 209, 211, 256-268
 troubleshooting, 29, 99, 106, 111, 112, 117, 123, 126, 128, 129, 132, 133, 138, 263, 268

Reference Oscillator (Reference Divider), 58-61, 82

Reflector, antenna, 329, 330, 332

Regulation, See Voltage Regulation

Relay T/R switching, 128, 132, 162, 262, 281, 282, 290, 292, 299

Resonance, 42-45, 48, 57, 103, 123, 161, 189, 192, 211, 233-235, 306, 311, 315, 320, 346, 349

Reverse bias, 36, 37, 56, 57, 93, 106, 108, 109, 149, 151, 162, 173, 189, 190, 239, 260, 286, 290

Reverse-polarity diode, 279, 284, 298

RF Ammeter, 6, 168, 175, 309

RF amplifier:
 receiver, 91-95, 281
 transmitter, 149-157, 238-247
 vacuum tube, 153, 168

RF compression, 248

RF feedback, 131, 177, 303, 313, 316

RF filtering, 155, 177, 180, 194, 197, 198, 226, 235, 237, 239, 248, 250, 258, 267, 286, 347, 354-357

RF GAIN control, 19, 92-94

RF Interference (RFI), 146, 278, 355, 356

"RF Meter Reading Incorrect" symptom, 192, 205, 269, 312

RF meter, 5, 6, 26, 81, 192, 269, 312

RF noise suppression, 288, 357

RF overload, See Front-end Overload

RF Probe, 3, 4, 29, 47, 82, 229, 357

RF sampling methods, 81, 184-187

RF Voltmeter, 3, 4, 82, 192, 204

Ripple, 105, 231, 281, 284, 286, 298

Roger Beep Oscillator circuit, 199, 200

ROM programming, 68, 74, 77-79

R-S Flip-Flop, 58, 64

S

SAMS Fotofacts, 2, 81, 266, 279, 288, 290
 drawing errors, 85, 198, 219, 225, 240, 259, 287, 294

Scanning circuit, 71, 126, 136
 Selectivity, See Receiver
 Selective calling (Sel-Call):
 decoder, 127
 encoder, 202
 Self-oscillation, 43, 48, 63, 74, 95,
 102, 104, 105, 111, 131, 146, 152,
 154-157, 181, 241, 278, 299, 301
 Sensitivity, See Receiver
 Series feed, in mixers, 98, 258
 Series-gate Noise Blanker circuit, 108,
 115
 Series-gate squelch circuit, 126
 Series-mode crystal, 43, 45, 48, 104,
 211, 212, 233
 Series-pass voltage regulator, 32, 115,
 136, 241, 245, 246, 281, 283, 294, 301
 Series-pass transistor, 136, 241, 281,
 294, 301, 302
 Shape factor, 231, 232
 Shunt capacitor, 50, 106, 250
 Shunt (Parallel) Feed:
 in antennas, 340, 346, 347, 351
 in mixers, 98, 99, 259
 Shunt type AMC circuit, 182, 183
 Shunt type ANL circuit, 108, 109
 Shunt type Noise Blanker circuit, 114
 Sidebands, 89, 166, 171, 206, 207, 256
 Sideband suppression factor,
 See Carrier Suppression
 Sidetone Oscillator, 200, 201
 Signal Generator, 4, 5, 8, 9, 12, 26, 29,
 47, 82, 99, 105, 117, 139, 235, 268
 Signal injection, 28, 35, 105, 129
 Signal-to-Noise (S/N) ratio, 17, 89, 91,
 94, 117, 120, 124, 140, 200, 207
 Signal rejection, in antenna, 321, 329
 Signal tracing, 3, 5, 28, 105, 123, 126,
 128, 129, 133, 178, 192, 229
 Silicon diode, See Diode
 Single-balanced mixer, 96
 Single-conversion receiver, See Receiver
 Single-ended audio amplifier, 129
 Skip (sky-wave) propagation, 188,
 307-309, 325, 330
 Skirt selectivity, 18, 105, 136, 140,
 231, 234
 Slide mount, 299, 318
 Slope detection, 123
 "S-Meter Reading Incorrect" symptom, 111,
 112, 141, 272
 S-Meter, 9, 26, 106, 111-113, 126, 128,
 139, 141, 184, 192, 266, 268, 272
 Speaker, 26, 29, 41, 89, 105, 119,
 123-126, 128, 129, 131-133, 139, 141,
 281
 Specifications, defined, 13-18, 109,
 140-142
 Spectrum Analyzer, 17, 48, 161, 251-253
 Speech amplifier, 178-182, 223
 Speech clipping, 168, 190
 Speech processing, 168-170, 178, 182,
 189-191, 208, 248
 Spike suppression, 173, 279, 281, 357
 Splatter, 131, 167, 235, 238, 241, 248,
 252
 "Spurious FM or AM" symptom, 58, 69, 189,
 190, 247
 Spurious signals, 17, 55, 103
 "Squelch" symptom, 105, 177, 299, 303, 313
 Squelch, 123-126, 139, 259, 266, 267
 Squelch sensitivity, 18, 111, 123, 141
 Squelch range adjustment, 141, 272
 Squelch troubleshooting, 126, 128
 S/R Meter, 7, 36, 41, 112, 113, 155,
 168, 184, 192, 204, 303, 312, 313

SSB (Single Sideband), 16, 206-276
 AGC circuits, 250, 265-268
 Balanced Modulator, 200, 208, 223-229,
 251, 252
 characteristics, 206-208
 detector, 256-260
 duty cycle, 241, 242
 failure symptoms, 206, 229, 234, 237,
 247, 251, 253-255, 263-265, 268
 filter, 209, 210, 229, 231-235, 265
 linear amplifier, 149, 150, 154, 157,
 159, 172, 177, 209, 235, 238, 248,
 251-254, 316, 340, 352
 power comparison with AM, 208
 power supply, 242-247, 290-298
 reception, 209, 211, 256-268
 selection methods, 229
 testing, 251-255
 transmission, 208-256
 waveforms, 253-255
 Stability, in oscillator, 14, 43, 44, 50,
 51, 55, 56, 191, 207, 211, 214, 226,
 262, 263, 265, 280
 Stability, in power amp, 131, 152, 153,
 155, 156, 162, 175, 239
 Standing waves, 310, 312, 314
 Static, 82, 95, 161, 163, 187, 340
 "Stuck On RX (or TX)" symptom, 298, 299
 Superheterodyne, 89
 Surge protection, 281, 292
 Switching:
 electronic T/R, 93, 162, 280, 281, 297,
 299
 in power supply, 290-297
 relay T/R, 281, 282, 299
 transistor, 31, 32, 123
 SWR (Standing Wave Ratio), 5, 7, 19, 158,
 177, 196, 312-317, 319, 336, 337,
 343, 345
 defined, 196, 312
 determining loss, 313
 effect on Final, 312, 313, 316
 effect on SWR meter, 314-317
 SWR Meter, 5, 19, 26, 41, 195-197, 205,
 312-317, 347
 SWR matching, 7, 321, 334-352
 Synthesizer:
 Crystal, 51-54, 87, 88, 216-218,
 220-222, 256, 281
 offsets, 209-223, 256, 260
 PLL, 53-86, 146, 256
 troubleshooting, 3, 47, 48, 53, 81-85

T

"T" network, 160, 190, 199, 204
 Temperature compensation, 42, 44, 56,
 137, 211, 212, 214, 260, 262, 264
 Test Equipment, 2-13
 Test equipment set-up:
 oscilloscope for modulation, 184-187
 receiver, 139
 PLL synthesizer, 80
 transmitter, 204
 Thermal problem, 28
 Thermistor, 131
 Time constant, 58, 106, 110, 115, 117,
 120, 123, 170, 179, 182, 190, 194, 195,
 200, 248-250, 266, 268, 286
 Tone Control, 138
 Total Harmonic Distortion (THD), 18, 131

Transformer:
 audio, 129, 131, 302
 checking, 41, 133
 coupling, 129, 173, 179, 196, 229, 235
 impedance, 30, 349-351
 modulation, 133, 243, 280, 302
 power, 284, 286, 300, 302
 where to find, 302
 Transient, 128, 131, 286, 292
 Transistor tester, 8
 Transistor:
 amplifier classes, 32, 33, 89, 91, 95
 biasing, See Amplifier
 checking, 35-39
 failure conditions, 36, 41
 identification, 38-40
 in voltage regulation, 136, 245-247,
 281, 283
 NPN type, 8, 31, 32, 38, 89, 183, 247,
 297
 PNP type, 8, 31, 32, 38, 39, 89, 115,
 183, 294, 297, 298
 series-pass, 136, 241, 281, 294, 301,
 302
 substitution, 157
 switching, 31, 32, 123, 178, 184, 229,
 246
 T/R LED circuit, 198
 T/R shift pin, 69
 Transmission line transformer, 350
 Transmitter, 146-205
 accessory circuits, 192-204
 alignment, 204, 205, 269
 Buffer stage, 149, 150
 failure symptoms, 146, 303
 interference, 167, 235, 238, 241, 248,
 252, 278, 347, 348, 353-355
 modulation, 163-184
 oscillator, 49, 51, 53, 55
 power amplifier, See Amplifier
 power regulation circuits, 172-175,
 241-247
 RF feedback, 131, 177, 303, 313, 316
 SSB, 208-256
 waveforms, 164, 167, 169, 188, 253-255
 Trapezoidal modulation measurement,
 See Modulation
 Truth Chart, 66, 68, 135, 297
 Tube:
 biasing, 62, 153, 154, 239, 243
 failure symptoms, 30, 41
 in audio amplifier, 129, 133, 179, 184
 in RF amplifier, 153, 168
 modulator, 174, 175
 oscillator, 45, 47
 power supplies, 286-290
 Tuning:
 antenna, 306, 334-352
 PLL synthesizer, 80, 81
 receiver, 139-142, 269
 transmitter, 204, 205, 269
 TVI (Television Interference), 17, 146,
 158, 187, 198, 278, 347, 348, 353-355
 TV receiver overload, 354
 Two-tone test, 5, 6, 208, 252, 253, 255,
 268

U

UK CB, 66, 68, 78, 79, 117, 123, 124,
 131, 157, 176, 187, 190, 191, 203
 Unbalancing BM for AM/FM, 226-229

Undermodulation, 165, 167, 168, 247
Unwanted sideband suppression, 16, 235
uPD858 PLL IC, 62, 64, 68, 290, 291
uPD2814/uPD2816 PLL IC, 62, 68, 77
uPD2824 PLL IC, 62, 68
UP/DOWN channel control, 71, 127
Upper Sideband (USB), 166, 206-208

V

Varactor, 56, 136-138, 189, 260, 263-265, 301
Variator, 240, 241, 297
VCO (Voltage-Controlled Oscillator), 3, 55-58, 61, 75-79, 82, 85, 99, 146-148, 172, 188-191, 219, 237, 269, 281
Velocity Factor, 314, 315, 328, 336, 337, 343
Vertical angle of radiation, See Antenna
Vertical Polarization, See Antenna
VFO (Variable Frequency Oscillator), 20, 50
Vibrator, 288
Voltage Comparator, 199, 200
Voltage Detector, 107
Voltage Doubler, 106, 110, 114, 192, 194, 267, 286, 300
Voltage regulation, 31, 129, 168, 189, 207, 240, 245, 280-284, 301
Voltmeter, 268, 269, 278, 299, 312, 313
Volume compression, 182
"Volume Control Erratic" symptom, 27
VOM (Volt-Ohm-Milliammeter), 3, 298
VTVM (Vacuum Tube Voltmeter), 3

W

Walkie-Talkie, 14, 42, 49, 157
Wattmeter, 5-8, 19, 155, 158, 204, 205, 208, 225, 251, 252, 268, 269, 312
Waveform:
 in AM detector, 107
 in CW filter, 201
 in Phase Detector, 59
 in SSB testing, 253-255
 in transmitter stages, 163-165, 187
Wave propagation, 307, 308
Wavelength, 306-309, 315, 322, 326, 330
"Weak Modulation" symptom, 154, 167, 168, 175, 179
"Weak Receive" symptom, 16, 48, 81, 91, 105, 107, 111, 112, 117, 123, 268, 303
"Weak Receive Audio" symptom, 106, 126, 128, 131
"Weak Transmit" symptom, 16, 47, 48, 81, 146, 163, 206, 247, 303
Where to find parts, 19-25, 103, 177, 299, 302, 315, 336, 345

Y

Yagi beam antenna, 320, 329, 330, 343

Z

Z-axis, in 'scope measurement, 81
Zener diode:
 clamp, 292
 in ALC circuit, 248, 249
 regulator, 51, 280, 281, 285, 292, 294, 301, 302
 testing, 38

NOTES