

Index

Editor's Note: Except for commonly used phrases and abbreviations, topics are indexed by their noun names. Many topics are also cross-indexed.

The letters "ff" after a page number indicate coverage of the indexed topic on succeeding pages.

A separate Project Index and Author Index follow the main index.

1-Wire:	14.4
4nec2 by Arie Voors:	21.21
555 timer IC:	3.55
8-level vestigial sideband (8-VSB):	8.11
802.11 network:	4.29

A

A index:	19.12
AADE <i>Filter Design and Analysis</i> :	11.26
Abbreviations list:	22.62
Absorption:	19.2
Atmospheric:	19.23
D-layer:	19.13
MF:	19.32
Absorption Glass Mat, battery (AGM):	7.44
Absorption wavemeter:	25.11
AC circuit models:	5.14ff
AC component:	25.1, 25.9
AC coupling:	3.28
Oscilloscope:	25.12
AC ground:	3.29
AC measurements:	25.9
Average:	25.9
Frequency response:	25.10
Oscilloscope:	25.10
Peak, peak-to-peak:	25.9
RMS:	25.9
RMS, true-RMS:	25.9ff
AC power:	7.2ff
AC-DC power conversion:	7.4
Comparison of rectifier circuits:	7.7
Filter, capacitive and inductive:	7.5
Full-wave bridge and center-tap rectifier:	7.6
Half-wave rectifier:	7.5
Ripple:	7.4
AC-line filter:	27.23
Accuracy:	25.2
Active filter:	3.46, 11.18ff
Design tools:	11.22
Adaptive compression:	16.4
Adaptive filter (DSP):	15.17
Adcock antenna:	21.69
Adjacent channel rejection:	25.33
Adjacent-channel power:	8.21
Admittance (Y):	2.47
Advanced Circuits (PCB vendor):	6.16
<i>Advanced Design System (ADS)</i> :	6.10
AF (<i>see</i> Audio Frequency)	
AGC (<i>see</i> Automatic gain control)	
Airmail:	16.26
Alias:	15.7
Aliasing	
Digital oscilloscope:	25.14
Alignment tools:	23.6, 23.24
Alternating current (AC):	2.15
Average values:	2.21
Frequency:	2.16
Fundamental:	2.16
Harmonic:	2.16
Instantaneous values:	2.19
Non-sinusoidal measurements:	2.21
Peak and peak-to-peak values:	2.20
Peak envelope power (PEP):	2.21
Peak power:	2.20
Period:	2.16
Periodic waveform:	2.16
Phase:	2.17
Root-mean-square (RMS):	2.20
Waveform measurements:	2.21
Waveforms:	2.15
Alternator:	2.16
Alternator whine:	27.37
Aluminum	
Alloy types and specifications:	22.41
Tubing sizes:	21.34
AM (<i>see</i> Amplitude modulation)	
Amateur Radio	
American Radio Relay League (ARRL):	1.1
Call sign:	1.6
Contesting:	1.12
Direction finding:	1.17
DXing:	1.13
Getting on the air:	1.10
In the classroom:	1.19
License:	1.5
Log (on-air activity):	1.9
Mobile operating:	1.16
Modes:	1.10
Operating awards:	1.14
Public service:	1.18
QRP (Low power operating):	1.15
QSLs:	1.14
Resources:	1.20
Rules and regulations:	1.2
Satellites:	1.15
Study guides:	1.4
VHF, UHF, microwave:	1.16
Amateur Radio Emergency Service (ARES):	1.18
Amateur television (ATV):	8.18
8-VSB:	8.19
Digital:	8.19
DVB-S:	8.19
NTSC channel:	8.18
Remote sensing:	14.12

AMBE vocoders:	16.28, 16.31, 18.14
American Radio Relay League (ARRL):	1.1, 1.6
Ammeter:	25.2
Ammeter, RF:	25.20, 25.46
Ampere (A):	2.2
Ampere-hours (Ah):	2.11
Amplification:	3.1
Linear:	17.2
Amplifier:	3.1
Bode plot:	3.3
Buffer:	3.40
Class:	3.29, 5.16, 17.2, 17.7ff, 17.31
Classes of operation:	13.26
Common-emitter/base/collector:	3.31, 3.32
Configuration:	3.29
Cutoff (corner) frequency:	3.5
Dynamic range:	3.2
Emitter-follower (EF):	3.31
Feedback:	5.17
Field-effect transistor:	3.36
Frequency response:	3.2, 3.28
Gain:	3.2
Half-power frequency:	3.5
High-frequency model:	3.29
Hybrid:	13.27
Input impedance:	3.33
Large-signal model:	3.29
Limiter:	3.5
Linear:	13.26ff, 17.2
Load line:	3.32
Log:	3.5
Low-frequency model:	3.29
Microphone:	13.10
Nonlinear:	13.26
Operating point:	3.32
Output impedance:	3.35
QSK Controller:	24.43
Quiescent (Q) point:	3.32
Slew rate:	3.2
Small-signal model:	3.29
Stability:	3.4
Summing:	3.4
TR switching:	13.32
Transconductance:	3.6
Transmitter:	13.26ff
Vertical:	25.12
Wideband:	25.29
Amplifier, RF power:	17.1ff
Automatic level control (ALC):	17.25
Broadband transformer:	17.30
Cold tuning:	17.13
Combiners and splitters:	17.33
Common cathode:	17.6
Comparison of solid state vs vacuum tube:	17.3
Component ratings:	17.13ff
Cooling methods:	17.19ff
DC blocking capacitor:	17.17
Filament voltage:	17.17
Grid bias:	17.18
Grounded grid:	17.6
Harmonic rejection:	17.10ff
Impedance matching:	17.31ff
Mobile operation:	29.12
MOSFET design:	17.26ff
Neutralization:	17.21
Parasitic oscillation:	17.23
Parasitic suppressor:	17.24
Pi network:	17.10
Pi-L network:	17.11
Plate voltage:	17.17
Protection and control circuits:	17.37
References:	17.50
RF choke:	17.16
Screen voltage:	17.18
Solid state:	17.31ff
Solid state HF amplifier design:	17.36ff
Solid state, advantages:	17.31
Stabilization:	17.21ff, 17.34ff
Surplus parts:	17.42
Tank circuit:	17.9ff
Tank circuit design methods:	17.10ff
Transmission line transformer:	17.29
Troubleshooting:	26.28ff
Tuning procedure:	17.14
VHF/UHF tank circuit:	17.13
Amplitude modulation (AM):	3.5, 8.3, 10.5ff
Demodulation:	3.5, 10.8
Full-carrier, double-sideband:	13.5
Modulator:	13.4
Transmitter:	13.4
Amplitude-shift keying (ASK):	8.8
Analog (signal):	4.1
Analog Filter Wizard by Analog Devices:	11.22
Analog switches and multiplexers:	3.56
Crosspoint switch:	3.56
Crosstalk:	3.56
Analog systems:	3.27
Analog signal:	3.1
Black box:	3.27
Buffering:	3.29
Cascading stages:	3.28
Interstage loading:	3.28
Network:	3.27
Port:	3.27
Signal processing:	3.1
Terminology:	3.6
Transfer function:	3.27
Analog-digital conversion:	3.48
Accuracy:	3.48
ADC, DAC:	3.48
Aliasing:	3.49, 15.7
Anti-aliasing filter:	15.7
Band-limiting:	3.49
Bandwidth:	3.49
Binary coded decimal (BCD):	3.48
Bipolar and unipolar:	3.48
Choosing a converter:	3.54
Code:	3.48
Conversion rate:	3.49
Decimation:	15.8
Differential nonlinearity:	3.49
Digitization:	3.48
Effective number of bits (ENOB):	3.49
Full-scale (FS) value:	3.48
Full-scale error:	3.49
Hexadecimal:	3.48
Integral nonlinearity (INL):	3.49
Interpolation:	15.9
Jitter:	3.49
Least significant bit (LSB):	3.48
Linearity error:	3.49
Nyquist frequency:	3.49
Nyquist rate:	3.49
Nyquist Sampling Theorem:	3.49
Offset:	3.49
Over- and undersampling:	3.49
Percentage resolution:	3.48
Quantization:	15.9ff
Quantization code:	3.48
Quantization error:	3.49, 15.2, 15.10
Range:	3.48
Reconstruction filter:	15.8
Resolution:	3.48, 15.2
Sample:	3.49
Sample rate:	15.2, 15.6ff
Sampling:	15.6ff
Signal-to-noise and distortion ratio (SINAD):	3.49
Sinc function:	15.8
Spurious-free dynamic range (SFDR):	3.49, 15.2
Step size:	3.48

Total harmonic distortion plus noise (THD+N):	3.49	Pattern ratios (F/B, F/S, F/R):	21.5
Zero-stuffing:	15.9	Polarization:	21.2, 21.55
Analog-digital interfacing:	4.20	Portable operation:	29.18ff
Analog-to-digital converter (ADC):	4.21, 15.2	Quad:	21.39
Analog and digital ground:	3.52	Radiation pattern:	21.4, 21.56
Delta-encoded converters:	3.51	Radiation resistance:	21.2
Dual-slope integrating converter:	3.51	Radio direction finding (RDF):	21.66
Flash (direct-conversion) converter:	3.50	References:	21.75
Input buffering and filtering:	3.52	Remotely-tuned antennas:	21.49, 21.51
Parallel I/O interfaces:	4.20	Repeater operation (home station):	18.7
Sample-and-hold (S/H):	3.51	Safety:	28.13ff
Serial I/O interfaces:	4.20	Safety references:	28.22
Sigma-delta converter:	3.51	Satellite:	21.61
Single-ended and differential inputs:	3.52	Sense:	21.68
Successive-approximation converter (SAC):	3.50	Skeleton slot:	21.43
AND gate:	4.5	Stacking:	21.60
Anderson Powerpole:	29.6	T antenna:	21.28
Angle modulation:	10.9ff	Temperature:	5.31
Analog signals:	8.6	Through-the-glass (mobile):	18.7
Demodulation:	10.12	Trap dipole:	21.14, 21.17
Digital signals:	8.10	Trap vertical:	21.27
Equations:	10.9	Turnstile:	21.61
Quadrature detection:	10.12	Vertical:	21.22
Transmitter:	13.6	VHF/UHF:	21.55ff
Angle, radians and degree-radian conversion:	2.17	VHF/UHF mobile:	18.7
Ansoft Designer SV2:	6.2	Whip:	21.45ff
Antenna		Wire strength:	22.40
Azimuth(al) pattern:	21.4	Yagi, optimized designs:	21.36
Balun:	21.8, 21.38, 21.57	Yagi, Yagi-Uda:	21.32ff, 21.60
Bandwidth:	21.3	Zoning:	28.13
Coaxial dipole:	21.58	Antenna analyzer:	25.25
Conductor diameter:	21.3	Broadcast interference:	26.33
Construction:	21.8	Antenna coupler:	20.14
Construction, Yagi:	21.35ff	Antenna rotator	
Current and voltage distribution:	21.2	Controller:	24.18
Delta loop:	21.41	Antenna switch	
Dipole:	21.6ff	Automatic:	24.14
Dipole, multiband:	20.6	Remote:	24.18, 24.50
Dipole, sloping and vertical:	21.28ff	Antenna systems	
Directivity:	21.1	Troubleshooting:	26.32ff
E- and H-field:	21.2	Antenna tuner (ATU, Antenna coupler, Matchbox,	
Effects of ground:	21.5	Transmatch):	20.14
Elevation angle:	21.5	Adjusting:	20.16
Elevation pattern:	21.4	Balanced and unbalanced load:	20.14
Far (near) field:	21.22	Location in the antenna system:	20.15
Feed point impedance:	21.2	T configuration:	20.10, 20.15
Feeding, ground-plane:	21.25	Unbalanced-to-balanced:	20.14
Folded dipole:	21.12, 21.57	Z-Match:	24.1
Gain:	21.1, 21.4, 21.55	Anti-VOX:	13.29
Glossary:	21.74	Anticyclone:	19.24
Ground losses:	21.22, 21.50	APCO-25:	16.27
Ground systems:	21.23	Apparent power:	2.49
Ground-plane:	21.22ff	Application-specific integrated circuit (ASIC):	3.27, 15.3
Height above ground:	21.3	APRS:	16.23
HF mobile:	21.45	Automatic Identification System (AIS):	16.24
Impedance matching:	21.38, 21.51	Beacon:	16.23
Impedance matching at VHF/UHF:	21.56	D-STAR and DPRS:	16.25
Installation:	28.18	Email:	16.25
Insulators:	21.9	GPS:	16.23
Inverted-L:	21.28	Igate:	16.23
Inverted-V:	21.11	Relay:	16.23
Isotropic:	21.1	Secondary Station ID (SSID):	16.23
Length-to-diameter (l/d) ratio:	21.3	Software:	16.23
Lightning arrestor:	28.9	Tactical call:	16.23
Loading:	21.25, 21.47ff	Tracker:	16.23
Lobes and nulls:	21.4	Winlink:	16.25
Loop:	21.39	Arbitrary waveform generator (AWG):	25.18
Loop and halyard:	28.13	Arcing:	5.10
Magnet (mag) mount:	18.7	Arduino:	4.23
Mast material:	28.18	SDR control accessory:	24.34
Mobile mounting:	21.50, 21.54	Arithmetic logic unit (ALU):	15.4
Modeling:	21.21	Armstrong, Maj. Edwin:	12.7
Multiband:	21.44	ARRL:	1.1
Multiband dipole:	21.13, 21.22	RF Safety Committee:	28.23
National Electrical Code (NEC):	28.8	Section Manager (SM):	27.2

Technical Coordinator (TC):	27.2	Quarter-wave:	20.18
Technical Information Service (TIS):	22.2	Transmitting, ferrite:	20.23
ARRL Lab		Voltage:	20.19
Receiver test procedure:	25.30ff	Wound-coax ferrite choke:	20.23
Transmitter test procedure:	25.22, 25.34ff	Band-pass filter:	11.2
ARRL Radio Designer:	6.5	Band-stop (band-reject) filter:	11.2
ASAPS:	19.22	Bandpass filter:	3.5
ASK (<i>see</i> Amplitude-shift keying)		Transmitter:	13.23
Astrotex (shock mounts):	29.9	Bandwidth	
Atmosphere:	19.6	Antenna:	21.3
Attenuation:	3.1, 11.2	Communication modes:	12.9
Conversion between reflection coefficient, SWR, and		Digital signals:	8.17
return loss:	22.61	Filter:	11.3ff
Free space:	19.2	Occupied:	8.21
Of transmission lines:	20.4	Resonant circuits:	2.57
Attenuation constant (α):	20.7	Barkhausen criteria:	9.3
Attenuator:	3.3, 25.29	BASIC Stamp:	4.23
Pi- and T-network values:	22.44	Battery:	7.32
ATV (<i>see</i> Amateur television)		Absorption Glass Mat (AGM):	7.35, 7.45
Audio		Alkaline:	7.34ff
Intelligibility enhancement:	24.36	Battery Monitoring System (BMS):	29.12
Radio interface:	24.40	Cold-cranking amps (CCA):	7.44
Audio amplifier IC:	3.56	Deep-cycle:	7.35, 7.44
Audio equalizer, intelligibility enhancement:	24.36	Discharging methods:	7.41
Audio equipment RFI:	27.33	Electronic Load Detector (ELD):	29.12
Audio frequency (AF):	2.18	Handling guidelines:	7.43ff
Audio frequency shift keying (AFSK):	8.14	Lead acid:	7.34ff
Aurora:	19.14	Lithium chemistries:	7.34ff
Auroral E:	19.14	Marine:	7.44
Authority having jurisdiction (AHJ):	28.2	NiCd:	7.34ff
AutoCAD:	6.3	NiMH:	7.34ff
Automatic frequency control (AFC):	9.30	Recycling:	7.44
Automatic gain control (AGC):	12.23ff	Remote sensing:	14.10
Circuits:	12.26	Reserve capacity (RC):	7.44
DSP-based:	15.28	Safety:	7.32
Automatic level control (ALC):	13.11, 13.17, 17.2	Starter-lights-ignition (SLI):	7.35, 7.44
Automatic link establishment (ALE):	16.16	Test and monitoring:	7.43
FSK:	16.16	Voltage regulation:	29.17
Link quality analysis (LQA):	16.16	Battery charging:	7.37ff
Scanning:	16.16	Chargers:	7.37
Automatic noise limiter (ANL):	12.26	From USB:	7.38
Automatic Packet Reporting System (APRS)		Full charge detection:	7.39
Position data:	14.8	Lead acid:	7.38
Remote sensing:	14.7	Lithium chemistries:	7.40
Telemetry:	14.7	NiCd:	7.39
Tracking:	14.10	NiMH:	7.40
Automatic repeat request (ARQ)	16.17	Battery Council Institute (BCI):	7.44
Automotive RFI:	27.36, 29.14	Battery Monitoring System (BMS):	29.12
Alternator whine:	27.37	Baud rate:	8.9
Electric vehicle (EV):	27.39	Bazooka (balun):	20.18
Hybrid-electric vehicle (HEV):	27.39	Beacon (radio propagation):	19.22
Ignition noise:	27.38	Transmitter:	13.38
Autoranging:	25.5	Beam antenna:	21.33
Autotransformer:	2.66	Beat frequency:	2.17
Avalanche breakdown:	3.15	Beat frequency oscillator (BFO):	8.5, 12.2
		Bermuda high:	19.26
B		Bessel (constant delay) filter:	11.5
B2 Spice:	6.3	Beta (current gain):	3.17, 3.31
Back-EMF:	2.35	Bias (amplifier):	3.7, 17.2
Background noise:	5.33	Bias point:	3.7
Backscatter:	19.18	Quiescent (Q) point:	3.7
Backwave:	13.16	Bias (device), forward and reverse:	3.9
Balanced modulator:	8.5, 10.30ff, 13.11	Bias-Tee:	24.49
MC1496P:	10.33ff	Bilateral diode switch (<i>see</i> Diac)	
Balun:	20.16, 21.8, 21.38, 21.57	Bilateral networks:	5.26
Bazooka:	20.17	Bill of Materials (BOM):	6.17
Bead:	20.24	Binary	
Broadband:	20.22	Number:	4.2
Choke:	20.17ff	State:	4.3
Coiled coaxial:	20.22	Binary coded decimal (BCD):	3.48, 4.3
Combination ferrite and coiled coax:	20.25	Binary phase-shift keying (BPSK):	8.11, 10.24
Current:	5.23, 20.19ff	Bipolar junction transistor (BJT):	3.10, 3.18
Current (ferrite bead) balun:	20.19	Active (linear) region:	3.18
Quarter-Three-Quarter Wave (Q3Q):	20.19	Breakdown region:	3.19
		Common-emitter/base/collector:	3.19, 3.29

Current gain (β):	3.18	Dissipation factor (DF):	2.29
Cutoff region:	3.18	Effective series resistance (ESR):	2.28
Dynamic emitter resistance, r_e :	3.31	EIA identification and marking:	22.10
Early effect:	3.19	Electrolytic, aluminum and tantalum:	22.7
Ebers-Moll model:	3.31	Electrolytic, reforming:	26.36
Emitter, collector, and base:	3.18	Equivalent (effective) series inductance (ESL):	5.5
High-frequency models:	5.15	Film:	22.6
Hybrid- π model:	3.32, 5.16	High-voltage:	7.29
Operating parameters:	3.19	Labeling:	22.8
Phototransistor:	3.21	Leakage resistance:	2.28
Saturation region:	3.18	Loss angle or tangent (θ):	2.29
Small-signal characteristics:	3.19	Oil-filled:	7.29
Specifications:	22.25	Parasitic inductance:	5.5
Birdies:	25.34	Parasitic inductance model:	5.5
Bit error ratio (BER):	25.38	Poly-chlorinated biphenyls (PCB):	7.30
Bit rate:	16.1	Ratings:	2.29
Audio and video:	16.6	Ratings, RF power amplifier:	17.15
BJT (<i>see</i> Bipolar junction transistor)		RC time constant (τ):	2.25
Bleeder resistor:	2.26, 7.13	Series and parallel capacitors:	2.25
High-voltage supplies:	7.29, 7.30	Standard values:	22.6
Blocking dynamic range (BDR):	25.31	Temperature characteristics:	22.7
Blocking gain compression:	12.20	Temperature coefficient (tempco):	2.29
Bluetooth:	4.26	Types:	2.29
BNC connector:	29.7	Voltage ratings:	22.9
Boat Anchor Manual Archive:	26.14	Capacity (battery):	7.33
Bode plot:	3.3	Capture effect:	8.7, 10.13
Bolometer:	25.20	Capture range:	9.32
Boolean		Carabiner:	28.16
Algebra:	4.4	Carrier squelch:	18.8
Theorems:	4.6	Carrier-current device:	27.5
Boost converter:	7.23	Carson's rule:	8.7
BPL (broadband over power lines):	27.5	Cascode buffer:	3.40
BPSK (<i>see</i> Binary phase-shift keying)		Cathode-ray tube (CRT):	3.27
Branch (circuit):	2.7	Cauer (elliptic function) filter:	11.4
Break-in (CW):	13.29	Cavity resonator oscillator:	9.27
Breakdown, dielectric:	5.10	CDMA (<i>see</i> Code-division multiple access spread spectrum)	
Brick wall response (filter):	11.3	Ceramic microphone:	13.10
Bridge		Channel capacity:	8.17
LCR:	25.18	Characteristic (surge) impedance (Z_0):	20.3
Wheatstone:	25.3	Characteristic curve:	3.6, 17.4ff
Wien:	25.17	Charge-coupled device (CCD):	3.27
Broadband noise:	27.14	Chatter (comparator):	3.45
Buck converter:	7.21	Chebyshev (equiripple) filter response:	11.3
Critical inductance:	7.22	Chinook wind:	19.26
Buck-boost converter:	7.23	Chip rate:	8.15
Buffer (digital), inverting and non-inverting:	4.6	Chip64 and Chip128	
Buffer amplifier		Spread spectrum:	16.12
Cascode buffer:	3.40	Choke balun:	20.17ff
Darlington pair:	3.40	Choke, common-mode:	27.25ff
Emitter-follower (EF):	3.40	Chordal hop:	19.16
Source-follower:	3.40	Circuit:	2.2
Burden voltage:	25.7	Branches and nodes:	2.7
Butterworth (maximally flat) filter response:	11.3	Equivalent circuit:	2.9
Bypass capacitor (RFI):	27.23	Open (short) circuit:	2.2
Bypassing:	5.10	Parallel (series) circuit:	2.2
Paralleling capacitors:	5.11	Circuit breaker:	2.13, 7.2
		Ground fault circuit interrupter (GFCI or GFI):	7.2, 28.5
		Ratings:	2.13
		Circuit simulation	
		Component models and sources:	6.4
		DC operating or bias point:	6.7
		Electromagnetic:	6.13
		Harmonic balance:	6.10, 6.13
		Limitations at RF:	6.12
		Scale factors:	6.3
		Sources, voltage and current:	6.4
		Switchmode power conversion:	7.28
		Time and frequency domain:	6.8
		Time step:	6.6
		Transient:	6.8
		Circular mil:	22.39
		Clamping (<i>see</i> Clipping)	
		Class (amplifier):	13.26, 17.2, 17.7ff, 17.31
		A, B, AB, C, D, E, F:	3.29, 5.16
		Efficiency:	5.17

C

C-rate:	7.33
C4FM:	16.29, 16.31, 18.15
Cable TV, frequencies and leakage:	27.30ff
CadWeld (exothermic welding):	28.8
Calibration (sensors):	14.4
Call sign:	1.6
Capacitance (C):	2.22
Capacitor:	2.22
AC current and voltage:	2.27
AC-rated:	27.24
Axial and radial leads:	2.29, 5.5, 22.6
Ceramic, disc and monolithic:	22.6
Charging and discharging:	2.26
Color codes, obsolete:	22.9
DC blocking:	17.17
Dielectric constant:	2.24

Clipping:	3.5	Voltage:	3.44
Audio, speech:	13.10	Compensation	
Clock frequency and period:	4.8	Frequency:	3.42
CLOVER:	16.20	Oscilloscope probe:	25.15
Coder efficiency:	16.20	Complex frequency:	3.3
Modulation:	16.20	Complex loss coefficient (η):	20.7
Phase-shift modulation (PSM):	16.20	Compression	
CMOS:	3.13	Audio, speech:	13.11
Families:	4.17	Receiver dynamic range:	12.20
Integrated circuit (IC):	4.17	Compression (data):	16.4, 16.4ff
Interface to TTL:	4.19	Compression (signal):	3.5
Coaxial cable (coax):	20.1	Computer-aided design (CAD) (<i>see</i> Circuit simulation)	
Center insulator:	20.1	Conductance (G):	2.3
Dielectric:	20.2	Leakage:	5.3
Hardline:	20.1	Series and parallel:	2.8
Jacket:	20.1, 20.6	Siemens (S):	2.3
Shield:	20.1	Conducted emissions:	27.6
Types of:	20.6	Conduction current:	5.5
Coaxial detector:	25.29	Conductor:	2.1
Code-division multiple access spread spectrum (CDMA):	8.16	Connector:	29.6ff
Codec:	16.4	Audio:	29.6
CODEC2 vocoder by VK5DGR:	16.16, 18.15	BNC:	22.47, 22.49
Coded orthogonal frequency-division multiplexing (COFDM): ..	8.12	Coaxial, types:	22.50
Coded squelch (repeater):	18.8	Computer, pinouts:	22.44
COFDM (<i>see</i> Coded orthogonal frequency-division multiplexing)		Crimp:	29.6
Cohn ladder crystal filter:	11.25	Data:	29.8
Coil (<i>see</i> Inductor)		F:	22.52
Cold Cranking Amps:	7.33	Identification guide:	22.53
Color code		N:	22.51
AC wiring:	28.4	Powerpole, Anderson:	29.6
Capacitor, obsolete:	22.9	RF:	29.7
Diode:	22.16	RJ:	29.8
Inductor:	22.11	Troubleshooting:	26.7
Resistor:	22.3	UHF:	22.46
Transformer:	22.15	Weatherproofing:	28.10
Colpitts oscillator:	9.9	Constellation diagram:	8.11, 15.24
Combinational logic:	4.4ff	Construction techniques	
Combiner, power:	20.21	Circuit layout:	23.21ff
Common reference potential:	28.7	Common standard parts:	23.15
Common-base (CB) amplifier:	3.31, 3.35	Component mounting:	23.16
Current gain:	3.35	Crimping tools:	23.6
Input impedance:	3.36	Drill sizes:	23.5
Output impedance:	3.36	Drilling:	23.30
Common-collector (CC) amplifier:	3.31	Electrostatic discharge (ESD):	23.14
Input impedance:	3.35	Enclosure fabrication:	23.30
Output impedance:	3.35	Ground-plane (dead-bug, ugly):	23.16
Power gain:	3.35	High-voltage:	23.25
Common-drain (CD) amplifier:	3.38	Manhattan style:	23.18
Output impedance:	3.38	Mechanical fabrication:	23.29
Common-emitter (CE) amplifier:	3.31	Metalworking:	23.29
AC performance:	3.35	Microwave:	23.27
Fixed-bias:	3.33	Nibbling tool:	23.6
Frequency response:	3.35	Painting:	23.30
Input impedance:	3.34, 3.35	Panel layout:	23.33
Output impedance:	3.34	PCB fabrication services:	23.20
Power gain:	3.35	Perforated board:	23.18
Self-bias:	3.33	Point-to-point:	23.16
Voltage gain:	3.35	Printed-circuit board (PCB):	23.20ff
Common-gate (CG) amplifier:	3.39	Recommended tools:	23.4
Input impedance:	3.40	Socket or chassis punch:	23.6
Output impedance:	3.40	Soldering:	23.7ff
Voltage gain:	3.39	Solderless breadboard or prototype board:	23.18
Common-mode:	27.9, 27.22	Surface-mount technology (SMT):	23.10
Current:	20.17	Terminal and wire:	23.18
Common-mode rejection ratio (CMRR):	3.42	Tools:	23.3ff
Common-source (CS) amplifier:	3.37	Winding coils:	23.25
AC performance:	3.39	Wire-wrap:	23.18
Input impedance:	3.37	Wired traces (lazy PC board):	23.18
Output impedance:	3.37	Wiring:	23.25
Self-bias:	3.39	Consumer Electronics Association (CEA):	27.17
Source bypass:	3.39	Contesting (radiosport):	1.12
Source degeneration:	3.38	Continuous conduction mode (CCM):	7.22
Voltage gain:	3.37	Continuous tone-coded squelch system (CTCSS):	18.6ff
Comparator		Tone frequencies:	18.8
Hysteresis:	3.45	Continuous wave:	9.2

Control interface		D-RATS:	16.29
Audio:	24.40	D-STAR:	16.27, 16.29, 18.12ff
Serial, RS-232:	24.25	Backbone:	16.28
Transceiver:	24.22	Call sign routing:	16.27
USB:	24.26	<i>d*Chat</i> :	16.29
Control wiring, low-voltage:	28.6	D-RATS:	16.29
Conventional current:	2.2	D-STAR TV:	16.29
Conversion		Digital data (DD):	16.28
Attenuation, SWR, return loss:	22.61	Digital voice (DV):	16.28
Degrees and radians:	2.17	<i>Dplus</i> :	16.29, 18.13
Power and voltage:	22.60	DPRS:	16.29
Conversion loss:	10.21	DV Dongle:	16.29
Convolution:	15.12	Ethernet bridge:	16.28
Cooperative agreement, utilities:	27.22	Gateway:	16.28
Coordination (repeater):	18.8	Hidden transmitter:	16.28
Corona discharge:	19.31, 27.21	JARL:	16.27
Coronal hole:	19.12	Network overview:	18.11
Coronal mass ejection (CME):	19.12	References:	18.14
Coulomb (C):	2.2	Repeater hardware:	18.13
Counter		Station ID:	18.12
Flip-flops:	4.11	Station routing:	18.12
Frequency:	25.10	Texas Interconnect Team:	16.28
Coupling (inductive):	2.37	Trust server:	16.27
Courtesy tone:	18.4	D-type flip-flop:	4.10
Crimp connector:	29.6	Damping:	9.2
Critical frequency:	19.8	Darlington pair:	3.40, 7.16
Cross-reference, semiconductor:	3.8, 26.10	Pass transistor:	7.16
Crossband repeater:	14.11	Data converter:	15.2
Crosspoint switch:	3.56	Data logger:	25.5
Crosstalk:	3.56	Data sheet:	3.7
Crowbar overvoltage protection (OVP):	7.20	dBd:	21.1
CRT (oscilloscope):	25.12	dB _i :	21.1
Crystal (lattice) filter:	11.24	dBm:	25.20
Superheterodyne receiver:	12.11	DC channel resistance, r_{DS} :	3.19
Crystal ladder filters:	11.25, 11.37	DC component:	25.1, 25.9
Transmitter:	13.13	DC coupling:	3.28
Crystal, quartz		Oscilloscope:	25.12
AT-cut:	11.23	DCS (<i>see</i> Digital coded squelch)	
Characterization:	11.26	Dead reckoning:	14.7
Equivalent (effective) series resistance (ESR):	11.23	Decimation:	15.8
Equivalent circuit:	9.21, 11.23	Decoupling:	5.11
Fundamental:	11.23	Deep-cycle battery:	7.44
Holders:	22.38	Delta loop antenna:	21.41
Measuring parameters:	11.28	Delta match:	21.56
Oscillator:	9.19ff	Demodulator:	10.1ff
CTCSS (<i>see</i> Continuous tone-coded squelch system)		I/Q:	8.12, 15.22ff
CubeSats:	14.1	DeMorgan's Theorem:	4.7
Current		Depletion region:	3.9
Conventional:	25.2	Design cycle:	6.2
Electronic:	25.2	Detection:	10.8
Current (I):	2.1	Detector	
Ampere (A):	2.2	Amplitude modulation (AM), DSP-based:	15.29
Conventional current:	2.2	Diode:	25.20
Current source:	2.9	Quadrature:	10.12
Electronic current:	2.2	Thermocouple:	25.20
Current balun:	5.23	Deviation (frequency):	8.6, 10.9
Current divider:	2.7	Measurement:	25.37
Current gain (β):	3.18	Deviation ratio:	8.6
Current inrush:	7.11	Diac:	3.10
Current shunt:	25.8	Diamagnetic:	2.32
Current transfer ratio (CTR):	3.23	Dielectric breakdown and arcing (strength):	5.10
Cutoff (corner) frequency:	3.5, 11.2	Dielectric constant:	2.24
Cutoff (semiconductor):	3.11	Transmission line:	20.2, 20.8
CW		Dielectric resonator oscillator:	9.28
Backwave:	13.16	Difference amplifier:	3.44
Keying waveform:	13.2, 13.15	Differential amplifier:	3.44
Modulation:	10.6	Differential phase-shift keying (DPSK):	8.10
Transmitter:	13.15	Differential quadrature phase-shift keying (DQPSK):	8.12
Waveshaping:	8.8	Differential-mode (signal, current):	20.19, 27.9, 27.22
		Digipeater:	16.24
		Digital (signal):	3.1, 4.1, 15.6
		Digital audio	
		Audio formats:	16.3
		Bit depth:	16.3
		Bit rate:	16.3
		D-RATS:	16.29
		D-STAR:	16.27, 16.29, 18.12ff
		Backbone:	16.28
		Call sign routing:	16.27
		<i>d*Chat</i> :	16.29
		D-RATS:	16.29
		D-STAR TV:	16.29
		Digital data (DD):	16.28
		Digital voice (DV):	16.28
		<i>Dplus</i> :	16.29, 18.13
		DPRS:	16.29
		DV Dongle:	16.29
		Ethernet bridge:	16.28
		Gateway:	16.28
		Hidden transmitter:	16.28
		JARL:	16.27
		Network overview:	18.11
		References:	18.14
		Repeater hardware:	18.13
		Station ID:	18.12
		Station routing:	18.12
		Texas Interconnect Team:	16.28
		Trust server:	16.27
		D-type flip-flop:	4.10
		Damping:	9.2
		Darlington pair:	3.40, 7.16
		Pass transistor:	7.16
		Data converter:	15.2
		Data logger:	25.5
		Data sheet:	3.7
		dBd:	21.1

Codec:	16.4	Infinite impulse response (IIR):	15.16ff
MIDI:	16.3	Microprocessors:	15.4
MP3:	16.4	Modulation:	15.21ff
Digital coded squelch (DCS):	18.8	Modulator and demodulator:	10.14, 15.29
Digital data (mode):	16.1	References:	15.31
Automatic repeat request (ARQ):	16.2	Sine wave generation:	15.17ff
Baud:	16.1	Speech processing:	15.30
Baudot code:	16.2	SSB modulator and demodulator:	15.22ff
Bit, bit rate (bps):	16.1	Tone decoder:	15.19
Bridge:	16.23	Digital TV modulation:	8.11
Checksum:	16.2	Digital video:	16.3
Code pages:	16.3	Bit rate:	16.4
Control characters:	16.3	Codec:	16.6
Cyclical redundancy check (CRC):	16.2	Digital voice, HF:	16.15
Data rate:	16.1	AOR:	16.15
Dibit:	16.9	<i>Dream</i> :	16.15
Emission designator:	16.1	<i>FreeDV</i> :	16.15
Encryption:	16.6	<i>WinDRM</i> by HB9TLK:	16.15
Error detection and correction:	16.2	Digital-analog converter:	4.21
Error-correcting code (ECC):	16.2	Digital-to-analog converter (DAC):	15.2
Forward error correction (FEC):	16.2	Binary weighting:	3.53
FSK:	16.6	Current output DAC:	3.53
Gray code:	16.10	Monotonicity:	3.53
Gross and net bit rate:	16.1	Parallel I/O interfaces:	4.20
Hybrid ARQ:	16.2	R-2R ladder DAC:	3.53
Networking modes:	16.17	Serial I/O interfaces:	4.20
Parity:	16.2	Settling time:	3.53
Sound card:	16.5	Summing:	3.53
Symbol, symbol rate:	16.1	Diode:	3.14, 22.15
Table of modes:	16.30	AC circuit model:	5.14
Throughput (bps):	16.2	Anode:	3.14
Unicode:	16.3	At high frequencies:	5.14
Varicode:	16.2, 16.9	Cathode:	3.14
Viterbi algorithm, coding:	16.9	Color code:	22.16
Digital downconverter (IC):	15.27	Dynamic resistance:	5.14
Digital image		Fast-recovery:	3.15, 7.10
Color depth:	16.3	Forward voltage:	3.14, 3.15
High, true color:	16.3	Free-wheeling:	7.5, 7.22
JPEG:	16.4	Package dimensions:	22.17
Palette:	16.3	Peak Inverse Voltage (PIV, PRV):	3.15
Pixel:	16.3	Photodiode:	3.21
Raster:	16.3	PIN:	3.15
Vector:	16.3	Point-contact:	3.15
Digital logic		Ratings:	3.14
3.3 V - 5 V interface:	4.19	Schottky:	3.15, 7.10
Bipolar families:	4.14	Specifications:	22.16
Combinational:	4.4ff	Switching time:	5.14
Comparing families of:	4.13	Transient voltage suppressor (TVS):	3.16
Families:	22.31	Vacuum tube:	17.4
Gates:	4.5	Varactor:	3.16
Positive and negative:	4.7	Zener:	3.16
Programmable devices:	4.22	Diode detector:	25.20
Sequential:	4.8ff	Diode mixer:	10.18ff
Transistor-transistor logic (TTL):	4.14	Dip (grid dip) meter:	25.11, 26.3
Digital Mobile Radio (DMR):	16.31, 18.14	Diplexer:	10.22ff
Digital modulation:	8.8	<i>Diplexer Designer</i> by W4ENE:	11.42
Bit error ratio (BER):	25.38	Dipole:	21.6ff
Channel capacity:	8.17	Coaxial:	21.58
Constellation diagram:	8.11	Fan:	21.13
Packet error ratio (PER):	25.38	Folded:	21.12, 21.57
Test procedures:	25.38	Inverted-V:	21.11
Digital Radio Mondiale (DRM):	16.15	Multiband:	21.13, 21.22
Slow-scan television (SSTV):	8.20	Near Vertical Incidence Skywave (NVIS):	21.14
Digital sensor interfaces:	14.4	Sloping:	21.11, 21.28ff
Digital signal processing (DSP):	15.1ff	Trap:	21.14, 21.17
Adaptive filter:	15.17	Vertical:	21.28ff
Analytic signals:	15.21ff	Direct conversion receiver:	12.12
Automatic gain control (AGC):	15.28	Direct current (dc):	2.15
Embedded systems:	15.6	Direct digital synthesis (DDS):	9.30, 15.17, 15.28
Filters:	12.12, 15.11ff	Sine-wave generator:	25.18
Finite impulse response (FIR) filter:	15.11ff	Direct FM:	10.11
Glossary:	15.32	Direct sampling:	12.2
Hilbert transformer:	15.23	Direct sequence spread spectrum (DSSS):	8.16
I/Q demodulator:	15.22ff	Direction finding:	1.17
I/Q modulator:	15.22ff	Directional coupler:	25.29

Directional wattmeter:	25.20
Directional wattmeter (<i>see also</i> Reflected power meter)	
Discharge (battery):	7.41
Discontinuous conduction mode (DCM):	7.22
Displacement current:	5.5
Dissipation (power):	2.11
Distributed elements:	5.1
Dithering:	15.10
DMM (digital multimeter):	25.4
Autoranging:	25.5
DominoEX:	16.10
Doppler shift:	21.73, 25.12
Mobile communication:	19.27
Double sideband (DSB):	8.4, 10.7
Double-balanced mixer:	10.20ff
Doubler (frequency):	13.7
<i>Dplus</i> :	16.29
<i>DPRS</i> :	16.29
DPSK (<i>see</i> Differential phase-shift keying)	
DQPSK (<i>see</i> Differential quadrature phase-shift keying)	
<i>Dream</i> :	16.15
Drift velocity:	3.12
Driver array IC:	3.54
DSP (<i>see</i> Digital signal processing)	
DSP filter:	11.18
DTMF (<i>see</i> Dual-tone multi-frequency)	
DTV, HDTV (<i>see</i> Digital television)	
Dual-tone multi-frequency (DTMF)	
Tone frequencies:	18.8
Ducting:	19.25ff
Dummy load:	25.28, 26.3
Duplexer:	18.4
Adjustment using spectrum analyzer:	25.24
DVB-S:	8.19
DVD (Digital Video Disk) player RFI:	27.32
DXing:	1.13
Dynamic microphone:	13.10
Dynamic range:	3.2, 12.1
Blocking (BDR):	12.20
Compression (CFDR):	12.20
Intermodulation distortion (IMD):	10.14, 10.16, 25.32
Receiver:	12.19
Spectrum analyzer:	25.22
Spurious-free (SFDR):	12.21
Test procedures, receiver:	10.16
Dynamic resistance:	2.58, 5.14

E

E layer propagation (E skip):	19.13ff
E-field:	21.2
<i>EAGLE</i> (CAD software):	6.2
Earth-Moon-Earth (EME) communication	
Propagation:	19.30
Ebers-Moll transistor model:	5.15
EchoLink:	18.10
Eddy current:	2.39, 2.65
Education	
Amateur Radio in the classroom:	1.19
Effective sunspot number (SSNe):	19.21
Efficiency (Eff, η):	2.12
EHF (frequency range classification):	2.19
EIA-RS-232:	4.28
Electret microphone:	13.10
Electric charge:	2.1
Coulombs (C):	2.2
Electric fence RFI:	27.15
Electric field	
Electromagnetic wave:	19.1
Electrostatic field:	2.22
RF exposure:	28.26
Electric vehicle (EV) RFI:	27.39
Electrical length (L_e , transmission line):	20.7
Electroluminescence:	3.23

Electromagnetic	
Radiation:	19.1
Spectrum:	19.1
Wave:	19.1
Electromagnetic compatibility (EMC):	27.1
Electromagnetic interference (EMI):	27.1
Electromotive force (EMF):	2.1
Voltage (V, E):	2.1
Electron:	2.1
Free electron:	2.1, 3.8
Mobility:	3.12
Electronic current:	2.2
Electronic design automation (EDA) (<i>see</i> Circuit simulation)	
Electronic Load Detector (ELD):	29.12
Electrostatic discharge (ESD):	3.20
Prevention:	23.14
Elliptic-function filter:	11.4
Elmer:	1.6
<i>Elsie</i> by W4ENE:	11.9
Embedded system (DSP):	15.6
EME (Earth-Moon-Earth) communication:	1.16
Emergency communication:	1.18
Using repeaters:	18.3
Emission designators:	8.1
Table, ITU Radio Regulations:	8.2
Emitter-follower (<i>see</i> Common-collector amplifier)	
Encryption:	16.6
Energy and work:	2.2, 2.11
Ampere-hours (Ah):	2.11
Energy density:	2.11
Horsepower (hp):	2.11
Joule (J):	2.2
Potential energy:	2.22
Watt (W):	2.11
Watt-hour (Wh):	2.11
Envelope detection:	10.8
Equator, geomagnetic:	19.19
Equipment	
Arranging a station:	29.3
Interconnection:	29.5
Mobile mount:	29.9
Equivalent (effective) series inductance (ESL):	5.5
Equivalent (effective) series resistance (ESR)	
Capacitor:	2.28
Quartz crystal:	11.23
Error vector magnitude:	8.22
Error, measurement:	25.2
Ethernet:	4.25, 4.29
Bridge:	29.24
RFI:	27.14
European Telecommunications Standards Institute	
(ETSI):	16.31, 18.15
Excess noise ratio (ENR):	25.27
Excess temperature:	5.30
<i>ExpressPCB</i> (PCB vendor):	6.16, 17.36, 17.49
Eye diagram:	8.22
<i>EZNEC</i> by W7EL:	21.21

F

F layer propagation:	19.16ff
Facsimile (Fax):	8.19, 16.13
Formats:	16.13
Index of cooperation:	16.13
Fading	
Digital signals:	19.28
Ionospheric:	19.9
Tropospheric:	19.27
FAI:	19.14
Fair-Rite Products Corp:	5.19
Fan-out:	4.14
Farad (F):	2.23
Faraday rotation:	19.30
Fast Fourier Transform (FFT):	8.14, 15.18, 16.10, 25.25
Fast-scan television (FSTV) (<i>see</i> Amateur television)	

FCC		
Basis and Purpose:	1.2	
Citation:	27.22	
Field Inspector:	27.22	
Interference Handbook:	27.32	
Notice of Apparent Liability (NAL):	27.22	
RF Interference, cooperation with ARRL:	27.10	
RFI:	27.2ff	
FCC Part 15:	27.4	
Absolute emission limits:	27.7	
Certification:	27.9	
Declaration of conformity:	27.9	
Notification:	27.9	
Operator requirements:	27.11	
RFI rules and definitions:	27.8	
FCC Part 18:	27.4	
FCC Part 2 definitions:	27.6	
FCC Part 97:	1.2, 27.2ff	
Spurious emission limits:	27.4	
Feed line (<i>see</i> Transmission line)		
Feed line radiation:	27.24	
Feed point impedance:	20.7, 21.1	
Feed-through termination:	25.29	
Feedback:	3.4	
Oscillator:	9.3	
Feld-Hell:	16.13	
Ferri- and ferromagnetic:	2.32	
Ferrite:	5.19	
Bead:	5.20	
Chokes:	5.23	
Equivalent circuits:	5.19, 5.22	
Permeability:	5.19	
Permeability vs frequency:	5.21	
Resonances of cores:	5.20	
Toroid cores:	22.14	
Type 31 material:	5.23	
Type or mix:	5.19, 22.11	
Use for EMI suppression:	5.23	
Ferrite bead		
Current balun:	20.24	
FET (<i>see</i> Field-effect transistor)		
FFT (<i>see</i> Fast Fourier transform)		
Fiber optics:	3.23	
Field		
Electric (electrostatic):	2.22, 19.1	
Magnetic:	2.31, 19.1	
Field Day stub filters:	20.10	
Field programmable gate array (FPGA):	4.20, 4.22, 15.3	
Field-aligned irregularities (FAD):	19.14	
Field-effect transistor (FET):	3.12, 3.18	
Breakdown region:	3.20	
Channel:	3.12	
CMOS, NMOS, PMOS:	3.13	
Common-source/gate/drain:	3.20, 3.37	
Cutoff region:	3.20	
DC channel resistance, r_{DS} :	3.19	
Depletion mode:	3.13	
Enhancement mode:	3.13	
Forward transconductance, g_m :	3.19	
Gate leakage current, I_G :	3.19	
High-frequency circuit model:	5.16	
Junction breakpoint voltage:	3.19	
Junction FET (JFET):	3.12	
Mixer:	10.17ff	
MOSFET:	3.12	
N-channel, P-channel:	3.12	
Ohmic region:	3.20	
On resistance, $r_{DS(ON)}$:	3.12	
Operating parameters:	3.20	
Phototransistor:	3.21	
Pinch-off:	3.12	
Saturation region:	3.20	
Small-signal model:	5.17	
Source, drain, and gate:	3.12	
Specifications:	22.24, 22.28	
Field-strength meter (FSM):	25.38	
Filter:	3.4	
Active:	3.46	
Active filter design tools:	11.22	
Active RC:	11.18, 11.20	
Adaptive (DSP):	15.17	
All-pass:	3.5	
Anti-aliasing:	15.7	
Band-stop (band-reject):	11.2	
Bandpass:	3.5	
Bandpass, transmitting:	13.23	
Bandwidth:	11.3ff	
Basic types and definitions:	11.2ff	
Bessel (constant delay):	11.5	
Brick wall response:	11.3	
Butterworth (maximally flat):	11.3	
Capacitor- and inductor-input:	11.6	
Cauer (elliptic function):	11.4	
Center frequency:	11.6	
Chebyshev (equiripple):	11.3, 11.24	
Crystal:	11.37	
Cutoff frequency:	11.2	
Denormalizing (scaling):	11.15	
Design examples:	11.11ff	
Digital:	15.11ff	
Digital commutating:	10.28	
Digital signals:	8.17	
Effect of component Q:	11.9	
Effect of ripple:	11.10	
Family comparison:	11.5	
Family selection:	11.15	
Finite impulse response (FIR):	15.11ff	
Group delay:	11.4	
Helical resonator:	11.33ff	
High-, Low-, Bandpass:	11.2	
High-pass:	3.5	
Infinite impulse response (IIR):	15.16ff	
Insertion loss:	11.9	
Intermediate frequency (IF):	12.2	
Ladder:	11.6	
Linear phase response:	11.25	
Low-pass:	3.5	
Lumped-element (LC):	11.5	
Magnitude response:	11.2	
Mesh capacitor-coupled:	11.9	
Mid-band response:	3.5	
Multiple-feedback:	11.20	
Nodal-capacitor- and -inductor-coupled:	11.8	
Normalized design values:	11.11	
Normalized value tables:	11.12	
Notch:	11.2	
Order:	11.3	
Overshoot:	11.5	
Passband:	3.5, 11.2	
Phase response:	11.2	
Reconstruction:	15.8	
Return loss:	11.11	
RFI:	27.22	
Ringing:	11.5	
Ripple:	11.3	
Ripple bandwidth:	11.3	
Ripple-VSWR-Return Loss table:	11.10	
Roll-off:	3.5, 11.3	
Sallen-Key:	11.20	
Scaling, frequency and impedance:	11.15	
Stop band:	3.5, 11.2	
Stop band depth and frequency:	11.4	
Switched-capacitor (SCAF):	11.18ff	
Topology:	11.7	
Transformation, high-pass to band-stop:	11.7	
Transformation, low-pass to band-pass:	11.6	
Transition region:	11.2	
Ultimate attenuation:	11.2	
Use at VHF and UHF:	11.36	

Filter, crystal:	11.23ff	Frequency synthesizer	
Cohn minimum-loss (min-loss):	11.25	Automatic frequency control (AFC):	9.30
Dishal crystal-ladder filter:	11.25	Direct analog (DAS) and digital synthesis (DDS):	9.30
Evaluation:	11.28	Fractional-N:	9.41
Group delay:	11.25	Phase noise:	9.43
Half-lattice:	11.24	Phase-locked loops (PLL):	9.30ff
Insertion loss:	11.24	Voltage-controlled oscillator (VCO):	9.43
Monolithic:	11.24	Friis formula:	5.31
Motional parameters:	11.23	FSK441:	16.14
Overtone:	11.23	Bit sequences and messages:	16.14
Parallel-resonator-end-section (PRES):	11.25	Meteor scatter:	16.14
Parameters:	11.24	Ping Jockey:	16.14
Pole-zero separation (PZ):	11.23	Synchronization to WWV:	16.14
Shape factor:	11.24	FSTV (<i>see</i> Amateur television)	
Transmitting:	13.13	FTP:	16.23
Unloaded Q:	11.23	Full-bridge converter:	7.25
Filter, surface acoustic wave (SAW):	11.29	Quasi-square wave:	7.25
Filter, transmission line:	11.29	Full-wave bridge, center-tap rectifier:	7.6
Band-pass:	11.31	Output voltage:	7.6
Emulating LC filters:	11.32	Voltage ratings:	7.6
Hairpin resonator:	11.31	Function generator:	25.17ff
Interdigital:	11.31	Fundamental (signal):	2.16
Microstrip:	11.30	Fundamental diode equation:	3.9
Quarter-wave:	11.31	Fundamental overload:	27.12ff
Stripline:	11.30	Fuse:	2.13, 7.2
<i>FilterPro</i> by Texas Instruments:	11.22	Fuse holders:	2.14
Finite impulse response (FIR) filter:	15.11ff	High-voltage:	7.31
Coefficient:	15.14	Ratings:	2.13
Tap:	15.12	G	
Window function:	15.13	G-TOR:	16.20
Window function equations:	15.15	Golay FEC:	16.20
Fire extinguisher:	29.5	Huffman A and B coding:	16.20
FireWire (IEEE-1394):	4.29	GaAs FET:	3.21
Flat topping:	17.2	Gain	
<i>FLDIGI</i> by W1HKJ:	16.5	Amplifier:	3.2, 3.6
Flip-flop (digital):	4.9ff	Antenna:	21.1, 21.55
Flyback converter:	7.23	Noise:	5.31
Flywheel effect:	17.9	Voltage, current, and power:	3.2
Foldback current limiting:	7.18	Gain-bandwidth product (F_T , GBW):	3.28, 3.42, 5.15
Forecast (propagation):	19.20ff	Gallium Arsenide (GaAs):	3.12
Tropospheric ducting:	19.27	Gamma match:	21.38, 21.57
Forward bias:	3.9	Gap noise circuit:	27.15
Forward converter:	7.25	Gate (digital):	4.5
Forward resistance:	3.9	Gate leakage current, I_G :	3.19
Fourier transform:	15.18	Gateway (D-STAR):	18.12
Free space attenuation:	19.2	Gauss (G):	2.32
<i>FreeDV</i> by KDØEAG and VK5DGR:	16.15	Gaussian filter:	8.10
Frequency:	2.16	Gaussian minimum-shift keying (GMSK):	8.10
Calibration:	25.12	<i>GC Prevue</i> (CAD software):	6.24
Complex:	3.3	<i>gEDA</i> (CAD software):	6.2
Counters:	25.10ff	Generator, function:	25.17
Deviation:	8.6, 10.9	Generator, power:	28.5, 29.15ff
Discrimination:	10.11	Safety:	29.17
Marker generators:	25.11	Generator, signal:	25.27
Measurement:	25.11, 25.15	Generator, tracking:	25.24
Multiplier:	10.10	Generic array logic (GAL):	4.20, 4.22, 15.3
Frequency accuracy, receiver:	25.34	Geomagnetic equator:	19.19
Frequency coordination, repeater:	18.9	Geomagnetic storm:	19.12
Frequency counter:	25.10	<i>Gerbv</i> :	6.24
Use for troubleshooting:	26.6	Germanium (device):	3.9
Frequency Division Multiple Access (FDMA):	16.31, 18.14	Gilbert (Gb):	2.32
Frequency domain:	25.21	Gilbert cell mixer:	10.5, 10.30ff, 10.33ff
Frequency hopping spread spectrum (FHSS):	8.15	Gin-pole:	28.16
Frequency modulation (FM):	8.6, 10.9	Global Positioning System (GPS):	25.12
Equipment, FM voice:	18.6	Glossary	
Receiver:	12.28ff	AC theory and reactance:	2.22
Transmitter:	13.7	Amateur Radio, general terms:	1.21
Frequency multiplier:	13.7, 13.22	Analog electronic terms:	3.57
Frequency response:	3.2, 3.28	Antenna:	21.74
AC measurement:	25.10	DC and basic electricity:	2.2
Measurement with noise source:	25.28	Digital electronics:	4.30
Frequency shift keying (FSK):	8.10, 16.6	Digital modes:	16.31
Frequency stability, receiver:	25.34	Digital signal processing (DSP):	15.32
Frequency standard stations:	25.12	Filters:	11.45

FM and Repeater:	18.15
Modulation:	8.23
Oscillators and Synthesizers:	9.47
Power sources:	7.45
Propagation:	19.31
Radio frequency interference (RFI):	27.42
Remote stations:	29.27
RF techniques:	5.36
Software defined radio (SDR):	15.32
Test equipment and measurements:	25.58
Transmission lines:	20.28
GMSK (<i>see</i> Gaussian minimum-shift keying)	
GPIO:	25.7, 25.17, 25.27
GPS:	14.7ff
Sentences (data):	14.7
Gray (grey) line propagation:	19.17
Gray code:	16.10, 16.11
Grid (vacuum tube):	17.5
Bias:	17.18
Control:	17.5
Screen:	17.5
Suppressor:	17.5
Grid-dip meter (GDO):	25.11
Measuring L and C:	25.18
Ground:	29.2
AC (signal) ground:	3.29
Bonding:	28.6, 28.10
Coax shields:	28.9
Cold water pipe:	28.7
Common reference potential:	28.7
Concrete encased grounding electrode (CEGR):	28.7
Conductors:	28.8, 28.10
Dissimilar metals:	28.10
Earth:	28.7
Exothermic welding (CadWeld):	28.8
Galvanizing:	28.10
Lightning dissipation:	28.7
Methods of grounding:	28.7
Radio frequency interference (RFI):	27.13
RF ground:	28.6
Safety ground:	27.13, 28.6
Single-point:	28.10
Soldering and brazing:	28.7
Star:	27.13
Ground fault circuit interrupter (GFCI or GFI):	7.2, 28.5
RFI:	27.35
Ground loop:	27.13
Ground rod:	28.7
Ground wave:	19.6
Ground-plane antenna:	21.22ff
Feeding:	21.25
Grounded grid:	17.6
Group delay (filter):	11.4
Guanella transformer:	20.20
Gummel-Poon transistor model:	5.16
Guy wire, lengths to avoid:	22.40

H

H (hybrid) parameters:	5.15, 5.35
H-field:	21.2
Half-bridge converter:	7.25
Half-power frequency:	3.5
Half-wave rectifier:	7.5
Output voltage:	7.5
Voltage ratings:	7.6
Half-wave vertical dipole (HVD):	21.11
<i>Ham Radio Deluxe</i> digital communications software:	16.13
Hamfests:	1.8
Hardware description language (HDL):	15.3
Harmful interference:	27.4, 27.6
Harmonics:	2.16
Measurement with spectrum analyzer:	25.22
RFI:	27.4, 27.12
Hartley oscillator:	9.10

Harvard architecture:	15.4
Heat management:	2.67
Forced-air and water cooling:	2.70
Heat pipe cooling:	2.70
Rectifiers:	2.70
RF heating:	2.70
RF power amplifier:	17.19ff
Thermoelectric cooling:	2.70
Transistor derating:	2.70
Heat sink:	2.68, 7.11
Selection:	2.68
Helical by W4ENE:	11.34
Helical resonator:	11.33ff
Coupling:	11.36
Design nomograph:	11.34
Insertion loss:	11.36
Tuning:	11.35
Hellschreiber:	16.12
Henry (H):	2.34
Hertz (Hz):	2.16
Heterodyne:	12.2
Hexadecimal:	3.48, 4.3
HF (frequency range classification):	2.19
h_{FE} , h_{fe} :	3.18
<i>HFTA</i> (HF Terrain Analysis):	29.21
High-pass filter:	3.5, 11.2
RFI:	27.3, 27.23
High-voltage power supply:	7.29
Bleeder resistor:	7.29, 7.30
Capacitors:	7.29
Construction techniques:	7.30, 23.25
Equalizing resistors:	7.29
Fuses:	7.31
Grounding stick (hook):	7.31, 28.12
Inductors:	7.30
Metering:	7.30
Transformers:	7.30
Hilbert transformer:	15.23
Hipot test:	7.30
Hop rate:	8.15
Horizon (radio):	19.23
Horsepower (hp):	2.11
Hot stick:	27.21
Hot, neutral, ground wiring:	7.2, 28.4
Hot-carrier diode (<i>see</i> Schottky diode)	
HP8640B generator:	25.27
HPIB:	25.7, 25.17
Huffman coding:	16.4
Hybrid combiner:	25.25
Wilkinson:	25.30
Hybrid-electric vehicle (HEV)	
Automotive RFI:	27.39
Hybrid- π transistor model:	3.31, 5.15
Hysteresis (comparator):	3.45
Hysteresis (magnetic):	2.34

I

I-V curves:	3.6
I/Q	
Demodulator:	8.12, 15.22ff
Modulator:	8.12, 15.22ff
I ² C:	14.5
IC (<i>see</i> Integrated circuit)	
<i>ICAP4</i> :	6.15
IEC (International Electrotechnical Commission):	27.24
IEEE-1394 (FireWire):	4.29
IEEE-488:	25.7, 25.17
IF (<i>see</i> Intermediate frequency)	
IF rejection:	25.33
Ignition noise:	27.38
Image	
Frequency:	12.4, 12.9
GIF:	16.3
Image modulation:	8.18

Image rejection:	25.33	Series resistance:	5.6
Image response:	5.32	Slug-tuned:	2.54
IMD (<i>see</i> Intermodulation distortion)		Standard values:	22.11
Immunity, RF:	27.4, 27.9	Swinging choke:	7.14
Impedance (Z):	2.44	Infinite impulse response (IIR) filter:	15.16ff, 15.17
Antenna:	21.2	Insertion loss (filter):	11.9
Calculating from R and X:	2.46	Insertion loss (IL):	5.13
Equivalent series and parallel circuits:	2.47	Instrumentation amplifier:	3.44
Graphical representation:	2.44	Insulated-gate FET (<i>see</i> MOSFET)	
Mobile antenna:	21.50	Insulator:	2.1
Ohm's law for impedances:	2.47	Antenna:	21.9
Phase angle:	2.44	Integrated circuit (IC):	22.18
Polar and rectangular forms:	2.45	Application-specific IC (ASIC):	3.27
Polar-rectangular conversion:	2.45	Bipolar families:	4.14
Power factor:	2.49	CMOS:	4.16
Reactive power (VA):	2.49	Comparing logic families:	4.13
Rectangular form:	2.44	Digital:	4.13ff
Impedance inversion, pi networks:	5.26	Latch-up:	3.27
Impedance matching:	5.24ff	Metal-oxide semiconductor (MOS):	4.16
Antenna to transmission line:	20.11	Mixer:	10.30ff
Antennas:	21.56	NMOS:	4.16
Conjugate matching:	20.10	Parasitic SCR:	3.27
L network:	5.24, 20.10ff	PMOS:	4.16
Network:	20.10	Programmable-gate arrays (PGA):	3.27
Pi network:	5.26, 17.10, 20.10	Transistor-transistor logic (TTL):	4.14
Pi-L network:	17.11	Integrated circuits (Linear):	3.24
Quarter-wave (Q) section:	20.12	Hybrid circuits:	3.24
Resonating the antenna:	20.12	Monolithic:	3.26
Series- and shunt-input circuits:	20.10	Silicon-on-sapphire (SOS):	3.26
Solid state amplifier:	17.31ff	Substrate:	3.26
Switching:	24.11	Intentional emitters:	27.5
T network:	5.26, 20.10ff, 20.15	Inter-IC Communication (I2C) bus:	4.20, 4.21
Transformer:	20.12, 21.57	Inter-symbol interference:	8.10, 8.17, 19.29
Transmission line:	20.10, 20.13	Intercept point (IP):	10.15, 10.16, 25.32
Twelfth-wave transformer:	20.13	Receiver:	12.21
Vertical antenna:	24.9	Interface	
Impedance matching unit (<i>see</i> Antenna Tuner)		Analog-digital:	4.20
Impedance transformer		Between logic families:	4.18
Transmission line:	20.19ff	Bluetooth:	4.26
Incidental emitters:	27.5	Digital to analog I/O:	4.19
Independent sideband (ISB):	10.7	Ethernet:	4.25
Indirect FM:	10.11	High voltage equipment:	29.8
Inductance (L):	2.35	Microcontroller:	4.22
Air core formula:	2.51	Microcontroller I/O:	4.21
Henry (H):	2.34	PC parallel (LPT) port:	4.24
Induced voltage (back-voltage):	2.35	PC serial (COM) port:	4.24
Mutual inductance (M):	2.36	Personal computer:	4.27ff
Straight wires:	2.52	RS-232:	4.25
Inductance index (A_L):	2.54	USB:	4.25
Inductor:	2.31	WiFi:	4.26
AC current and voltage:	2.38	Zigbee:	4.26
Air core:	2.50	Interference (<i>see</i> Electromagnetic interference)	
Air gap:	2.35	Intermediate frequency (IF):	12.2
At radio frequencies:	5.6	Speech clipping:	13.13
Color code:	22.11	Intermodulation distortion (IMD):	8.20, 10.4, 12.20
Coupling:	2.36	Dynamic range:	10.14, 10.16, 12.20
Eddy current:	2.38	Dynamic range test procedures:	10.16
Effects of coupling:	5.7	Identifying:	27.16
Effects of shielded enclosures:	5.7	Measurement:	25.32ff
Encapsulated:	2.50	Products:	12.20
Energizing and de-energizing:	2.38	RFI:	27.4, 27.12ff
Ferrite toroid cores:	22.14	Spectrum analyzer:	25.22
Ferrite toroidal:	2.55	Internal impedance	
High-voltage:	7.30	Voltage and current sources:	2.9
Inductance index (A_L):	2.54	International power standards:	28.4
Iron core:	2.53	Internet Radio Linking Project (IRLP):	18.10
Kick-back:	2.38	Interpolation:	15.9
Laminations:	2.39	Inverse FFT:	8.14
Machine-wound coil specifications:	22.42	Inversion:	19.24
Parasitic capacitance:	5.6	Inverted-L antenna:	21.28
Powdered-iron toroid cores:	2.54, 22.12	Inverted-V antenna:	21.11
Ratings, RF power amplifier:	17.15	Inverter (digital):	4.6
RL time constant (τ):	2.37	Inverters, dc-ac:	7.44
Saturation:	2.35	Sine-wave output:	7.44
Series and parallel:	2.37	Square-wave output:	7.44
		Volt-ampere (VA) product, rating:	7.44

Inverting amplifier:	3.43
Ion:	2.1
<i>IONCAP</i> :	19.22
Ionogram:	19.8
Ionosonde:	19.8
Ionosphere:	19.7ff
Ionospheric	
Fading:	19.9
Forward scatter:	19.2
Refraction:	19.7
IR drop (<i>see</i> Voltage, Voltage drop)	
ISM (Industrial, Scientific, Medical):	27.4
Isolation	
Summing amplifier:	3.4
Isotropic:	21.1
Isotropic path loss:	5.33
ITU emission designators:	8.2

J

J-K flip-flop:	4.10
Johnson, Johnson-Nyquist noise:	5.30
Joules (J):	2.2
JPEG compression:	16.4
JT65:	16.14
Data compression:	16.14
Earth-moon-earth (EME):	16.14
Reed-Solomon code:	16.15
Synchronization:	16.15
JT6M:	16.14
FSK, 44-tone:	16.14
Ping Jockey:	16.14
<i>WSJT</i> by K1JT:	16.14
Junction FET (JFET):	3.12

K

K index:	19.12
<i>kalibrate-rtl</i> :	15.33
Kelvin, Lord (<i>see</i> Thompson, Sir William)	
Key click:	8.7, 10.7, 13.2
Key clicks:	26.18
Keyer, miniature, TiCK-4:	24.31
Keying interface, universal:	24.29
Keying, CW waveform:	10.7, 13.2
<i>Kicad</i> (CAD software):	6.2
Kirchoff's Current Law (KCL):	2.7
Kirchoff's Voltage Law (KVL):	2.7
Kit, transceiver:	13.32
Klystron:	9.29
Knife-edge diffraction:	19.2

L

L network:	5.24, 20.10ff
Ladder (filter):	11.6
Lagging (leading)	
Power factor:	2.49
Large-signal model:	3.29
Laser diode:	3.23
Lasing current:	3.23
Monochromatic light:	3.23
Latch-up:	3.27
Lead acid battery:	7.32ff
Leakage current:	7.29
Leakage flux:	2.64
Leakage path:	5.10
Leakage reactance:	2.65
Leakage resistance	
Capacitor:	2.28
Least significant bit (LSB):	3.48
Level converter:	29.9
LF (frequency range classification):	2.19
Licensing:	1.5

Light-emitting diode (LED):	3.23
Circuit design:	3.23
Electroluminescence:	3.23
Lightning (source of noise):	19.31
Lightning protection	
Cable entrance panel:	28.10
Lightning arrester:	28.9
Suppliers:	28.10
Limiter (amplifier):	3.5, 8.7
Limiting:	3.5
Line loss:	20.4
Line of sight propagation:	19.22
Linear (system):	3.1
Linear amplifier:	13.26ff, 17.2
Liquid-crystal displays (LCD):	3.27
Lithium-ion battery	
Charging:	7.40
Litz wire:	2.51, 5.6
Loading (antenna):	21.25
Lock range:	9.32
Log (logarithmic) amplifier:	3.47
Log (on-air activity):	1.9
Logbook of The World (LoTW):	1.14
Logic analyzer:	25.37
Logic probe:	25.37
Logic-gate oscillator:	9.26
Logical operations:	4.5ff
Long-path propagation:	19.17
Loop antenna:	21.39
Loss	
Filter insertion loss:	5.13
Loss angle or tangent (θ):	2.29
Losses (radiative):	5.10
Lossless and lossy compression:	16.4
Low-pass filter:	3.5, 11.2
DC motors:	27.37
RFI:	27.3, 27.23
Telephone RFI:	27.33
Lowest usable frequency (LUF):	19.9
<i>LTS</i> by Linear Technologies:	6.2, 17.11
LUF:	19.9
Lumped elements:	5.1
Lumped-element (LC) filter:	11.5
LZW compression:	16.4

M

M-factor:	19.9
Macros:	16.5
Magnetic circuit analogies:	2.32
Magnetic field:	2.31
Electromagnetic wave:	19.1
Gauss (G):	2.32
Hysteresis:	2.34
Magnetic field strength (H):	2.32
Magnetic flux:	2.32
Magnetic flux density (ϕ):	2.32
Magnetic flux linkage:	2.34
Magnetomotive force (MMF, $\Im$):	2.32
Mean magnetic path length:	2.32
Oersted (Oe):	2.32
Permeability (μ):	2.32
RF exposure:	28.26
Right-hand rule:	2.32
Saturation:	2.34
Tesla (T):	2.32
Magnetic flux	
Maxwell (Mx):	2.32
Weber (Wb):	2.32
Magnetism:	2.31
Magnetometer:	19.12
Magnetomotive force (MMF, $\Im$):	2.32
Reluctance ($\Re$):	2.33
Magnetosphere:	19.6
Magnetron:	9.29

Magnitude response (filter):	11.2	NE602/SA602/SA612:	10.30ff
Manuals, equipment:	26.14	Nonlinear signal combinations:	12.3
Marine battery:	7.44	References:	10.35
Marine layer:	19.26	Switching:	10.18ff
Marker generator:	25.11	Taylor:	10.28ff
Master-slave flip-flop:	4.10	Transistor:	10.24ff
<i>MATCH</i> by WØIYH:	20.11	Mixing products:	10.4
Matchbox (<i>see</i> Antenna Tuner)		<i>MixW</i> digital communications software:	16.12
Maunder minimum:	19.10	Mobile	
Maxim, Hiram Percy:	1.1	Antenna impedance matching:	21.50
Maximum usable frequency (MUF):	19.8	Antenna mounting:	21.50, 21.54
Prediction:	19.20ff	Antennas (HF):	21.45
Maxwell (Mx):	2.32	Antennas (VHF/UHF):	21.54
Megger:	7.30	Ground losses:	21.50
MESFET:	3.21	Impedance matching:	21.51
Metal-oxide semiconductor (MOS)		Remotely-tuned antennas:	21.49, 21.51
Integrated circuit (IC):	4.16	SSB and CW antennas at VHF/UHF:	21.54
Metal-oxide varistor (MOV)		Mobile operation:	29.9ff
Specifications:	22.37	Air bags:	29.11
Meteor scatter:	19.15	Amplifiers:	29.13
Meteor shower:	19.16	Automotive interference:	29.14
Meter		Cables and wiring:	29.10ff
Digital panel (DPM):	25.8	Mounts, control head:	29.10
Internal resistance:	25.3	Operating techniques:	29.15
Panel:	25.7	RFI:	27.36
Protection diodes:	25.8	Shock mounts:	29.9
Resistance:	25.7	VHF/UHF propagation:	19.27ff
Scales:	25.8	Modem:	16.17
Shunt:	25.5	Modes:	8.1ff
<i>Meter Basic</i> by W4ENE:	17.49	Digital:	16.1ff
Method of moments:	21.21	Typical bandwidths:	12.9
Metric units:	22.59	Modulation:	8.1ff
MF (frequency range classification):	2.19	Accuracy:	8.21
MF propagation:	19.32	Amplitude modulation (AM):	3.5, 8.3, 10.5ff
MFSK (<i>see</i> Multi-level FSK)		Amplitude-shift keying (ASK):	8.8
<i>MICROCAP9</i> :	6.15	Analog:	8.3ff
Microcontroller:	4.23, 4.23ff	Angle:	8.6ff, 10.9ff
CPU size:	4.24	Continuous wave (CW):	8.8, 10.6
Development tools:	4.25	Digital:	8.7
FLASH memory:	4.26	Digital signal processing (DSP):	15.21ff
I/O:	4.21	Double sideband (DSB):	8.4
I/O requirements:	4.24	Frequency modulation (FM):	8.6
Interfacing:	4.22	Image:	8.18
Memory:	4.24	Impairments:	8.20ff
Peripherals:	4.24	Linearity:	10.6
Programming:	4.25	Multi-carrier:	8.13
Resources:	4.26	On-off keying (OOK):	8.8
Selecting:	4.24	Phase modulation (PM):	8.6
Microphone		Products:	3.5
Amplifier:	13.10	Pulse:	8.9
Types of:	13.10	Quadrature:	8.11ff
Microprocessor:	15.4	Single sideband (SSB):	8.5
Microstrip:	11.30	Transmitter:	13.24
Microwave band designations:	25.29	Modulation index	
Microwave construction techniques:	23.27	AM:	8.3
Microwire:	4.20, 4.21, 14.5	FM:	8.6
Military Auxiliary Radio Service (MARS):	1.19	Modulation percentage	
Minimum discernible signal (MDS):	25.22, 25.30	Measurement:	25.37
Minimum-shift keying (MSK):	8.10	Modulator:	10.1ff, 10.35
Mirror scale, meter:	25.7	Balanced:	8.5, 13.11
Mix (ferrite and powdered iron):	2.54	Balanced, MC1496:	10.33ff
Mix (ferrite):	5.19	I/Q:	8.12, 15.22ff
Mix, Tom 1TS:	14.1	Molex connector:	29.6
Mixer:	10.1ff	Monolithic microwave IC (MMIC)	
Diode:	10.18ff	Specifications:	22.22
Diplexer:	10.22	Monopole:	21.22
Double-balanced:	10.20ff	Monte Carlo analysis:	6.1
Dynamic range:	10.14ff	Moonbounce (<i>see</i> EME)	
Equations:	10.3	Morse code:	8.8
FET:	10.17ff	MOSFET:	3.12, 3.20
Gain controlled amplifier:	10.16ff	Depletion mode:	3.21
Gilbert cell:	10.26ff	Electrostatic discharge (ESD):	3.21
Image:	12.4	Enhancement mode:	3.21
Image-rejecting:	12.12	Pass transistor:	7.17
MOSFET:	10.19.29	Power:	3.21

MOSFET, RF Power			Noise:	5.30ff
Data sheet parameters and ratings:	17.28		Atmospheric:	12.17
Gate structures:	17.26		Background:	5.33
LDMOS vs VDMOS:	17.27		Bandwidth:	12.17
RF power amplifier design:	17.26ff		Broadband:	27.14
Thermal design:	17.28		Cosmic:	19.31
Transfer characteristics:	17.30		Effects on receivers:	12.17
Voltage ratings:	17.27		Factor (F) or Figure (NF):	3.28
Moxon rectangle:	21.61		Friis formula:	5.31
MP3 compression:	16.4		From losses:	5.31
MSFK16:	16.9		Gain:	5.31
Convolution code:	16.10		Galactic:	12.17
Fast Fourier Transform (FFT):	16.11		Gap noise:	27.15
Gray code:	16.10		Generator, use in transmission line measurements:	20.9
Hamming distance:	16.11		Ignition:	27.38
Interleaver:	16.10		Image response:	5.32
Modulation:	16.11		Immunity (digital IC):	4.14
Quadbit, nibble:	16.10		Johnson noise:	3.28
MSK (<i>see</i> Minimum-shift keying)			Johnson, Johnson-Nyquist:	5.30
MT63:	16.12		Man-made:	12.17, 19.30
Error-correction:	16.12		Narrowband:	27.14
Latency:	16.12		Noise blanker (NB):	12.27
Navy MARS:	16.12		Noise limiter (ANL, NL):	12.26
Noise immunity:	16.12		Of cascaded amplifiers:	5.31
Tuning error:	16.12		Of preamplifiers:	5.32
Walsh function:	16.12		Phase noise:	12.17
MUF (<i>see</i> Maximum usable frequency)			Power:	5.30, 12.18
Multi-level FSK (MFSK):	8.10		Pulse noise:	12.26
Multi-protocol controller (MPC):	16.17		Signal-to-noise ratio (SNR):	3.28
Multimeter:	25.3		Simulation:	5.17
Input impedance:	25.7		Sun:	5.32
Specifications:	25.5		Temperature:	5.30
Use of:	25.5		Thermal:	12.17
Used and surplus:	25.7		Thermal noise:	3.28
Multimode communications processor (MCP):	16.17		White:	5.30
Multipath propagation:	19.28		Wideband, transmitting:	13.16
Multiplier, frequency:	13.7, 13.22		Noise bandwidth:	25.31
MultiPSK:	16.13		Noise factor (F):	3.28, 5.31
Multivibrator:	4.12		Noise figure (NF):	3.28, 5.31, 12.18, 25.31
Astable (free-running):	4.13		Measuring:	25.27
Bistable:	4.12		Relationship to noise temperature (Table):	22.43
Monostable (one-shot):	4.12		Noise floor:	12.1
Mutual inductance (M):	2.36, 2.62		Noise reduction (NR)	
			DSP:	12.28
			Pulse noise:	12.26
			Noise source:	25.27
			Noise temperature	
			Relationship to noise figure (Table):	22.43
			Nominal value:	2.4, 22.2
			Non-inverting amplifier:	3.43
			Non-linear junction:	27.16
			NOR gate:	4.5
			Northern California DX Foundation (NCDXF):	19.21
			Norton equivalent circuit:	2.10
			Norton's Theorem:	2.10
			Notch filter:	11.2
			NTSC (analog TV):	8.18
			Number systems:	4.2ff
			Binary:	4.2
			Binary coded decimal (BCD):	4.3
			Conversion techniques:	4.3
			Hexadecimal:	4.3
			Numerically controlled oscillator (NCO):	15.17
			NVIS (<i>see</i> Near-vertical incidence skywave)	
			Nyquist	
			Criterion:	8.10, 15.6ff
			Frequency:	3.49, 8.10, 15.6ff
			Rate:	3.49, 15.6ff
			Nyquist filter:	8.17
			Nyquist sampling theorem:	3.49
			O	
			O wave:	19.9
			Occupied bandwidth:	8.21

Oersted (Oe):	2.32	Troubleshooting:	26.24
OFDM (see Orthogonal frequency-division multiplexing)		Twin-T, audio:	25.17
Off-center fed dipole:	21.7	UHF and above:	9.26
Offset quadrature phase-shift keying (OQPSK):	8.12	Variable crystal oscillator (VXO):	9.25
Ohm (Ω):	2.3	VFO construction:	9.15ff
Ohm's law:	2.3	Wien bridge:	25.17
Power formulas:	2.12	YIG-tuned oscillator:	9.28
Ohmmeter:	25.3	Oscillators and Synthesizers	
Oil-filled capacitor:	7.29	Glossary:	9.47
Olivia:	16.12	References:	9.48
MFSK:	16.12	Oscilloscope:	25.12ff
Orthogonal tones:	16.12	AC measurement:	25.10
On-off keying (OOK):	8.8, 13.2	Analog:	25.12
Open-collector output:	3.45	Buying used:	25.17
Open-wire line:	21.7	Digital:	25.14
Operational amplifier (op amp)		Dual-trace:	25.13
Transimpedance:	14.3	Features and specifications:	25.16ff
Operational amplifier (op-amp):	3.42	Probes:	25.15
Active filter:	3.46	Rise time and bandwidth:	25.14
Common-mode rejection ratio (CMRR):	3.42	Use for troubleshooting:	26.4
Comparator:	3.44	Use of:	25.15ff
Compensation (frequency):	3.42	X-Y mode:	25.14
Difference amplifier:	3.44	OSI networking model:	16.17
Differential amplifier:	3.44	Layers:	16.17
Gain:	3.42	Protocol stack:	16.17
Gain-bandwidth product (F_T , GBW):	3.42	Out-of-band emissions:	27.4
Input and output impedance:	3.42	Overmodulation:	10.5
Input bias current:	3.42	Overshoot:	11.5
Input offset voltage:	3.42	Ozonosphere:	19.6
Instrumentation amplifier:	3.44		
Inverting and non-inverting amplifier:	3.43	P	
Log amplifier:	3.47	P25:	16.29
Open-loop gain:	3.42	APCO-25:	16.29
Peak detector:	3.47	Continuous 4-level FM (C4FM):	16.29
Power-supply rejection ratio (PSRR):	3.42	Improved MultiBand Excitation (IMBE):	16.29
Rail-to-rail:	3.42	Tetra:	16.29
Rectifier circuit:	3.46	Packet error ratio (PER):	25.38
Specifications:	22.32	Packet radio (AX.25):	16.23
Summing amplifier:	3.44	APRS:	16.24
Summing junction:	3.43	Cluster:	16.23
Unity-gain buffer:	3.44	Digipeater:	16.24
Use of feedback:	3.43	FTP:	16.24
Virtual ground:	3.43	KISS:	16.24
Voltage-current converter:	3.47	Packet bulletin-board systems (PBBS):	16.23
Voltage-follower circuit:	3.43, 3.44	TCP/IP:	16.24
Optoisolator:	3.23, 4.20	TNC interface:	16.23
Circuit design:	3.23	PACTOR	
Current transfer ratio (CTR):	3.23	Contact flow:	16.18
OR gate:	4.5	Link establishment:	16.18
Order (filter):	11.3	PACTOR-I, -II, -III - IV:	16.18ff
Orthogonal frequency-division multiplexing (OFDM):	8.13	PACTOR-III link establishment:	16.19
Oscillation:	3.4	Speed comparison:	16.18
Oscillator		Panadapter:	25.25
Active device selection:	9.17	Parallel I/O interface:	4.20, 4.27ff
Audio frequency:	25.17ff	Parallel-bridge converter:	7.25
Capacitor selection:	9.15	Paramagnetic:	2.32
Cavity resonator oscillator:	9.28	Parasitic:	5.1
Crystal:	9.19ff	Capacitance (stray):	5.3, 5.5
Crystal circuits:	9.22ff	Capacitance of inductors:	5.6
Crystal test:	11.27	Effect on filter performance:	5.13
Dielectric resonator oscillator:	9.28	Effect on Q:	5.8
Disciplined:	25.12	Effects of parasitic characteristics:	5.3
Feedback loop:	9.3	General component model:	5.3
Inductor selection:	9.17	Inductance:	5.3, 5.17
LC circuits:	9.9ff	Inductance of capacitors:	5.5
Logic-gate oscillator:	9.26	Inductance of resistors:	5.4
Negative resistance:	9.4	Inductance per inch of wire:	5.3
Numerically controlled (NCO):	15.17	Inter-electrode capacitance:	5.6
Phase noise:	9.5ff, 12.17	Leakage conductance:	5.3
RC circuits:	9.11	Oscillation:	17.23, 17.34
Resonator:	9.3	Package capacitance:	5.6
Shielding:	9.19	Parasitic SCR:	3.27
Start-up:	9.4	Radiative losses:	5.10
Temperature compensation:	9.18	Resistance:	5.3
Transmitter:	13.22	Self-resonance:	5.9

Parasitic suppressor:	17.24, 17.32	Loop filter:	9.32, 9.39ff
Parasitics (oscillation):	27.4, 27.12	Measurement and troubleshooting:	9.45
Part 15 devices:	27.4	Modulator:	10.11
Part 18 devices:	27.4	Noise:	9.33
Passband (filter):	11.2	Phase (frequency) detector:	9.35
PC board construction:	23.20ff	Phase detector:	9.31
PC board layout:	6.15ff	Prescaling:	9.38
Annotation, forward and backward:	6.17	Reference oscillator:	9.32, 9.39ff
Annular ring:	6.18	Voltage-controlled oscillator (VCO):	9.32
Auto-placement:	6.20	Phased array:	21.69
Auto-router (autorouting):	6.22	Phasing line:	20.12
Bill of Materials (BOM):	6.17	Phasing method (SSB generation):	8.5, 12.12, 13.6
Board house:	6.17	Phasor diagram:	15.22
Component and solder sides:	6.17	Photoconductivity:	3.21
Component footprint:	6.16	Photoconductor:	3.8, 3.21
Copper fill:	6.23	Photodiode:	3.21
Design Rule Check (DRC):	6.23	Photoelectricity:	3.22
Double- and multi-layer:	6.17	Photoisolator (<i>see</i> Optoisolator)	
Drill file:	6.24	Photoresistor:	3.22
Excellon file:	6.24	Phototransistor:	3.22
Gerber file (RS-274X):	6.23	Optoisolator:	3.23
Net:	6.16	Photovoltaic cell:	3.22
Netlist:	6.17	Conversion efficiency:	3.23
Panelizing:	6.18	Open-circuit, V_{OC} , or terminal, V_T , voltage:	3.22
Photoplotter:	6.24	Photovoltaic potential:	3.22
Plated-through hole:	6.17	Short-circuit current, I_{SC} :	3.23
RF interference:	6.22	Solar panel:	3.23
Routing (traces):	6.20	Pi network:	5.26, 20.10
Silkscreen:	6.18	Impedance inversion:	5.26
Software:	6.15ff	RF power amplifier:	17.10
Solder mask:	6.18	<i>PI-EL Design</i> by W4ENE:	17.10
Surface-mount component:	6.17	Pi-L network	
Symbol library:	6.16	Component selection:	17.11
Through-hole component:	6.17	RF power amplifier:	17.10
Tin plating:	6.18	Table of values:	17.12
Trace current limits:	6.23	PICAXE:	4.23
PC board material, FR4:	6.17	Picket fencing:	19.28
PCB fabrication services:	6.17ff	Piezoelectric effect:	9.19
Peak and peak-to-peak values:	2.20	Pilot carrier:	13.8
Peak detection:	3.5	PIN diode:	3.15
Peak detector:	3.47	Pinch-off:	3.12
Peak envelope power (PEP):	2.21, 25.20	Pinouts:	3.7
Peak inverse voltage (PIV, PRV):	3.15, 7.11	PL-259 connector:	29.7
Peak power:	2.20	Plasma frequency	19.8
Peak surge current, I_{SURGE} :	7.11	Plastic repair and restoration:	26.38
Pedersen ray:	19.16	PN junction:	3.8
Peltier effect:	2.70	Anode:	3.9
Pentode:	17.5	Barrier (threshold) voltage:	3.9
Performance requirements:	3.31, 6.2, 11.11	Cathode:	3.9
Period:	2.16	Depletion region:	3.9
Permeability (μ):	2.32	Forward resistance:	3.9
Ferrite:	5.19	Forward voltage drop:	3.10
Of magnetic materials:	2.33	Fundamental diode equation:	3.9
Phase:	2.17	Junction capacitance:	3.15
Lag and lead:	2.17	Recombination:	3.8
Phase shift:	3.3	Response speed, recovery time:	3.15
Phase angle (impedance):	2.44	Reverse breakdown voltage:	3.15
Phase constant (β):	20.7	Reverse leakage current:	3.9, 3.15
Phase detector:	9.31, 9.35	Reverse-bias saturation current, I_S :	3.10, 3.15
Phase modulation (PM):	8.6, 10.9	PNPN Diode:	3.10
Transmitter:	13.8	Point-contact diode:	3.15
Phase noise:	9.5ff, 12.17	Polar cap absorption (PCA):	19.12
Frequency synthesizer:	9.43	Polarity (phase):	2.18
Measurement:	9.6	Polarity (voltage):	2.1
Reciprocal mixing:	9.7	Polarization	
Transmitted:	9.8	Antenna:	21.2, 21.55
Phase response (filter):	11.2	Circular:	21.56
Phase-locked loops (PLL):	9.30ff	Radio wave:	19.9
Capture range:	9.32	Pole (transfer function):	3.4, 11.20, 11.23
Charge pump:	9.36	Port, electronic:	25.25
Demodulator:	10.13	Portable operation:	29.15ff
Dynamic stability:	9.33	Antennas:	29.18ff
Frequency resolution (step size):	9.33	DC power sources:	29.17
Lock range:	9.32	Power sources:	29.15ff
Loop bandwidth:	9.31, 9.33		

Potentiometer:	2.6	E layer:	19.13ff
Taper (log, audio):	2.6	Emerging theories:	19.19
Powdered-iron core:	22.12	F layer:	19.16ff
Power:	2.11	Forecast:	19.20ff
Horsepower (hp):	2.11	Glossary:	19.31
Joule (J):	2.2	References:	19.33
Station:	29.2	Sky wave:	19.6ff
Watt (W):	2.11	Software:	19.21, 19.22
Watt-hour (Wh):	2.11	Space communication:	19.30ff
Power density		Summary by band:	19.4ff
Spectral:	5.30	Tropospheric:	19.22ff
Power divider:	25.30	VHF/UHF mobile:	19.27ff
Power factor:	2.49	<i>PropLab Pro</i> :	19.22
AC measurement:	25.9	Protocol, digital	
Power filtering		APRS:	16.24
Bleeder resistor:	7.12	Automatic repeat request (ARQ):	16.2, 16.17
Capacitor-input:	7.13	B2F:	16.26
Choke inductor constant (A):	7.14	Broadcast:	16.17
Choke-input:	7.14	CLOVER:	16.20
Swinging choke:	7.14	Connected and connectionless:	16.17
Power strip load rating:	28.2	D-STAR:	16.27
Power supply:	7.1ff	G-TOR:	16.20
Fault symptoms:	26.22	Multicast:	16.17
Use for troubleshooting:	26.5	P25:	16.29
Power supply regulation:	7.12	Packet radio (AX.25):	16.23
Crowbar OVP circuit:	7.20	PACTOR:	16.18ff
Foldback current limiting:	7.18	RMS:	16.26
Linear regulator:	7.16	SMTP:	16.24
Load resistance:	7.12	Stack:	16.17
MOSFET:	7.17	TCP/IP:	16.17, 16.24
Over-voltage protection (OVP):	7.20	TELNET:	16.24, 16.26
Overcurrent protection:	7.17	Terminal node controller (TNC):	16.17
Pass transistor:	7.16	UDP:	16.17
Pass transistor power dissipation:	7.16	Unicast (point to point):	16.17
Remote sensing:	7.16	WINMOR:	16.22
Series and shunt regulator:	7.15	PSK31:	16.8
Three-terminal voltage regulator:	7.18	BPSK, QPSK:	16.9
Voltage regulation:	7.12	Convolution code:	16.9
Zener diode regulator:	7.15	Dibit:	16.9
Power-line noise:	27.15, 27.18ff	Envelope modulation:	16.9
Cooperative agreement:	27.22	Phase-shift modulation:	16.9
Corona discharge:	27.21	PSK63, PSK125:	16.9
Noise-locating equipment:	27.19	Varicode:	16.9
Signature or fingerprint:	27.20	Viterbi algorithm:	16.9
Ultrasonic location:	27.19	<i>PSPICE</i> :	6.14
Utility complaint:	27.18	Public service:	1.18
Powerpole, Anderson:	29.6	Public-address equipment RFI.....	27.34
Powerstat (transformer):	2.66	Pull-up resistor:	3.45
Preamplifier:	12.18	Pulse modulation:	8.9
Dual-band, 2 m and 70 cm:	12.30	Pulse noise reduction:	12.26
Noise:	5.32	Pulse-amplitude modulation (PAM):	8.10
Precipitation static:	19.31	Pulse-position modulation (PPM):	8.10
Precision (value):	2.4	Pulse-width modulation (PWM):	8.10
Precision rectifier circuit:	3.46	Switchmode power conversion:	7.22, 7.26
Precision resistor:	2.4, 22.2	Push-to-talk (PTT):	13.29
Prescaler:	9.38, 25.10		
Preselector:	11.1	Q	
Primary battery:	7.32	Q section:	20.12
Probe		QAM (<i>see</i> Quadrature amplitude modulation)	
Logic:	25.37	QRP (Low power operating):	1.15
Oscilloscope:	25.15	QSL card:	1.14
RF:	25.19	Quad antenna:	21.39
Sniffer:	25.23	QuadNet by W4ENE:	11.21
Voltage:	25.23	Quadrature amplitude modulation (QAM):	8.11ff
Processing gain:	8.14	Quadrature detector:	10.12
Product detector:	8.5	Quadrature phase shift keying (QPSK):	8.12, 10.24
Programmable Array Logic (PAL):	4.20	Quality factor (Q):	2.50
Programmable gate array (PGA):	3.27, 4.22	Amplifier tank circuit:	17.9
Programmable logic device (PLD):	4.19, 4.22, 15.3	Loaded:	2.61
Propagation:	19.1ff	Loaded and unloaded:	5.13
Back- and sidescatter:	19.18	Of components:	2.50
Below AM broadcast:	19.32	Unloaded:	2.55
Chart:	19.19	Quantization:	15.6ff, 15.9ff
D layer:	19.13	Quantization error:	15.2, 15.3.50, 15.10
Delay (digital circuit):	4.4		

R

Radians:	2.17, 11.4
Radiated emissions:	27.6
Radiation	
Ionizing and non-ionizing:	28.21
Radiation inversion:	19.24
Radiation pattern:	21.4, 21.56
Radiation resistance:	21.2
Radio Amateur Civil Emergency Service (RACES):	1.18
Radio direction finding (RDF):	1.17, 21.66ff
Doppler shift:	21.73
Electronic antenna rotation:	21.70
Methods at VHF/UHF:	21.70
RFI:	27.18
Switched antennas:	21.72
Time of arrival:	21.72
Radio frequency (RF):	2.18
Radio frequency interference (RFI):	27.1ff
AC line (brute-force) filter:	27.24
Alternator whine:	27.37
Audio equipment:	27.33
Audio filter:	27.34
Automotive:	27.36
Bypass capacitors:	27.23
Choke placement:	27.29, 27.35
Common-mode:	27.9, 27.22
Common-mode choke:	27.25ff
Computers and accessories:	27.34
Consumer Electronics Association (CEA):	27.17
Cooperative agreement:	27.22
Corona discharge:	27.21
Differential mode:	27.9, 27.22
Electric fence:	27.15
Electric vehicle (EV):	27.39
Electrical noise:	27.15
Fundamental overload:	27.12ff
Glossary:	27.42
Ground:	27.13
Ground loop:	27.13
Ground-fault circuit interrupters (GFCI):	27.35
Harmful interference:	27.4
High-pass filter:	27.3, 27.23
Hybrid-electric vehicle (HEV):	27.39
Identifying:	27.13
Ignition noise:	27.38
Immunity:	27.4, 27.9
Intermodulation distortion (IMD):	27.4, 27.12ff
Keeping a log:	27.14
Locating source of:	27.16
Low-pass filter:	27.3, 27.23
Non-linear junction:	27.16
Notch filter:	27.28
Path:	27.9
Power-line noise:	27.15, 27.18ff
Product review testing:	27.4
Public-address equipment:	27.34
References:	27.43
Source:	27.9
Speakers:	27.34
Survival kit:	27.27
Susceptibility:	27.3ff
Switching supplies:	27.35
Telephone:	27.32
Transmitters:	27.27
Troubleshooting:	27.26ff
Ultrasonic location:	27.19
Utility complaint:	27.18
Victim:	27.9
Radio horizon:	19.23
Radio propagation:	19.1ff
Radio spectrum:	2.18
Classifications:	2.19
Radiosport (contesting):	1.12
Radioteletype (RTTY):	16.6
AFSK, FSK:	16.6
Baudot code:	16.6
Diddle character:	16.6
F1B <i>versus</i> F2B:	16.6
Fading:	16.8
Inverted or reverse shift:	16.6
Keyed AFSK:	16.6
Mark:	16.6
Minimal shift keyed (MSK):	16.8
Shift, LTRS and FIGS:	16.6
Shifts:	16.8
Space:	16.6
Spotting an RTTY signal:	16.6
Start and stop bit:	16.6
Terminal Unit (TU):	16.6
Tone pair:	16.6
Unshift-on-space (USOS):	16.8
USB and LSB:	16.6
Rain scatter:	19.24
Ramp wave:	2.16
Raspberry Pi:	24.18
Rate of change (Δ):	2.34
Rayleigh fading:	19.27
RC time constant (τ):	2.25
Reactance (X):	2.27
Capacitive (X_C):	2.27
Chart <i>versus</i> frequency:	2.40
Complex waveforms:	2.44
Inductive (X_L):	2.40
Like, in series and parallel:	2.41
Ohm's law for reactance:	2.40
Unlike, in parallel:	2.42
Unlike, in series:	2.42
Reactance modulator:	10.10
Reactive power (VA):	2.49
Reber, Grote W9GFZ:	14.1
Receive converters	
VHF and UHF:	12.29
Receiver	
Automatic gain control (AGC):	12.23ff
Bandwidth, various modes:	12.7ff
Beat frequency oscillator (BFO):	12.2
Direct conversion:	12.3ff
Dynamic range:	12.1, 12.19
FM:	12.28ff
Frequency accuracy:	25.34
Frequency stability:	25.34
Front end:	12.2
Image:	12.4, 12.9
Image rejection:	12.9, 12.12, 12.19
Intercept point (IP):	10.16
Intermediate frequency (IF):	12.2
Intermediate frequency (IF) selection:	12.9
Limiting, FM:	12.29
Noise and sensitivity:	12.17
Noise figure:	12.18
Noise floor:	12.1
Preamplifier:	12.18
Selectivity:	12.1
Sensitivity:	12.1, 12.17, 25.30
Software defined radio (SDR):	15.25ff
Superheterodyne (superhet):	12.2, 12.7ff
Third-order intercept point (IP3):	10.16
Troubleshooting:	26.25
Two-tone IMD test:	10.16
UHF and microwave:	12.31ff
Up- and down-converting:	12.19
VHF and UHF:	12.28ff
Reciprocal mixing:	9.7, 25.32
Recombination:	3.8
Reconstruction filter:	15.8
Rectification:	3.5, 7.4
Rectifier:	7.10
Average dc current rating, I_o :	7.11
Circuits:	3.17
Current inrush:	7.11

Equalizing resistors:	7.11	Internet and telephone access:	29.24
Fast-recovery:	7.10	Internet bandwidth:	29.24
Heat sinking:	7.12	Latency:	29.24
Inrush current limiting:	7.11	Licensing:	29.22
Parallel diodes:	7.11	Property and access:	29.21
Peak inverse voltage (PIV, PRV):	7.11	Requirements:	29.20
Peak repetitive forward current, I_{REP} :	7.11	Resources:	29.25
Peak surge current, I_{SURGE} :	7.11	Safety:	29.22
Power dissipation:	7.11	Site preparation:	29.21
Ratings and protection:	7.11	Repeater:	18.1ff
Reverse recovery time:	7.11	AM and SSB:	18.2
Schottky diode:	7.10	Amateur television (ATV):	18.2
Semiconductor:	7.10	Closed:	18.6
Series diode strings:	7.11	Controller:	18.4
Switching speed:	7.11	Coordination:	18.2, 18.9
Thermal resistance (θ):	7.11	D-STAR:	18.12ff
Reed-Solomon code:	16.15	D-STAR hardware:	18.13
References		Digital:	18.2, 18.3
Analog basics:	3.59	Digital voice:	18.15
Antenna:	21.75	DMR:	18.14
Antenna safety:	28.22	Duplexer:	18.4
Computer-Aided Circuit Design:	6.24	FM voice:	18.2, 18.4ff
D-STAR:	18.16	Glossary:	18.12
Digital electronics:	4.31	History:	18.1
Digital modes:	16.33	Internet linking:	18.10
Digital signal processing (DSP):	15.31	Linking:	18.4, 18.9
Electrical safety:	28.12	Narrowbanding:	18.9
Filters:	11.45	Offsets, standard:	18.9
Mixers, Modulators and Demodulators:	10.29ff	Operation (FM voice):	18.4
Modulation:	8.25	P25:	18.15
Oscillators and Synthesizers:	9.48	Remote receiver:	18.5
PC-board layout:	6.24	Rules and regulations:	18.3
Power sources:	7.47	Timer:	18.4
Propagation:	19.33	Tone access:	18.6
Radio frequency interference (RFI):	27.43	Reserve capacity, battery (RC):	7.44
Receivers:	12.37	Resistance (R):	2.3
Remote stations:	29.27	Bridge circuits:	25.3
RF power amplifier:	17.50	Effect of temperature:	2.4
RF techniques:	5.37	Equivalent resistance:	2.7
Software defined radio (SDR):	15.31	Four-wire resistance measurement:	25.5
Telemetry and Navigation Data:	14.12	Ohmmeter:	25.3
Test equipment and measurements:	25.57	Resistivity (ρ):	2.3
Transmission lines:	20.30	Resistor:	2.2, 2.5
Transmitters and Transceivers:	13.39	Bleeder:	7.13
Troubleshooting:	26.39	Carbon composition (carbon comp):	22.2
Reflection:	19.2	Carbon film:	22.2
Reflection coefficient (Γ_p):	5.36, 20.4	Color code:	22.3
Conversion between attenuation, SWR, return loss:	22.61	EIA identification and marking:	22.4
Refraction:	19.2	Equalizing:	7.29
Ionospheric:	19.7	Metalized film:	22.2
Tropospheric:	19.24	Non-inductive:	5.4
Refractive index:	19.2	Package dimensions:	22.3
Regeneration:	3.4	Parallel resistors:	2.7
Register		Parasitic inductance:	5.4
Formed by flip-flops:	4.11	Parasitic inductance model:	5.4
Shift:	4.11	Power:	22.4
Storage:	4.11	Precision:	2.4, 22.2, 25.3
Relay:	2.14	Pull-up:	3.45
Configurations:	2.14	Resistor pack:	3.44
Construction:	2.14	Series resistors:	2.8
Ratings:	2.14	Standard values:	22.5
Types of relays:	2.15	Temperature coefficient (tempco):	2.5
Reluctance ($\mathfrak{R}$):	2.33	Thick-film power:	22.3
Remote sensing:	14.1	Thin-film resistor:	3.26
Batteries:	14.10	Types of resistors:	2.5
HF payloads:	14.12	Wire-wound:	22.3
High-altitude:	14.10	Resolution:	25.2
Payloads:	14.11	Resolution bandwidth (RBW):	25.22
Platform design:	14.9	Resonance:	2.43, 9.1
Remote stations:	29.19ff	Of ferrite cores:	5.20
Basic HF station:	29.25	Resonant circuits:	2.55
Connecting and controlling:	29.20ff	Antiresonance:	2.57
Electrical power:	29.21	Bandwidth:	2.57
Ethernet bridge:	29.24	Circulating current:	2.60
Insurance and security:	29.22	Parallel:	2.58

Parallel, above and below resonance:	2.59	RTL-SDR:	15.30ff
Parallel, loaded Q:	2.61	Run length encoding (RLE):	16.4
Parallel, use for impedance matching:	2.61	Ruthroff transformer:	20.21
Resonant frequency:	2.55		
Selectivity:	2.56	S	
Series:	2.56	S (scattering) parameters:	5.35
Series and parallel:	2.43	S-R flip-flop:	4.9
Series, unloaded Q:	2.56	Safe operating area (SOA):	3.14, 7.17
Resonant frequency:	2.55	Safety	
Return loss (RL):	5.36, 11.11, 20.4	Antenna:	28.13ff
Converting between attenuation, reflection coefficient, and SWR:	22.61	Bleeder resistor:	7.30
Return loss bridge (RLB):	25.25	Chemical properties and hazards:	23.2
Reverse Beacon Network:	19.21	Electrical:	28.1ff
Reverse bias:	3.9	Electrical safety rules and guidelines:	26.1ff
Reverse breakdown voltage:	3.15	Generator:	29.15
Reverse leakage current:	3.9	Remote stations:	29.22
RF ammeter:	25.20, 25.46	RF exposure:	28.22ff
RF amplifier		Soldering:	23.9
Feedback:	5.17	Workbench and shop:	23.1ff
Power amplifiers:	17.1ff	Safety ground:	7.2
RF choke:	2.55, 17.16, 22.10	Safety, electrical:	28.1ff
RF connectors:	22.46ff, 29.7	Back-feeding ac line:	28.5
RF exposure and safety:	28.22ff	Class 1, 2, 3 wiring:	28.5
Cardiac pacemakers:	28.27	Distribution box:	28.3
Environments, controlled and uncontrolled:	28.25	Energized circuits:	28.11
FCC exposure regulations:	28.26	Lockout:	28.2
Low-frequency fields:	28.28	National Electrical Code (NEC):	28.2
Maximum permissible exposure (MPE):	28.23	References:	28.12
MPE limits table:	28.26	Solar panel:	28.11
Power density:	28.29	Uninterruptible power supply (UPS):	28.11
Power threshold table:	28.27	Safety, RF exposure:	28.22ff
RF awareness guidelines:	28.30	Sample rate:	15.2
RF Exposure and You:	28.30	Sampling, analog-digital conversion:	15.6ff
RF safety standards:	28.25	Satellite	
Specific absorption rate (SAR):	28.23	Propagation:	19.30
Station evaluation:	28.27	Space weather:	19.21
Thermal and athermal effects:	28.23	Satellites (amateur):	1.15
RF heating:	2.70, 5.8	Saturation (magnetic):	2.34
RF impedance measurements:	25.25	Saturation (semiconductor):	3.11
RF interference (RFI):	27.1ff	Sawtooth wave:	2.16
Automotive:	29.14	Scalar network analyzer:	25.26
RF measurements:	25.19ff	Scale, meter:	25.8
RF power amplifier:	17.1ff	Scaling:	3.1
RF power measurements:	25.20	Scatter	
RF power modules		Forward:	19.12
Specifications:	22.31	Rain:	19.23
RF power transistors (MOSFET)		Tropospheric:	19.23
Specifications:	22.28ff	Scattering:	19.2
RF probe:	25.19	Scattering (S) parameters:	25.26
RF sniffer:	27.41	Schematic capture	
RF transformers:	5.27	Subcircuits:	6.6
Air-core resonant:	5.27	Schematic capture software	
Binocular core:	5.29	Eagle:	6.16
Broadband ferrite:	5.28	Kicad:	6.16
RF voltmeter:	25.55	Schematic diagram:	2.2
Right-hand rule:	2.32	Schottky barrier:	3.15
Ringing (filter):	11.5	Schottky diode:	3.15
Ripple:	7.4	Scintillation:	19.26, 19.30
Bandwidth (filter):	11.3	SCR (<i>see</i> Silicon controlled rectifier)	
Filter:	11.3	Screen grid:	17.5
Frequency:	7.13	SDR (<i>see</i> Software defined radio)	
Voltage:	7.13	SDR#	15.30ff
Rise and fall time		Secondary (battery):	7.32
Keying:	25.36	Secondary emission:	17.5
RJ connector:	29.8	Section Manager (SM):	27.2
RL time constant (τ):	2.37	Selective fading:	8.4, 8.10
Roll-off:	3.5	Selectivity:	12.1
Roll-off (filter):	11.3	Self-discharge:	7.32
Root-mean-square (RMS):	2.20, 25.9	Self-resonance:	5.9
Non-sinusoidal waveforms:	25.9	Semiconductor	
Rope:	28.16	Acceptor and donor impurities:	3.8
RS-232:	4.25, 4.28	Compound:	3.8
RS-274X:	6.24	Cross-reference:	26.10
RS-422:	4.29	Cutoff (semiconductor):	3.11

Depletion region:	3.9	Sine wave generation (DSP):	15.17ff
Doping:	3.8	Single sideband (SSB):	8.5, 10.7
Extrinsic:	3.8	DSP modulator and demodulator:	15.22ff
Free electron:	3.8	Filter method:	8.5, 13.5
Hole:	3.8	Lower and upper sideband (LSB and USB):	8.5
Intrinsic:	3.8	Phasing method:	8.5, 13.6
Junction semiconductor:	3.9	Single-sideband, suppressed-carrier:	13.5
Majority and minority carriers:	3.8	Weaver method:	8.5, 13.6, 15.24
Monocrystalline:	3.8	Skeleton slot antenna:	21.43
N-type, P-type:	3.8	Skew path:	19.19
Photoconductor:	3.8	Skin effect:	5.6, 5.8, 20.1
PN junction:	3.8	Skin depth (δ):	5.8
Polycrystalline:	3.8	Skip zone:	19.8
Recombination:	3.8	Sky wave propagation:	19.6ff
Safe Operating Area (SOA):	3.14	Slew rate:	3.2
Saturation:	3.11	Slow-scan television (SSTV):	8.19, 16.13
Substitution:	26.11	Analog modes:	8.19
Substrate:	3.12	Digital modes:	8.20
Temperature effects:	3.14	Frame sequential:	8.19
Thermal runaway:	3.14	Line sequential:	8.19
Sensitivity:	12.1, 12.17	Redundant digital file transfer (RDFT):	8.20
Sensors:	14.1ff	Remote sensing:	14.11
Calibration:	14.4	Vertical interval signaling (VIS):	8.19
Capacitance-based:	14.3	Small-signal transistor model:	3.29, 5.16
Current-based:	14.2	BJT:	3.29
Digital interfaces:	14.4	FET:	3.36
Powering:	14.6	Smith chart:	20.4
Remote sensing:	14.1	Sniffer probe:	25.23
Resistance-based:	14.2	Snubber network:	2.38
Voltage-based:	14.3	Software	
Sequencing, transverter:	13.35	4nec2 by Arie Voors:	21.21
Sequential logic:	4.8ff	AADE Filter Design and Analysis:	11.26
Serenade:	6.10	Airmail:	16.26
Serial I/O interface:	4.20ff, 4.27ff	Analog Filter Wizard by Analog Devices:	11.22
IEEE-1394 (FireWire):	4.29	ASAPS:	19.22
RS-232:	4.28	Codec2 by VK5DGR:	16.16
RS-422:	4.29	d*Chat:	16.29
Universal serial bus (USB):	4.29	D-RATS:	16.29
Serial Peripheral Interface (SPI):	4.20, 4.21, 14.5	Diplexer Designer by W4ENE:	11.42
Service monitor:	25.37	Dplus:	16.29, 18.13
Shack notebook:	26.6	DPRS:	16.29
Shannon-Hartley theorem:	8.17	Dream:	16.15
SHF (frequency range classification):	2.19	Elsie by W4ENE:	11.9
Shield, RFI:	27.22	ExpressPCB:	17.36, 17.49
Shielding, oscillator:	9.19	EZNEC by W7EL:	21.21
Shift register:	4.11	FilterPro by Texas Instruments:	11.22
Shock hazards and effects:	26.1, 28.12	FLDIGI by W1KHJ:	16.5
Shock mounts:	29.9	FreeDV by KDØEAG and VK5DGR:	16.15
Short skip:	19.13	GC Prevue:	6.24
Shortwave broadcast bands:	19.22	Gerby:	6.24
Shunt feed:	21.25	Helical by W4ENE:	11.34
Sidescatter:	19.18	HFTA (HF Terrain Analysis):	29.21
Siemens (S):	2.3, 2.28, 2.39	IONCAP:	19.22
Signal generator:	25.27	LTSpice:	17.11
Use for troubleshooting:	26.5	MATCH by WØIYH:	20.11
Signal injector		Meter by W4ENE:	17.49
Use for troubleshooting:	26.5	Modulators and demodulators:	15.29
Signal source		MUF prediction:	19.22
Use for troubleshooting:	26.5	MultiPSK:	16.13
Signal to noise ratio (SNR):	5.30	PC-board layout:	6.15ff
Signal tracing:	26.6	PI-EL Design by W4ENE:	17.10
Signal tracing and injection:	26.15ff	PropLab Pro:	19.22
Signal-to-noise and distortion ratio (see SINAD)		QuadNet by W4ENE:	11.21
Signal-to-noise ratio (SNR):	3.28, 12.1	SVC Filter Designer by W4ENE:	11.11, 17.31
Silicon (device):	3.9	TLW by N6BV:	20.4
Silicon controlled rectifier (SCR):	3.11	TubeCalculator:	17.7ff
Anode gate:	3.11	VOACAP:	19.22
Cathode gate:	3.11	W6ELProp:	19.22
Use in a crowbar circuit:	3.11	Webench by National Semiconductor:	11.22
Use in ac power control:	3.11	WinDRM by HB9TLK:	16.15
Simplex:	18.2	WSJT by K1JT:	16.14
Simplex repeater:	14.11	Software (CAD)	
SINAD:	3.49, 25.31	Advanced Design System (ADS):	6.10
Sinc function:	8.17, 15.8	Ansoft Designer SV2:	6.2
Sine wave:	2.16	ARRL Radio Designer:	6.5

<i>AutoCAD</i> :	6.3	Split operation:	18.2
<i>B2 Spice</i> :	6.3	Repeater offsets:	18.9
<i>EAGLE</i> :	6.2	Splitter, power:	20.21
<i>gEDA</i> :	6.2	Sporadic E propagation:	19.13
<i>ICAP4</i> :	6.15	Spread spectrum (SS):	8.14ff, 16.12
<i>Kicad</i> :	6.2	Chip rate:	8.15
<i>LTSpice</i> :	6.2	Code-division multiple access (CDMA):	8.16
<i>MICROCAP9</i> :	6.15	Direct sequence (DSSS):	8.16, 16.12
<i>OrCAD</i> :	6.2	Frequency hopping (FHSS):	8.15
<i>PSPICE</i> :	6.14	Processing gain:	8.14
RF-fluent:	6.9	Spreading:	16.12
<i>Serenade</i> :	6.10	Spurious emissions:	27.4ff, 27.12
Software defined radio (SDR):	15.1, 15.25ff	Spurious response	
Control accessory:	24.34	Spectrum analyzer:	25.22
Dynamic range:	15.26	Spurious signals	
Glossary:	15.32	Transmitter:	13.16
Hardware:	15.25ff	Spurious-free dynamic range (SFDR):	3.49, 15.2
HF upconverter:	15.33	Square wave:	2.16
Local oscillator (LO):	15.28	Square-law device:	3.37
Modulators and demodulators:	15.29	Squegging (squeeging):	9.11
References:	15.31	Squelch:	18.8
RTL-SDR:	15.30ff	Sensitivity test:	25.33
Sampling at RF:	15.27	SSNe:	19.21
Software architecture:	15.28ff	SSTV (<i>see</i> Slow-scan television)	
Speech processing:	15.30	Standard cell (battery) sizes:	7.32
USB dongle:	15.30ff	Standard frequency stations:	25.12
Solar (Sunspot) Cycle 24:	19.11	Standards	
Solar 27-day rotation:	19.12	Measurements:	25.1
Solar battery or cell (<i>see</i> Photovoltaic cell)		Symbols, IEEE 315A:	10.3
Solar cycle:	19.10	Traceability and transfer:	25.1
Solar flare:	19.12	Standing-wave ratio (SWR, VSWR, ISWR):	20.4
Solar flux:	19.10	Bridge:	20.24
Solar panel:	3.23	Bridge, audible:	24.20
Solar power		Conversion of attenuation, reflection coefficient, and return loss:	22.61
Remote stations:	29.21	Converting to return loss:	5.36
Solar wind:	19.6	Flat line:	20.4
Soldering:	23.7ff	Myths about:	20.16
Desoldering:	23.9	Star ground:	27.13
Irons and guns:	23.7	Static (precipitation):	19.31
Lead-free:	23.8	Station	
Printed-circuit board (PCB):	23.21	Accessory projects:	24.1ff
Reduction of Hazardous Substances (RoHS):	23.8	Assembly:	29.1ff
Safety:	23.9	Documentation:	29.8
Solder types	23.7	Layout:	29.2ff
Surface-mount technology (SMT):	23.11	Location:	29.1
Solenoid:	2.14	Power:	29.2
Solenoidal coil:	2.32	Stefan-Boltzmann's constant (k):	5.30, 5.33
Solid-state relay:	4.20	Step recovery diode (SRD):	13.7
Sound card:	16.5	Stethoscope	
Test equipment:	25.39	Use for troubleshooting:	26.6
Source, RFI:	27.11	Stop band (filter):	11.2
Source-follower (<i>see</i> Common-drain amplifier)		Stop band depth and frequency:	11.4
Space weather satellite:	19.22	Storage register:	4.11
Span, frequency:	25.22	Stratosphere:	19.6
Speakers		Stripline:	11.30
RFI:	27.34	Stub (transmission line):	20.7
Twisted-pair cable:	27.34	As filters:	20.7
Specific energy (battery):	7.33	Combinations:	20.9
Specific power (battery):	7.33	Connecting:	20.8
Spectral power and voltage density:	5.30	Field Day stub filters:	20.10
Spectral purity		Measuring:	20.8
Transmitter:	25.34	Quarter- and half-wave:	20.7
Spectrum analyzer:	25.20ff	Universal:	20.24
Features and specifications:	25.24ff	Subaudible tone:	18.8
Tracking generator:	25.24	Subaudible tone (<i>see also</i> CTCSS):	18.6
Use of:	25.22ff	Substitution guide (semiconductor):	3.8
Spectrum, frequency range classifications:	2.19	Sudden ionospheric disturbance (SID):	19.12
Speech		Summing amplifier:	3.44
Clipping, AF:	13.11	Sunspot:	19.10
Clipping, IF:	13.13	Sunstone Circuits (PCB vendor):	6.16
Compression:	13.11	Superheterodyne (superhet) receiver:	12.2, 12.7ff
Processing:	13.10	Bandwidth, various modes:	12.7
Processing, with digital signal processing (DSP):	15.30	Collins system:	12.11
Spike (<i>see</i> Transient)		Crystal lattice filters:	12.10
Splatter:	8.21		

IF selection:	12.9	Telemetry:	14.7ff
Multiple conversion:	12.11	Digital modes:	14.9
Sensitivity:	12.17	Non-licensed:	14.8
Superheterodyne (transmitter):	13.9	Telephone	
Superposition:	3.1	RFI:	27.32
Suppression, sideband		RFI filter:	27.33
Measurement:	25.35	Television interference (TVI):	27.1, 27.2ff
Surface acoustic wave (SAW):	11.29	Analog TV:	27.29
Surface-mount technology (SMT):	22.2, 23.10	Cable TV:	27.30ff
Package types:	23.10	Channel guide:	27.30
Soldering:	23.11	Digital TV:	27.29
Susceptance (B):	2.28	DVD and VCRs:	27.32
Capacitive (B_C):	2.28	Electrical noise:	27.30
Inductive (B_L):	2.39	Fundamental overload:	27.27
Susceptibility, RF:	27.3ff	High-pass filter:	27.28
<i>SVC Filter Designer</i> by W4ENE:	11.11, 17.31	Preamplifiers:	27.28
Sweep, oscilloscope:	25.13	Spurious emissions:	27.29
Swinging choke:	7.14	Temperature	
Switch:	2.12	Antenna:	5.31
Make and break:	2.13	Excess:	5.30
Poles and positions:	2.13	Noise:	5.30
Ratings:	2.13	Temperature coefficient (tempco):	2.5, 22.2
Types of switches:	2.13	Capacitor:	2.29
Switched-capacitor filter (SCAF):	11.19	Temperature compensated oscillator:	9.21
Switching circuit:	3.41	Temperature compensation:	2.71
Circuit design:	3.41	Oscillator:	9.18
High-side and low-side switching:	3.41	Temperature inversion:	19.24
Power dissipation:	3.41	Temperature sensor:	3.59
Reactive loads:	3.41	Terminal node controller (TNC):	16.17
Transistor selection:	3.41	Modem:	16.17
Switching mixer:	10.18ff	Multi-protocol controller (MPC):	16.17
Switching supplies (also <i>see</i> Switchmode power supplies)		Multimode communications processor (MCP):	16.17
RFI:	27.35	Terminations:	25.16, 25.29
Switching time:	5.14	Tesla (T):	2.32
Switchmode power conversion:	7.21	Test equipment	
Boost converter:	7.23	Troubleshooting:	26.3ff
Bridge converter:	7.25	Test probes:	26.4
Buck converter:	7.21	Adaptors:	25.6
Buck-boost converter:	7.23	Inductive pickup:	26.4
Continuous conduction mode (CCM):	7.22	Use for troubleshooting:	26.4
Design aids and tools:	7.28	Tetra (protocol):	16.29
Discontinuous conduction mode (DCM):	7.22	Tetrode:	17.5
Flyback converter:	7.23	Thermal conductivity (k):	2.67
Forward converter:	7.25	Thermal resistance (θ):	2.67
Pulse-width modulation:	7.22, 7.26	Rectifier:	7.11
RFI:	7.21, 27.13	Thermal runaway:	3.14
Switching loss:	7.21	Thermionic emission:	17.4
SWR meter:	25.38, 26.4	Thermistors:	2.71
SWR monitor:	24.4	Thermocouple detector:	25.20
Symbol library (PCB layout):	6.16	Thevenin equivalent circuit:	2.9
Symbol rate:	8.8	Thevenin's Theorem:	2.9
Synchronicity (logic):	4.8	Thin-film resistor:	3.26
Synchronous detector:	8.4	Third-order intercept point (IP3):	10.16, 25.32
Synchronous transformer:	20.12	Thompson, Sir William (Lord Kelvin):	25.1
Synthesizer, frequency:	9.30ff	Three-terminal voltage regulator:	7.18
Direct digital synthesis (DDS):	15.17	Adjustable regulator:	7.19
System Fusion (Yaesu):	16.29, 18.15	Current source:	7.20
		Increasing output current:	7.20
		Low dropout regulator:	7.19
		Throb:	16.12
		Thyristor:	3.10
T		Time base	
T antenna:	21.28	Frequency counter:	25.10ff
T match:	21.38	Time constant (τ)	
T network:	5.26, 20.10	RC:	2.25
Design:	20.15	RL:	2.37
Tank circuit:	9.1, 17.9ff	Time Division Multiple Access (TDMA):	16.31, 18.14
Component ratings:	17.15ff	Time domain:	2.17, 25.20
Efficiency:	17.10	Time standard stations:	25.12
Flywheel effect:	17.9	Time-invariant:	3.1
Manual design methods:	17.12	Timer (multivibrator) IC:	3.55
Tayloe mixer:	10.28ff	Astable (free-running):	3.55
TCP/IP:	16.23	Monostable (one-shot):	3.55
Technical Coordinator (TC):	27.2	<i>TLW</i> by N6BV:	20.4
Technical Coordinator (TC), ARRL:	26.2	Tolerance:	2.4, 22.2
Technical Specialist (TS), ARRL:	26.2		

Tone			
Decoder, DSP:	15.19		
Repeater access:	18.6		
Tools			
Care of:	23.3		
Recommended for electronics:	23.4		
Toroid winding:	5.29		
Total harmonic distortion+noise (THD+N):	3.49		
Tower			
Base, concrete:	28.15		
Carabiner:	28.16		
Climbing harnesses and belts:	28.20		
Climbing safety:	28.20		
Crank-up:	28.9		
Erection and maintenance:	28.16		
Gin-pole:	28.16		
Ground crew:	28.20		
Guy wires, lengths to avoid:	22.40		
Guyed:	28.14		
Guying and guy wires:	28.17		
Legal considerations:	28.13		
Roof-mounted:	28.15		
Ropes:	28.16		
Safety references:	28.22		
Safety tips:	28.22		
Self-supporting:	28.14		
TIA-222:	28.13		
Wind load:	28.13		
TR switching:	13.30		
Amplifier interfacing:	13.32		
Tracking generator:	25.24		
Transceiver			
Architecture:	13.28ff		
Break-in (CW):	13.29		
Handheld:	18.7		
Home station (FM voice):	18.7		
Mobile (FM voice):	18.7		
Push-to-talk (PTT):	13.29		
Software defined radio (SDR):	15.25ff		
TR switching:	13.30		
Troubleshooting:	26.28		
Upconverting:	13.28		
Voice-operated-transmit (VOX):	13.29ff		
Transconductance:	3.6		
Forward transconductance, g_m :	3.19		
Transducer:	2.16		
Transequatorial propagation (TE):	19.19		
Transfer characteristics:	3.3		
Transfer function:	3.3, 3.27		
Transfer switch:	28.5		
Transformer:	2.62		
50 Hz considerations:	7.3		
Broadband (RF):	17.31		
Color code:	22.15		
Evaluating:	7.3		
High-voltage:	7.30		
Impedance matching:	20.12, 21.57		
Impedance ratio:	2.64		
Interwinding capacitance:	2.65		
Isolation:	7.3		
Laminations:	2.63		
Leakage flux:	2.65		
Leakage reactance:	2.65		
Losses:	2.65		
Magnetizing inductance:	7.3		
Power:	7.3		
Power ratio:	2.64		
Primary and secondary:	2.62		
RF:	5.27		
Shielding:	2.66		
Step-up and step-down:	2.63		
Turns ratio:	2.63		
Volt-ampere rating:	7.3		
Voltage and current ratio:	2.63		
Transient:	7.12		
Transient protection			
Gas tube:	7.12		
Varistor:	7.12		
Zener diode:	7.12		
Transient suppressor diode (TVS):	3.17		
Transimpedance amplifier:	14.3		
Transistor			
Gain <i>versus</i> frequency:	5.16		
Switching circuits:	3.41		
Transistor array IC:	3.54		
Transistor tester			
Use for troubleshooting:	26.6		
Transistor-transistor logic (TTL):	4.14		
Circuits:	4.15		
Driving CMOS:	4.18		
Three-state outputs:	4.16		
Unused inputs:	4.16		
Transition region (filter):	11.2		
Transition time (digital circuit):	4.4		
Transmatch (<i>see</i> Antenna Tuner)			
Transmission line			
Attenuation (loss):	20.4		
Attenuation of two-conductor twisted pair:	22.41		
Balanced and unbalanced load:	20.17		
Balancing devices:	20.17		
Coaxial cable:	20.1		
Digital circuits:	20.27		
Effects of loss:	20.5		
Impedance of two-conductor twisted pair:	22.41		
Impedance transformation:	20.7		
Impedance transformer:	20.19ff		
Incident, forward, and reflected waves:	20.4		
Ladder line:	20.6		
Length per dB of loss:	20.6		
Load:	20.3		
Lumped-constant:	20.3		
Matched and mismatched:	20.3		
Matched- (ML) and mismatched-line loss:	20.5		
Mechanical considerations:	20.6		
Microstrip:	11.30		
Open-wire:	20.1		
Parallel-conductor (twin-lead):	20.1		
Phasing antennas:	20.12		
Quarter-wave (Q) section:	20.12		
Radiation cancellation in:	20.1		
Radiation from:	20.17		
Selecting type of line:	20.5		
Specifications:	22.48		
Stripline:	11.30		
Stub placement:	20.8		
Stubs:	20.7		
Synchronous transformer:	20.12		
Termination:	20.3		
Transformer:	17.29		
Twin-lead:	20.1		
Velocity factor (VF):	20.1, 20.8		
VHF/UHF:	21.56		
Waveguide:	20.28		
Weatherproofing:	28.19		
Window line:	20.1		
Transmitter			
Amplitude modulation (AM):	13.4		
Angle modulation (FM, PM):	13.6		
Automatic level control (ALC):	13.17		
Bandpass filter:	13.23		
Beacon:	13.38		
Carrier and unwanted sideband suppression:	25.35		
CW keying waveform:	13.2		
CW mode:	13.15		
Frequency modulation (FM):	13.7		
Intermodulation distortion:	25.35		
Modulation:	13.24		
Oscillator:	13.22		
Phase modulation (PM):	13.8		
Speech processing:	13.10		

Spurious signal:	13.16	Twisted-pair speaker cable:	27.34
Superheterodyne, SSB/CW:	13.9	Two-port network:	3.27
Troubleshooting:	26.26	Two-port network parameters:	5.34
Two-tone test:	13.14, 25.35	Two-port parameters:	5.34
VHF signal sources:	13.19	Two-tone IMD:	8.21, 10.16
Wideband noise:	13.16	Two-tone test:	25.35
Transverse electromagnetic mode (TEM):	11.30	Transmitter:	13.14
Transverter controller:	13.35		
Trap (antenna):	21.14, 21.17, 21.27	U	
Traveling wave tube:	9.29	Ufer ground:	28.7
Tri-state gate:	4.6	UHF (frequency range classification):	2.19
Triac:	3.11	UHF connector:	29.7
Triangle wave:	2.16	Ultimate attenuation (filter):	11.2
Triggering		Ultraviolet radiation:	19.6
Oscilloscope:	25.13, 25.17	Underwriter Labs (UL):	28.1
Triggering, flip-flop:	4.9	Unintentional emitters:	27.5
Triode:	17.5	Uninterruptible power supply (UPS)	28.11
Tripler (frequency):	13.7	Unipolar transistor (<i>see</i> Field-effect transistor)	
Triplexer:	20.8	Units	
Troposphere:	19.6	Systems of measurement:	25.1
Tropospheric		Units and conversion factors:	22.58
Bending:	19.27	Unity-gain buffer:	3.44
Ducting:	19.25ff	Universal serial bus (USB):	4.29
Fading:	19.27	Universal stub:	20.24
Propagation:	19.22ff	Upconverter (HF):	15.33
Refraction:	19.24	USB:	4.25
Scatter:	19.23	Battery charging:	7.38
Troubleshooting		V	
Amplifier circuits:	26.23	Vackar oscillator:	9.12
Amplifiers, power:	26.28ff	Vacuum tube:	17.4ff
Antenna systems:	26.32ff	Cathode:	17.4
Assessing symptoms:	26.13	Construction:	17.6
Battery hazards:	26.8	Cooling methods:	17.6
Circuit-level, analog:	26.18ff	Grid (control, screen, suppressor):	17.5
Circuit-level, digital:	26.20ff	Grid dissipation:	17.14
Completing repair:	26.21	Nomenclature:	17.5
Component level:	26.7ff	Operating parameters:	17.8ff
Connectors:	26.7	Pentode:	17.5
General symptoms:	26.26	Plate (anode):	17.4
Inspections:	26.14	Plate dissipation:	17.14
Microprocessor equipment:	26.17	Ratings:	17.14
Newly constructed equipment:	26.14	Screen dissipation:	17.13
Oscillators:	26.24	Secondary emission:	17.5
Power supplies:	26.22	Specifications:	22.34
Professional repair:	26.22	Tetrode:	17.5
Radio frequency interference (RFI):	27.26ff	Thermionic emission:	17.4
Receivers:	26.25	Triode:	17.5
Recommended equipment:	26.3ff	Troubleshooting:	26.12
References:	26.39	Varactor diode:	3.16, 13.7
Search engines:	26.2	Specifications:	22.19
Semiconductors:	26.9ff	Variable crystal oscillator (VXO):	9.25
Shack notebook:	26.6	Variac (transformer):	2.66
Signal tracing and injection:	26.15ff	Varicode:	8.8, 16.3, 16.8ff
Systematic vs instinctive:	26.12	Varistor:	7.12
Television interference (TVI):	27.27	VCR (Videotape Cassette Recorder) RFI:	27.32
Transceiver:	26.28	Vector:	2.44
Transmit amplifier modules:	26.25	Vector network analyzer (VNA):	20.9, 25.26
Transmitters:	26.26	Low-frequency adaptor:	25.55
Tube tester:	26.36	Velocity (radio wave):	19.1
Vacuum tubes:	26.12	Velocity factor (VF):	20.1, 20.8
TTL (<i>see</i> transistor-transistor logic)		Vertical amplifier:	25.12
Tube (<i>see</i> Vacuum tube)		Vertical antenna:	21.22ff
Tube tester:	26.36	Trap:	21.27
<i>TubeCalculator</i> software:	17.7ff	Vertical interval signaling (VIS):	8.19
Tubing, aluminum:	21.34	Vestigial sideband (VSB):	8.18
Tuned circuit		Digital television:	8.11
Single-tuned circuit:	5.13	VFO (<i>see</i> Oscillator)	
Tuned radio frequency (TRF) receiver:	12.3	VHF (frequency range classification):	2.19
Tuning procedure		VHF/UHF	
Amplifier, RF power:	17.14	FM voice equipment:	18.7
Tuning tools:	23.6, 23.24	Home station antenna (for repeaters):	18.7
Turn-around time, transmitter:	25.36	Mobile antennas:	18.7
Turnstile antenna:	21.61	Propagation (mobile):	19.27ff
Tuska, Clarence:	1.1	Victim, RFI:	27.11
Twelfth-wave transformer:	20.13		

Video bandwidth:	25.22
Vintage equipment:	1.17
Repair and restoration:	26.35ff
Virtual height:	19.7
VLF (frequency range classification):	2.19
VOACAP:	19.22
Vocoder:	16.28, 18.15
Voice-operated transmit (VOX):	13.29ff
Volt-amp reactive (VAR):	2.49
Volt-ampere rating (transformer):	7.3
Voltage	
Potential difference:	25.2
Voltage (V, E):	2.1
Potential:	2.1
Voltage drop:	2.9
Voltage source:	2.9
Volts (V):	2.1
Voltage divider:	2.8
Voltage multiplier:	7.7, 7.10
Full-wave voltage doubler:	7.7, 7.8
Half-wave voltage doubler:	7.7
Voltage tripler and quadrupler:	7.8
Voltage probe:	25.23
Voltage reference IC:	3.54
Voltage regulation:	7.13
Adjustable regulator:	7.19
Dynamic and static regulation:	7.13
Generator:	29.16
Three-terminal voltage regulator:	7.18
Voltage regulator IC:	3.54, 22.17
Specifications:	22.20
Voltage-controlled oscillator (VCO):	9.32, 9.37
Noise:	9.43
Phase-locked loops (PLL):	9.37
Voltage-current converter:	3.47
Voltage-follower circuit:	3.44
Voltage-power conversion:	22.60
Voltmeter	
Digital multimeter (DMM):	25.4
Multiplier resistor:	25.8
RF:	25.55
Sensitivity, ohms-per-volt:	25.3
Vacuum-tube, VTVM:	25.3
Volunteer Consulting Engineer (VCE), ARRL:	28.1
Volunteer Examiner (VE):	1.5
VOM (volt-ohm-meter):	25.3
Von Neumann architecture:	15.4
VOX (<i>see</i> Voice-operated transmit)	
VSB, 8-VSB (<i>see</i> Vestigial sideband)	

W

W1AW:	1.7
W6ELProp:	19.22
Waterfall display:	16.5
Watt (W):	2.11
Watt-hour (Wh):	2.11
Wattmeter:	26.4
Directional:	20.4, 25.20
Reflectometer:	20.4
Wave cyclone:	19.26
Waveguide:	20.26
Coax-to-waveguide adapters:	25.29
Coupling to:	20.27
Cutoff frequency:	20.26
Dimensions:	20.27
Dominant mode:	20.27
Modes (TM, TE):	20.27

Wavelength (λ):	2.18, 19.1
Wavemeter:	25.11
Waveshaping, CW:	8.8, 10.7
Weaver method (SSB generation):	8.5, 13.6, 15.24
Webench by National Semiconductor:	11.22
Weber (Wb):	2.32
Weston, Edward:	25.3
Wheatstone bridge:	25.3
Whip antenna:	21.45ff
Loading:	21.47
White noise:	5.30
Wien bridge:	25.17
Oscillator:	25.44
WiFi:	4.26
Wilkinson hybrid combiner:	25.29
WinCAP Wizard:	19.22
WinDRM by HB9TLK:	16.15
Winlink 2000 (WL2K):	16.25ff
Airmail:	16.26
B2F:	16.26
Common Message Servers (CMS):	16.26
Paclink:	16.24
PACTOR:	16.24
PMBO:	16.26
Radio Message Server (RMS):	16.26
TELNET:	16.26
WINMOR:	16.22
Comparison to PACTOR:	16.22
SCAMP:	16.22
Sound card:	16.22
TNC interface:	16.22
Wire size	
Mobile installations:	29.13
Wire, specifications:	22.39
Wireless network:	4.29
WIRES-X (Yaesu):	18.15
WSJT by K1JT:	16.14
Meteor scatter:	19.15
WSPR:	16.15
Wullenweber antenna:	21.70
WWV, WWVH:	19.21, 25.12
Propagation forecast:	19.10, 19.12

X

X wave:	19.9
XOR gate:	4.5

Y

Y (admittance) parameters:	5.35
Yagi antenna:	21.32ff
Stacking:	21.60
VHF/UHF:	21.60
YIG-tuned oscillator:	9.28

Z

Z (impedance) parameters:	5.35
Zener diode:	3.16
Noise generation:	3.18
Specifications:	22.18
Voltage regulator:	7.15
Zepp (antenna):	21.7
Zero (transfer function):	3.4, 11.20, 11.23
Zero bias:	17.2
Zero-stuffing:	15.9
Zigbee:	4.26

Project Index

A

Amplifier, RF Power	
10 GHz 2 W Amplifier:	17.40
250 W Broadband Linear Amplifier:	17.36
3CX1500D7 RF Linear Amplifier:	17.45
6 Meter Kilowatt Amplifier:	17.49
All-Mode, 2 Meter, 80 W Linear Amp:	17.38
Everyham's Amplifier:	17.42
QSK Controllers for Amplifiers:	24.43
Antenna accessory	
Eight-Channel Remote-Control Antenna Switch:	24.50
Legal-Limit Bias-Tee:	24.49
Antenna tuner	
160 and 80 Meter Matching Network for Your 43-Foot Vertical:	24.9
Switching the Matching Network for Your 43-Foot Vertical:	24.11
Z-match:	24.1
Antenna, accessory	
A Raspberry Pi Server/Client for Antenna Rotator s:	24.18
Audible Antenna Bridge:	24.20
External Automatic Antenna Switch for Use with Yaesu or ICOM Radios:	24.14
Low-cost Remote Antenna Switch:	24.18
Microprocessor-controlled SWR Monitor:	24.4
Mounts for Remotely-Tuned Antennas:	21.52
Transmitting Choke Baluns:	20.22
Antenna, HF	
40-15 Meter Dual-Band Dipole:	21.16
All-Wire 30 Meter CVD:	21.32
Compact Vertical Dipole (CVD):	21.30
Extended Double-Zepp For 17 Meters:	21.22
Family of Computer-Optimized HF Yagis:	21.37
Five-Band, Two-Element HF Quad:	21.40
Half-Wave Vertical Dipole (HVD):	21.29
Low-band Quad and Delta Loops:	21.41
Multiband Center-Fed Dipole:	21.14
Multiband Horizontal Loop Antenna:	21.44
Retuning a CB Whip Antenna:	21.53
Skeleton Slot for 14-30 MHz:	21.43
Top-Loaded Low-Band Antenna:	21.26
Triband dipole for 30, 17, and 12 meters:	21.22
Triband Moxon Yagi Antenna:	21.38
Two W8NX Multiband, Coax-Trap Dipoles:	21.21
Two-Band Loop for 30 and 40 Meters:	21.43
W4RNL Inverted-U Antenna:	21.17
Antenna, VHF/UHF	
A Medium-Gain 2 Meter Yagi:	21.61
Cheap Yagis by WA5VJB:	21.62
Fixed Moxons for Satellite Operation:	21.65
Homebrew Coaxial Dipole for VHF or UHF:	21.58
Simple, Portable Ground-Plane Antenna:	21.58
Three and Five-Element Yagis for 6 Meters:	21.60

C

Computer interface	
Simple Serial Interface:	24.25
Trio of Transceiver/Computer Interfaces:	24.22
USB Interfaces for Your Ham Gear:	24.26
CW Keyer	
TiCK-4 -- A Tiny CMOS Keyer:	24.31
Universal Keying Adapter:	24.29

F

Filter, audio	
Audio Intelligibility Enhancer:	24.35
Filter, RF	
Band-pass filter for 145 MHz:	11.43
Broadcast-Band Reject Filter:	11.38
Crystal Ladder Filter for SSB:	11.36
Diplexer Filters:	11.40
Field Day Stub Assembly:	20.10

High-Performance, Low-Cost 1.8 to 54 MHz Low-Pass Filter:	11.42
Optimized Harmonic Transmitting Filters:	11.40
Wave Trap for Broadcast Stations:	11.39

O

Oscillator	
JFET Hartley VFO:	9.15
Low-noise Differential Oscillator:	9.12
Modified Vackar VFO:	9.12

P

Power source	
12-V, 15-A Power Supply:	7.50
13.8-V, 5-A Regulated Power Supply:	7.53
Adjustable Resistive Load:	7.54
Adjustable Tracking Power Supply:	7.61
Automatic Sealed-Lead-Acid Battery Charger:	7.58
Four-Output Switching Bench Supply:	7.48
High-Voltage Power Supply:	7.56
Inverting DC-DC Converter:	7.54
Overvoltage Crowbar Circuit:	7.63
Overvoltage Protection for AC Generators:	7.62
Reverse-Polarity Protection Circuits:	7.57

R

Receiver	
10 GHz Preamplifier:	12.33
430 MHz Preamplifier:	12.31
Configuring an RTL-SDR for Amateur Radio:	15.30
Dual-Band LNA for 2 Meters and 70 Centimeters:	12.30
Micro R2 SSB or CW Receiver:	12.13
Rock-Bending Receiver for 7 MHz:	12.3
RF Interference	
RF Sniffer:	27.41

S

Station accessory	
An Arduino-based Knob Box for SDR:	24.34
Audio Interface Unit for Field Day and Contesting:	24.40

T

Test equipment	
Bipolar Transistor Tester:	25.38
Fixed-Frequency Audio Oscillator:	25.42
Gate-Dip Oscillator:	25.49
High-Power RF Samplers:	25.47
Hybrid Combiners for Signal Generators:	25.49
Inductance Tester:	25.41
Logic Probe:	25.40
Low-frequency VNA Adaptor:	25.55
RF Current Meter:	25.44
RF Oscillators for Circuit Alignment:	25.48
RF Power Meter:	25.53
RF Step Attenuator:	25.46
RF Voltmeter:	25.54
Test probe adaptors:	25.6
Two-Tone Audio Generator:	25.43
Wide-Range Audio Oscillator:	25.42

Transceiver	
A West Coast Lightwave Project:	13.1
TAK-40 SSB/CW Transceiver:	13.33

Transmitter	
A 50 MHz CW Beacon Exciter:	13.38
MicroT2 Single-Band SSB Transmitter:	13.18
MkII Universal QRP Transmitter:	13.19, 13.30
Near-Space Tracker:	14.10
Pebble Crusher 7 MHz QRP CW Transmitter:	13.3
VHF Signal Sources (50 and 144 MHz):	13.20

Transverter	
A Microwave Transverter Controller:	13.35

Author Index

Author	Call	Topic	Section Ref	Page Ref
Adams, Chuck	K7QO	Making PC Boards With Printed Artwork	Chapter 25	CD-ROM
Allison, Bob	WB1GCM	Measuring Crystal Parameters	11.6.3	11.28
Applegate, Alan	KØBG	ARRL phase noise measurement	9.2.5	9.10
		Mobile antennas	21.8	21.51ff
		Mobile battery selection	7.13.8	7.37
		Mobile stations	29.2	29.9ff
Apte, Anisha		Oscillator design	Chapter 9	CD-ROM
Audet, Jacques	VE2CZX	Low-frequency VNA Adaptor	25.8.16	25.55
Bartholomew, Wayde	K3MF	Dual-band antenna for 146/446 MHz	Chapter 21	CD-ROM
Belrose, John	VE2CV	Mobile antenna efficiency	21.8.9	21.57
		Mobile ground losses	21.8.5	21.55
		Sloping antennas	21.5.1	21.33
Blackburn, Wally	AA8DX	Station Construction	Chapter 29	29.1ff
Blevins, Ken	K5ALQ	Adapting Aviation Headsets to Amateur Radio	Chapter 24	CD-ROM
Bloom, Alan	N1AL	Digital Mode Table	16.5	16.30
		Digital Signal Processing (DSP)	Chapter 15	15.1ff
		Modulation	Chapter 8	8.1ff
		Test Equipment and Measurements	Chapter 25	25.1ff
		Test Instrument Bibliography	Chapter 25	CD-ROM
Botkin, Dale	NØXAS	Digital Basics	Chapter 4	4.1ff
Bramwell, Denton	K7OWJ	RF Step Attenuator	25.8.9	25.46
Brenner, James	NT4B	Two-band Loop for 30 and 40 Meters	21.49	21.49
Britain, Kent	WA5VJB	Cheap Yagi antennas	21.11	21.69
Brown, Bill	WB8ELK	Remote Sensing Payloads	Chapter 14	14.8-10
Brown, Jim	K9YC	Ferrite materials	5.4	5.14ff
		Ferrite transmitting chokes	20.5.4	20.21ff
		Measuring chokes	Chapter 20	CD-ROM
		Placement of stubs used as harmonic filters	20.3.2	20.8
Buchmann, Isidor		Batteries and Charging	7.13	7.32-7.45
Bunsold, Pat	WA6MHZ	Refurbishing Vintage Equipment	26.11.5	26.38
Burningham, John	W2XAB	Introduction to DMR	18.5	18.14
Buxton, Al	W8NX	Multiband, coax-trap dipoles	21.1	21.21
Campbell, Jeremy	KC8FEI	Automotive RF interference	27.9	27.36ff
Campbell, Rick	KK7B	Binaural I-Q receiver	Chapter 12	CD-ROM
		Micro R2 Receiver	12.3.2	12.16
		RF semiconductor design	Chapter 5	5.1ff
		VHF Signal Sources	13.2	13.19
Cebik, LB	W4RNL	Fixed Moxons for Satellite Operation	21.11	21.65
		Inverted-U antenna	21.1	21.17
		Medium-gain 2 meter Yagi	21.11	21.61
Chen, Kok	W7AY	Unstructured Digital Modes	16.2	16.5ff
Christensen, Paul	W9AC	QSK Controller	24.16	24.43
Colville, Jim	W7RY	QSK Controller	24.16	24.43
Cooknell, DA	G3DPM	Oscillator construction	9.3.2	9.16
Coval, Jeff	ACØSC	<i>FLDIGI</i>	16.1	16.5
Cutsogeorge, George	W2VJN	Transmission Lines	Chapter 20	20.1ff
Danzer, Paul	N1II	Digital Basics	Chapter 4	4.1ff
		FM voice repeaters	Chapter 18	18.1ff
		Parallel-port interface	Chapter 4	CD-ROM
Daughters, George	K6GT	6 Meter Kilowatt Amplifier	17.12	17.49
Dehaven, Jerry	WAØACF	Phase-locked loops	9.7	9.34ff
Demaw, Doug	W1FB	Tuna Tin 2 transmitter	13.3.2	CD-ROM
Dobbs, George	G3RJV	QRP CW Transmitter for 7 MHz	13.3.2	13.5
Dodd, Peter	G3LDO	Skeleton Slot Antenna for 14-28 MHz	21.7	21.50
Doig, Al	W6NBH	Multiband quad antenna	21.7	21.43ff
Doyle, Tom	W9KE	A Raspberry Pi Server/Client for Antenna Rotators	24.6	24.18
Duffey, Jim	KK6MC	Circuit Construction	Chapter 23	23.1ff
Eenhoorn, Anjo	PAØZR	Active attenuator	Chapter 27	CD-ROM
Eisenberg, Joe	KØNEB	Construction Techniques	Chapter 23	23.1ff
Fisher, Burns	W2BFJ	Fox-1 Telemetry	Chapter 14	CD-ROM
Fitzsimmons, John	W3JN	Restoring vintage equipment	26.9	26.32
Fletcher, Terry	WAØITP	Reverse-Polarity Protection Circuits	7.16.5	7.51
Ford, Jim	N6JF	Return Loss Bridge	25.8.12	CD-ROM
Ford, Steve	WB8IMY	Digital Communications	Operating Supplement	CD-ROM
		Space Communications	Operating Supplement	CD-ROM
Frey, Dick	K4XU	250 W Broadband Linear Amplifier	17.11	17.36
		RF Transistor tables	Chapter 22	22.28-31
		Solid-state amplifiers	17.26-17.30	17.29ff
Geiser, Dave	W5IXM	Simple seeker RFI receiver	Chapter 27	CD-ROM
Gordon-Smith, Dave	G3UUR	Crystal filters	11.6	11.30ff

Author	Call	Topic	Section Ref	Page Ref
Grebenkamper, John	KI6WX	Tandem match	25.8.14	CD-ROM
Grover, Dale	KD8KYZ	PC-board CAD	6.3	6.31ff
Gruber, Mike	W1MG	RF Interference	Chapter 27	27.1ff
Grumm, Linley	K7HFD	Low-noise oscillator	9.3.2	9.15
Hallas, Joel	W1ZR	Annual Transceiver Survey	CD-ROM	CD-ROM
		Handbook History	CD-ROM	CD-ROM
		Receiver and Transmitter Architectural History	CD-ROM	CD-ROM
		Receivers	Chapter 12	12.1ff
		Transceivers	Chapter 14	14.1ff
		Transmitters	Chapter 13	13.1ff
Halstead, Roger	K8RI	Amplifier tuning	17.9	17.26
		Surplus amplifier parts	17.11	17.44
Hansen, Markus	VE7CA	A West Coast Lightwave Project	Chapter 13	13.1
		High-Performance HF Transceiver - HBR-2000	Chapter 14	CD-ROM
Harden, Paul	NA5N	Component Data and References	Chapter 22	22.1ff
Hare, Ed	W1RFI	Circuit Construction	Chapter 23	23.1ff
		RF Interference	Chapter 27	27.1ff
		Troubleshooting and Maintenance	Chapter 26	26.1ff
Hartnagel, Hans		The Dangers of Simple Usage of Microwave Software	Chapter 6	CD-ROM
Hayward, Roger	KA7EXM	JFET Hartley VFO	9.3.2	9.17
Hayward, Wes	W7ZOI	JFET Hartley VFO	9.3.2	9.17
		Oscillator temperature compensation	9.3.5	9.19
		RF semiconductor design	Chapter 5	5.1ff
		Segment-tuned VCO	9.7.7	9.50
Henderson, Dan	N1ND	RFI Management	27.2	27.4
Henderson, Randy	WI5W	Rock-bending Receiver for 7 MHz	12.2.1	12.5
Hilding, Rick	K6VVA	Remote Stations	29.4	29.18ff
Hollingsworth, Riley	K4ZDH	RF Interference and the FCC	27.2	27.10
Honnaker, Scott	N7SS	Digital Modes	Chapter 16	16.1ff
Hood, Mike	KD8JB	All-copper, 2 meter J-pole antenna	Chapter 21	CD-ROM
Horrabin, Colin	G3SBI	High-Performance 45 MHz IF	Chapter 12	CD-ROM
Hranac, Ron	NØIVN	Cable and digital television	27.8.3-27.8.4	27.29ff
		HDTV modulation	8.3	8.11
Humbertson, Ken	WØKAH	<i>FLDIGI</i>	16.1	16.5
Hutchinson, Chuck	K8CH	Antennas	Chapter 21	21.1ff
Hutchinson, Sylvia	K8SYL	75 and 10 meter dipole	Chapter 21	CD-ROM
Jones, Bill	K8CU	1.8 to 54 MHz Low-Pass Filter	11.11.6	11.49
Jones, Dave	KB4YZ	Slow-scan television	Operating Supplement	CD-ROM
Karlquist, Rick	N6RK	Audio latency measurement system	29.4.3	29.21
		Mixers, Modulators, and Demodulators	Chapter 10	10.1ff
Kay, Leonhard	K1NU	Analog Basics	Chapter 3	3.1ff
		RF Techniques	Chapter 5	5.1ff
Keuken, Jack	KE2QJ	Base-loading system for whip antennas	21.8.3	21.54
Kleinschmidt, Kirk	NTØZ	Generators	29.3	29.13
Klitzing, James	W6PQL	All-Mode, 2 Meter, 80 W Linear Amp	17.11	17.38
Kocsis, Jim	WA9PYH	Dual Band LNA for 2 Meters and 70 Centimeters	Chapter 12	CD-ROM
Lakhe, Rucha		Mathematical stability problems in modern non-linear simulation programs	Chapter 6	CD-ROM
Lampereur, Steve	KB9MWR	10 GHz 2 W Amplifier	17.11	17.40
Langton, Anthony	GM4THU	RF Voltmeter	25.8.15	25.54
Lapin, Greg	N9GL	Analog Basics	Chapter 3	3.1ff
Larkin, Bob	W7PUA	RF semiconductor design	Chapter 5	5.1ff
Lau, Zack	W1VT	ARRL phase noise measurement	9.2.5	9.10
		Triband dipole for 30, 17, and 12 meters	21.2	21.22
Lewellan, Roy	W7EL	JFET Hartley VFO	9.3.2	9.17
Lindquist, Rick	WW1ME	What Is Amateur Radio	Chapter 1	1.1ff
Loveall, Pete	AE5PL	D-STAR repeaters	18.4	18.11
Luetzelschwab, Carl	K9LA	Propagation	Chapter 19	19.1ff
Lux, Jim	W6RMK	Electrical Safety	28.1	28.1ff
Martin, Mike	K3RFI	Power-line RF Noise	27.6	27.17ff
McClellan, Jim	N5MIJ	D-STAR repeaters	18.4	18.11
McCune, Earl	WA6SUH	Oscillators	Chapter 9	9.1
McDonald, Steve	VE7SL	A West Coast Lightwave Project	Chapter 13	13.1
Miller, Russ	N7ART	2 meter RF power amplifier	Chapter 17	CD-ROM
Moell, Joe	KØOV	Radio Direction-finding antennas	21.12	21.72ff
		Radio Direction-finding techniques	Chapter 27	CD-ROM
Montgomery, Christine	KGØGN	Digital Basics	Chapter 4	4.1ff
Morris, Steve	K7LXC	Tower and antenna safety	28.2	28.12ff
Mullett, Chuck	KR6R	CAD for power supplies	17.11	17.28
Newkirk, David	W9BRD	Computer-Aided Circuit Design	Chapter 6	6.1ff
		Mixers, Modulators, and Demodulators	Chapter 10	10.1ff
O'Hara, Tom	W6ORG	Amateur television	Operating Supplement	CD-ROM
Ott, Henry	WA2IRQ	Electromagnetic Compatibility	Chapter 27	27.1ff
Pearce, Gary	KN4AQ	FM voice repeaters	Chapter 18	18.1ff

Author	Call	Topic	Section Ref	Page Ref
Pittenger, Jerry	K8RA	3XC1500D7 RF Linear Amplifier	17.11	17.45
Pocock, Emil	W3EP	Propagation	Chapter 19	19.1ff
Portune, John	W6NBC	Coaxial Dipole for VHF or UHF	Chapter 21	21.64
Rado, John	KØIZ	Adapting Aviation Headsets to Amateur Radio	Chapter 24	24.34
Rauch, Tom	W8JI	RF Current Meter	25.8.7	25.44
Retzler, András	HA7ILM	Configuring an RTL-SDR Receiver	15.7.3	15.30
Rogers, Robert	WA1PIO	Inductance Tester	25.8.3	25.41
Rohde, Ulrich	N1UL	2 meter down-converter	12.7.4	12.34
		Butler oscillator	9.5.4	9.27
		Mathematical stability problems in modern non-linear simulation programs	Chapter 6	CD-ROM
		Measuring intermodulation performance	10.4	10.16
		Mixer performance capability	Chapter 10	CD-ROM
		Modified Vackar oscillator	9.3.1	9.15
		Oscillator design	Chapter 9	CD-ROM
		Phase noise	Chapter 9	CD-ROM
		Simulation at RF	6.3	6.28ff
		Testing mixer performance	10.5	10.21
		The Dangers of Simple Usage of Microwave Software	Chapter 6	CD-ROM
		Using Simulation at RF	Chapter 6	CD-ROM
		VHF/UHF Grounded-base Oscillator	Chapter 9	CD-ROM
Rowe, David	VK5DGR	Digital Voice - CODEC2	16.4.5	16.15
Sabin, Bill	WØIYH	Conversion Loss in Mixers	10.5.2	10.19ff
		CW Key Waveform	13.3.7	13.17
		Diplexer Filter	11.11.5	11.46
		Half-Lattice Single-Crystal Filter	11.6	11.31
		IF Speech Clipper	13.3.6	13.16
		<i>MATCH</i> by WØIYH	20.4.2	CD-ROM
		<i>MATCH</i> by WØIYH	5.6	CD-ROM
		Superhet Receiver	12.3.2	12.15
		Thermistor Uses	2.15.10	2.70
		Transmission-line transformers	20.5.2	20.19ff
Sapp, Michael	WA3TTS	VHF/UHF Beacon Transmitters	13.5.4	13.38
Severns, Rudy	N6LF	Power Sources	Chapter 7	7.1ff
Silver, Ward	NØAX	Amplifier maintenance	26.5.4	26.21
		Analog Basics	Chapter 3	3.1ff
		Antennas	Chapter 21	21.1ff
		Electrical Fundamentals	Chapter 2	2.1ff
		Filters	11.1-11.4	11.1ff
Siwiak, Kai	KE4PT	Discussion of Q	2.11, 2.16	2.49, 2.56
Stanley, John	K4ERO	Amplifiers, Vacuum-Tube	17.1-17.9	17.1ff
		Everyham's Amp	17.11	17.42
		Optimum Ground Systems	21.3.1	21.23
Steffka, Mike	WW8MS	Automotive RF Interference	27.9	27.36ff
Stein, William	KC6T	Multiband quad antenna	21.7	21.43ff
Stewart, Jim		Inverting DC-DC Converter	7.16.5	7.54
Stockton, David	GM4ZNX	Fractional-n Synthesizers	9.7.3	9.41
		Oscillators	9.1-9.6	9.1ff
		Poles and zeros	3.1.2	3.3
Stott, Michael	VE3EBR	An Arduino-based Knob Box for SDR	24.13	24.34
Stroud, Dick	W9SR	Top-loaded, low-band antenna	21.3.3	21.29
Straw, Dean	N6BV	Antenna modeling and design	Chapter 21	21.1ff
		HFTA antenna modeling software	29.4.2	29.18
		Transmission Lines	Chapter 20	20.1ff
Stuart, Ken	W3VVN	Power Sources	Chapter 7	7.1ff
Tayloe, Dan	N7VE	Active Filters	11.5	CD-ROM
		Tayloe mixer	10.5.5	10.28
Taylor, Joe	K1JT	Background noise	5.8.9	5.33ff
		Earth-Moon-Earth (EME) Communications	Operating Supplement	CD-ROM
Taylor, Roger	K9ALD	DC circuits and resistance	Chapter 2	2.1ff
Telewski, Fred	WA7TZY	Poles and zeros	3.1.2	3.3
		Synthesizers	9.7	9.33ff
Thompson, Chris	AC2CZ	Fox-1 Telemetry	Chapter 14	CD-ROM
Thompson, Tom	WØIVJ	High-Power RF Samplers	25.8.10	25.47
Tonne, Jim	W4ENE	Filters	11.1-11.4	11.1
		Optimized Harmonic Transmitting Filters	11.11.4	11.46
Ulbing, Sam	N4UAU	Surface-mount technology	Chapter 23	CD-ROM
Veatch, Jim	WA2EUJ	TAK-40 SSB/CW Transceiver	14.7.2	14.19
Verhage, Paul	KD4STH	Near-space Tracker	14.3.3	14.10
		Remote Sensing and Navigation Data	Chapter 14	14.1-8
Wade, Paul	W1GHZ	Microwave Construction Techniques	23.6	23.26-28
		Noise theory	Chapter 5	CD-ROM
Wetherhold, Ed	W3NQN	Broadcast-band Reject Filter	11.1.2	11.45
Whitten, Mel	KØPFX	Digital Voice	16.4.5	16.15
Yoshida, Wayne	KH6WZ	Surface-mount device desoldering	Chapter 23	CD-ROM
Youngblood, Gerald	K5SDR	Tayloe mixer	10.5.5	10.28